



OP-Amp Characteristics

DC Characteristics

→ The non-ideal dc characteristics that add error components to the dc op voltage are:


- i) Input bias current
- ii) Input offset current
- iii) Input offset voltage
- iv) Thermal drift

i) Input Bias Current

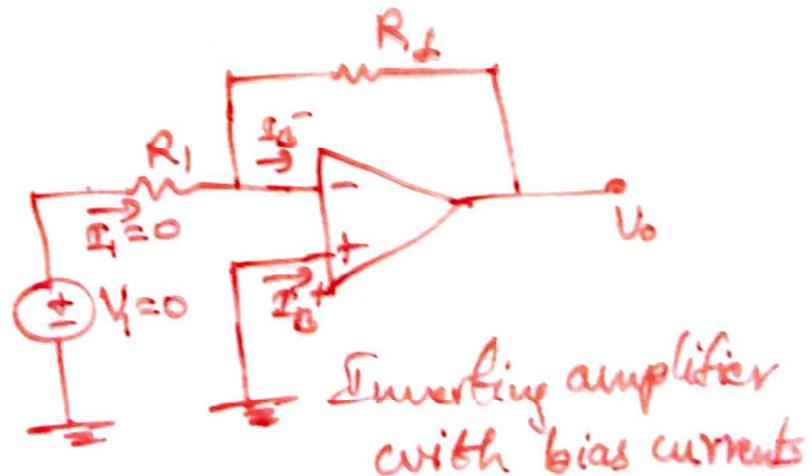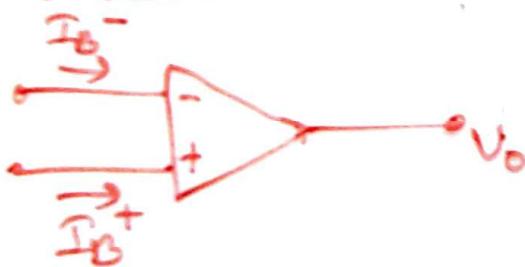

- In ideal op-amp, no current is drawn from the i/p terminals.
- Practically, i/p terminals conduct a small value of dc current to bias the i/p transistors
- Manufacturers specify i/p bias current I_B as the average value of base currents entering into the terminals of an op-amp. So $I_B = \frac{I_B^+ + I_B^-}{2}$

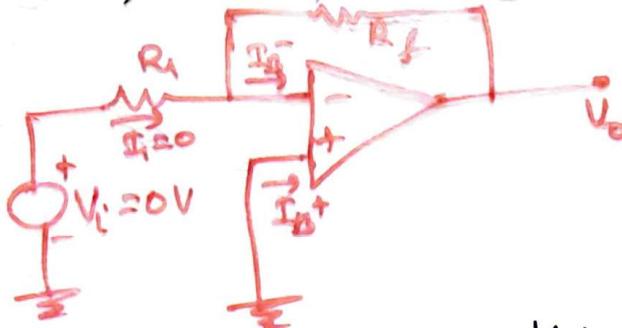→ Consider an inverting amplifier with i/p voltage $V_i = 0V$, the o/p voltage V_o should be zero volt




→ But we find the o/p voltage is offset by $V_o = (I_B^-) R_f$

→ For a 741 op-amp, with 1M Ω feedback resistor, $V_o = 500 \text{ nA} \times 1 \text{ M}\Omega = 500 \text{ mV}$

→ O/p is driven to 500 mV with zero i/p because of bias currents

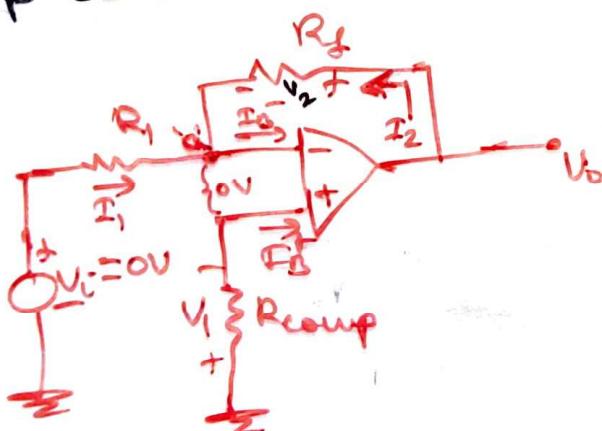→ This effect can be compensated by adding a compensation resistor R_{comp} b/w non-inverting i/p terminal & ground.



$$V_1 = I_B^+ R_{\text{comp}}$$

$$\Rightarrow I_B^+ = \frac{V_1}{R_{\text{comp}}}$$

→ With $V_i = 0$

$$I_1 = \frac{V_1}{R_1}$$

$$I_2 = \frac{V_2}{R_f}$$

$$\left. \begin{aligned} V_1 + 0 - V_2 + V_o &= 0 \\ \Rightarrow V_o &= V_2 - V_1 \end{aligned} \right\} \rightarrow \text{for compensation } V_o \text{ should be zero for } V_i = 0$$

$$\therefore V_2 = V_1$$


$$\Rightarrow I_2 = \frac{V_1}{R_f}$$

$$\rightarrow \text{At node 'a'} \quad I_B^- = I_2 + I_1 = \frac{V_1}{R_f} + \frac{V_1}{R_1} = V_1 \frac{(R_f + R_1)}{R_f R_1}$$

→ Assuming $I_B^- = I_B^+$

$$\frac{V_1 (R_1 + R_f)}{R_1 R_f} = \frac{V_1}{R_{\text{comp}}} \Rightarrow R_{\text{comp}} = \frac{R_1 R_f}{R_1 + R_f} = R_1 / R_f$$

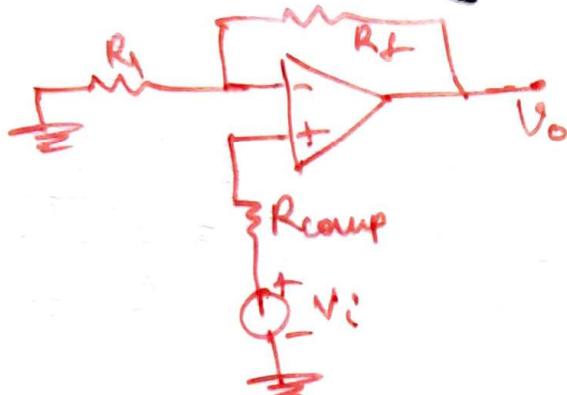→ The effect of i'lp bias current in a non-inverting amplifier can also be compensated by placing a compensating resistor, R_{comp} in series with the i/p signal V_i



→ The value of R_{comp} is again equal to $R_{comp} = R_f \parallel R_i$

Input Offset Current

- Bias current compensation will work if both bias currents I_B^+ & I_B^- are equal.
- Always there will be some small difference b/w I_B^+ & I_B^- . This difference is called offset current I_{os}

$$|I_{os}| = I_B^+ - I_B^-$$

- Absolute value indicates that there is no way to predict which currents will be larger.
- I_{os} for BJT op-amp is 200nA
- I_{os} for FET op-amp is 10pA

$$V_i = I_B^+ R_{comp}$$

$$I_1 = \frac{V_i}{R_i}$$


$$\rightarrow \text{At node 'a'} \quad I_2 = I_B^- - I_1 = I_B^- - \left(I_B^+ \frac{R_{comp}}{R_i} \right)$$

$$V_o = I_2 R_f - V_i = I_2 R_f - I_B^+ R_{comp}$$

$$= \left(I_B^- - I_B^+ \frac{R_{comp}}{R_i} \right) R_f - I_B^+ R_{comp}$$

$$\Rightarrow V_o = R_f [I_B^- - I_B^+] \Rightarrow V_o = R_f I_{os}$$

- Even with bias current compensation & with feedback resistor of $1M\Omega$, a 741 BJT op-amp has an o/p offset voltage. $V_o = 1M\Omega \times 200nA = 200mV$ with a zero i/p voltage.
- This effect of offset current can be minimized by keeping feedback resistance small.
- To obtain high i/p impedance, R_i must be kept large.
- With R_i large, the feedback resistor R_f must also be high so as to obtain reasonable gain.

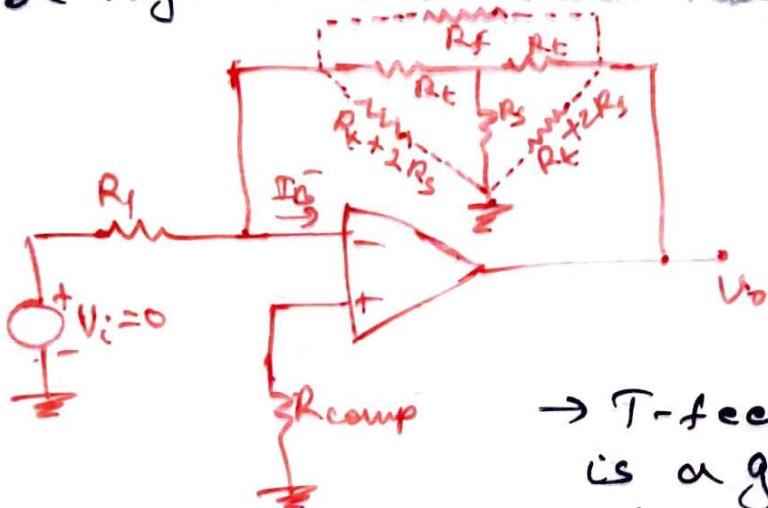

→ T-feedback n/w
is a good solution,
which allows large



feedback resistance, while keeping the resistance to ground low

$$\rightarrow \text{By T to } \pi \text{ conversion, } R_f = \frac{R_t^2 + 2R_t R_s}{R_s}$$


$$\rightarrow \text{To design a T n/w first pick } R_t \ll \frac{R_f}{2}, \\ \text{then calculate } R_s = \frac{R_t^2}{R_f - 2R_t}$$

Input Offset Voltage

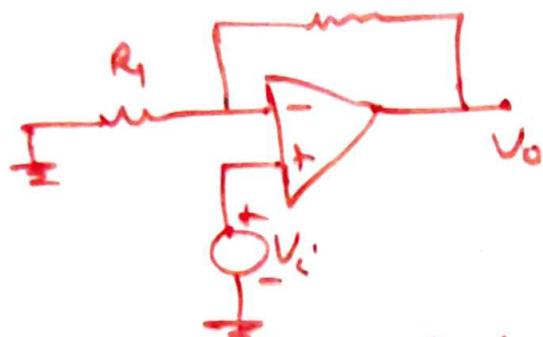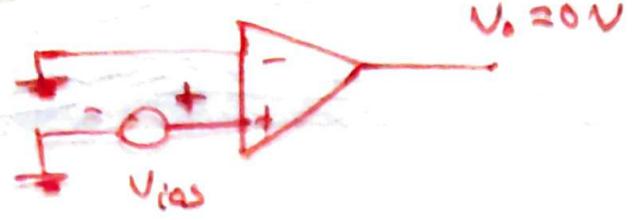
- Due to unavoidable imbalances inside the op-amp & one have to apply a small voltage at the i/p terminals to make off voltage zero for zero i/p voltage.
- This voltage is called i/p offset voltage, V_{ios} .



Non-inverting Amplifier

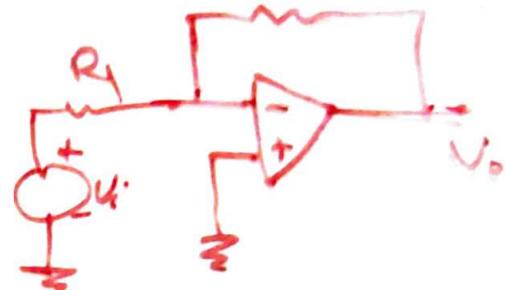

Inverting Amplifier

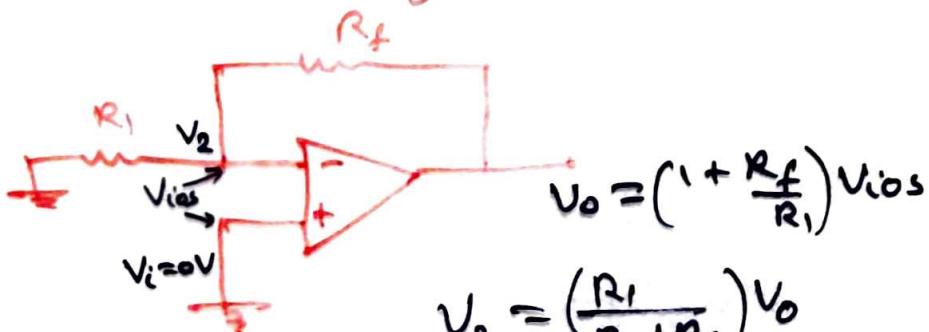

$$V_o = \left(1 + \frac{R_f}{R_1}\right) V_{ios}$$

$$V_2 = \left(\frac{R_1}{R_1 + R_f}\right) V_o$$

$$V_o = \left(\frac{R_1 + R_f}{R_1}\right) V_2 = \left(1 + \frac{R_f}{R_1}\right) V_2$$

$$V_{ios} = |V_i - V_2| \quad \& \quad V_i = 0$$

$$V_{ios} = V_2$$

$$\therefore V_o = \left(1 + \frac{R_f}{R_1}\right) V_{ios}$$


Total Output Offset Voltage

$$V_{OT} = \left(1 + \frac{R_f}{R_1}\right) V_{ios} + R_f I_B$$

→ V_{OT} could be either more or less than the offset voltage produced at o/p due to i/p bias current or i/p offset voltage alone. (since V_{ios} & I_B could be either positive or negative w.r.t ground)

→ With R_{comp} in the ckt, $V_{OT} = \left(1 + \frac{R_f}{R_1}\right) V_{ios} + R_f I_{los}$

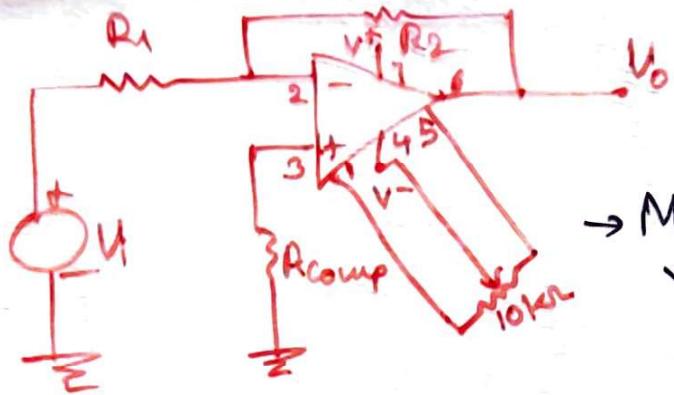→ Many op-amps provide offset compensation pins to nullify the offset voltage.



→ Manufacturers recommend that a 10k potentiometer be placed across offset null pins 1 & 5 & wiper be connected to negative supply pin 4.

- The position of wiper is adjusted to nullify the o/p offset voltage.

Thermal Drift


- Bias current, offset current & offset voltage change with temperature.
- A ckt nulled at 25°C may not remain same when temp. rises to 35°C . This is called drift.
- Offset current drift is expressed in $\text{nA}/^{\circ}\text{C}$ & offset voltage drift in $\text{mV}/^{\circ}\text{C}$ (indicates change in offset for each degree Celsius change in temp.)
- Carefully printed ckt board layout must be used to keep op-amps away from source of heat.
- Forced air cooling may be used to stabilize the ambient temp.

AC Characteristics

Frequency Response

- Ideally op-amp should have infinite bandwidth.

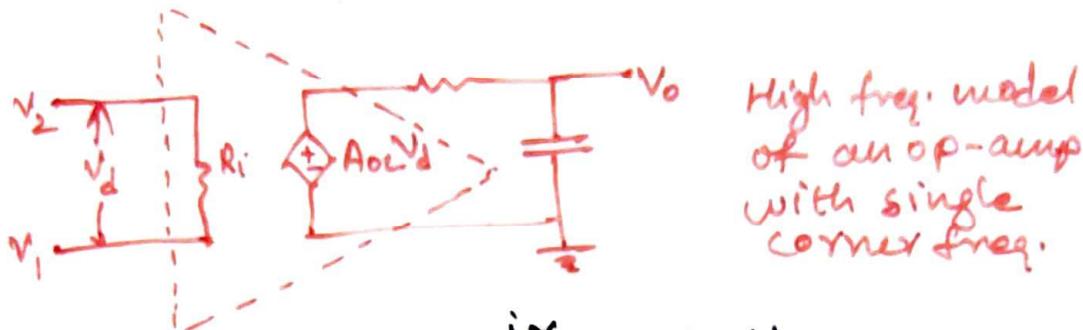→ But practical op-amp gain decreases (rolls-off) at higher freq's, because of a capacitive component in the equivalent ckt of op-amp.




$$V_0 = \frac{-jX_C}{R_O - jX_C} A_{OL} V_d$$

$$A = \frac{V_0}{V_d} = \frac{A_{OL}}{1 + j^2\pi f R_O C}$$


$$A = \frac{A_{OL}}{1 + j(f/f_i)} \text{ where } f_i = \frac{1}{2\pi R_O C}$$

$$|A| = \frac{A_{OL}}{\sqrt{1 + (f/f_i)^2}}$$

$$\phi = -\tan^{-1}(f/f_i)$$

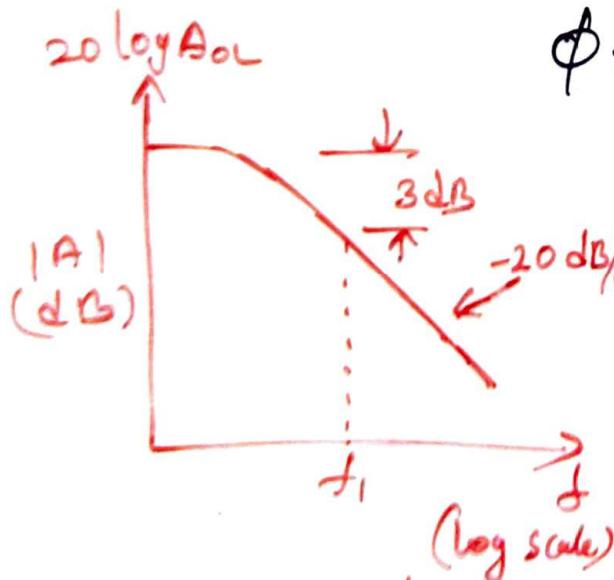


Magnitude characteristics

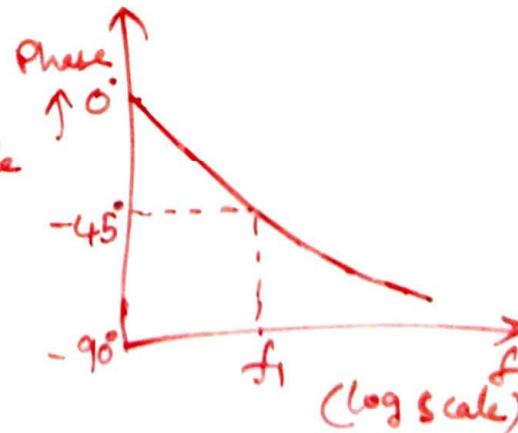

Phase Characteristics

Stability of an Op-amp

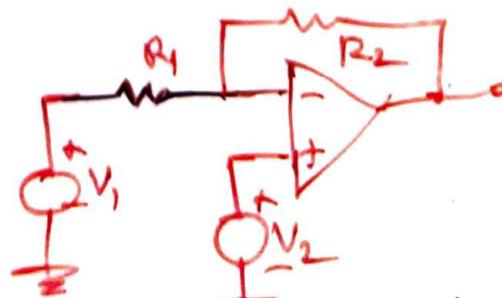→ Consider an op-amp amplifier with resistor feed back n/w & may be used as inverting amp. for $V_1 > 0$



& as non-inverting amp. for $V_1 < 0$

→ From negative feedback concepts, closed loop transfer function $A_{CL} = \frac{A}{1+AB}$ where A is open loop voltage gain & B is feedback ratio

→ If characteristic equation $(1+AB)=0$, circuit will become unstable, leads into sustained oscillations.

$$1 - (-AB) = 0$$

$$\text{loop gain, } -AB = 1$$


→ Since AB is complex quantity, $|AB|=1$

& $\angle AB = 0$ (or multiple of 2π)

$\angle AB = \pi$ (or odd multiple of π)

$$A = \frac{A_{OL}}{(1+\frac{j}{f_1})(1+\frac{j}{f_2})(1+\frac{j}{f_3})}, \text{ if } f_1 < f_2 < f_3$$
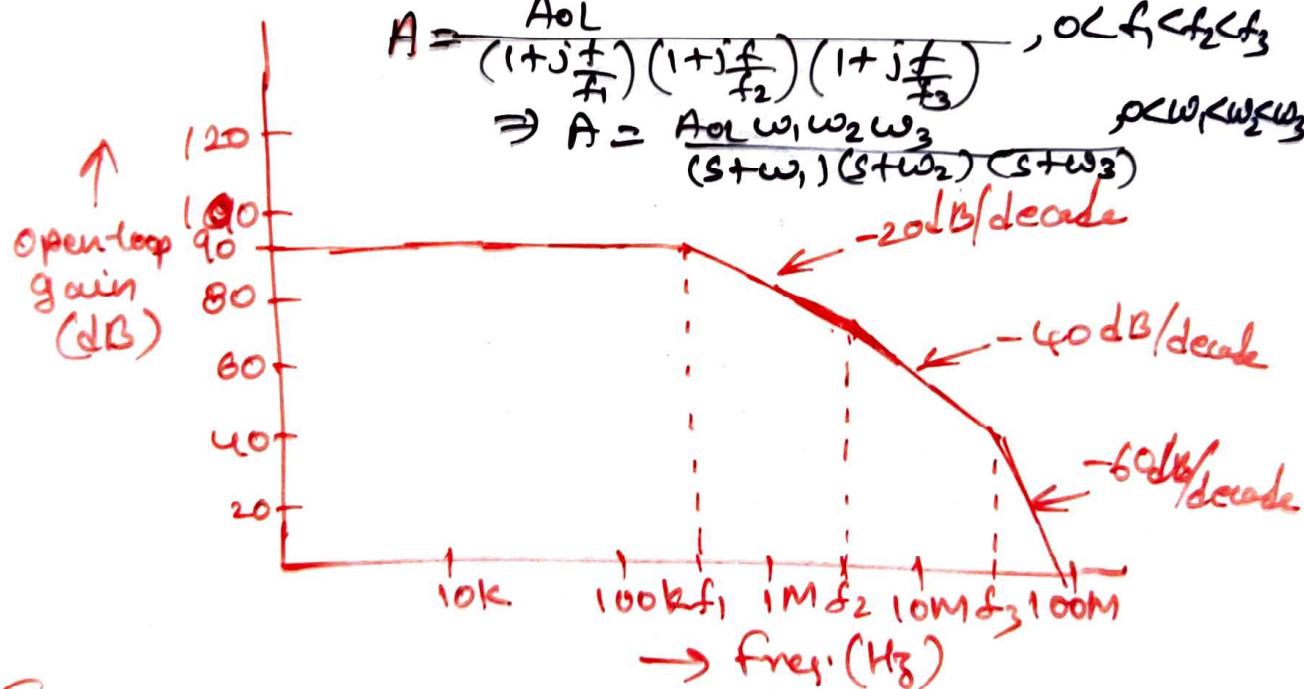
$$\Rightarrow A = \frac{A_{OL} \omega_1 \omega_2 \omega_3}{(s+\omega_1)(s+\omega_2)(s+\omega_3)}, \text{ if } \omega_1 < \omega_2 < \omega_3$$



Frequency Compensation

→ In applications where one needs large bandwidth & lower closed loop gain, suitable compensation techniques are used.


→ Two types of compensation techniques
 i) External Compensation
 ii) Internal Compensation

External Frequency Compensation

49

- Externally connected compensating N/w alters the open-loop gain, so that roll-off rate is -20 dB/decade over a wide range of freq.
- Dominant-pole compensation
- Pole-zero (lag) compensation

Dominant-pole compensation

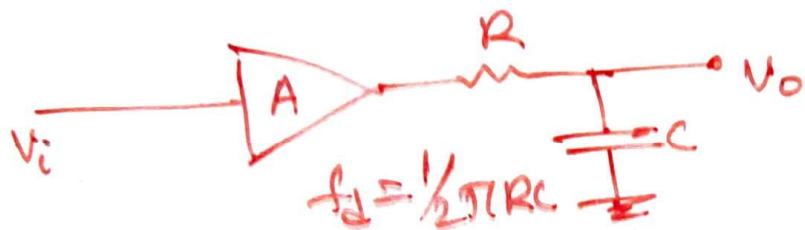

- A is uncompensated transfer function of op-amp in open-loop condition.
- Introducing a dominant pole by adding RC N/w in series with op-amp by connecting a capacitor C from a suitable high resistance point to ground
- The compensated transfer function A' becomes

$$A' = \frac{V_o}{V_i}$$


$$= A \cdot \frac{-j/\omega_C}{R-j/\omega_C} = \frac{A}{1+j\frac{f}{f_d}}$$

where $f_d = \frac{1}{2\pi RC}$

$$\therefore A' = \frac{A_0}{(1+j\frac{f}{f_d})(1+\frac{f}{f_1})(1+j\frac{f}{f_2})(1+j\frac{f}{f_3})}$$

where $f_d < f_1 < f_2 < f_3$

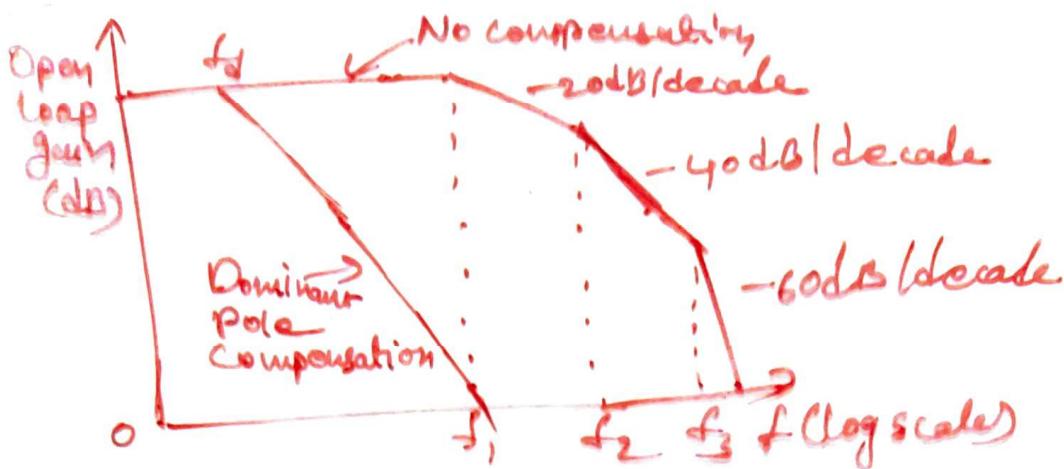
- The capacitance C is chosen so that the modified loop gain drops to 0dB with a slope of -20 dB/decade at a freq' where poles of uncompensated E/F/A contribute negligible phase shift.



- One disadvantage of this technique is that it reduces the open-loop bandwidth drastically
- But noise immunity of the system is improved since the noise freq. Components outside the bandwidth are eliminated.

Pole-zero Compensation

→

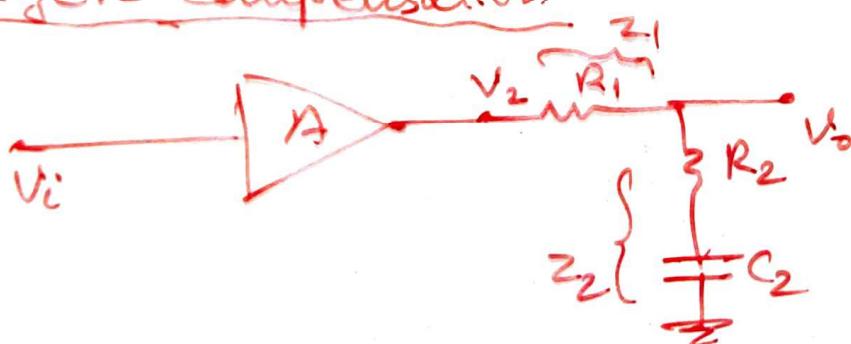


- Uncompensated transfer function A is altered by adding both a pole & a zero
- The zero should be at higher freq. than pole

$$\frac{V_0}{V_2} = \frac{Z_2}{Z_1 + Z_2} = \frac{R_2}{R_1 + R_2} \frac{1 + j \frac{f}{f_1}}{1 + j \frac{f}{f_0}}$$

where $Z_1 = R_1$, $Z_2 = R_2 + \frac{1}{j\omega C_2}$, $f_0 = \frac{1}{2\pi(R_1 + R_2)C_2}$

$$f_0 = \frac{1}{2\pi R_2 C_2}$$

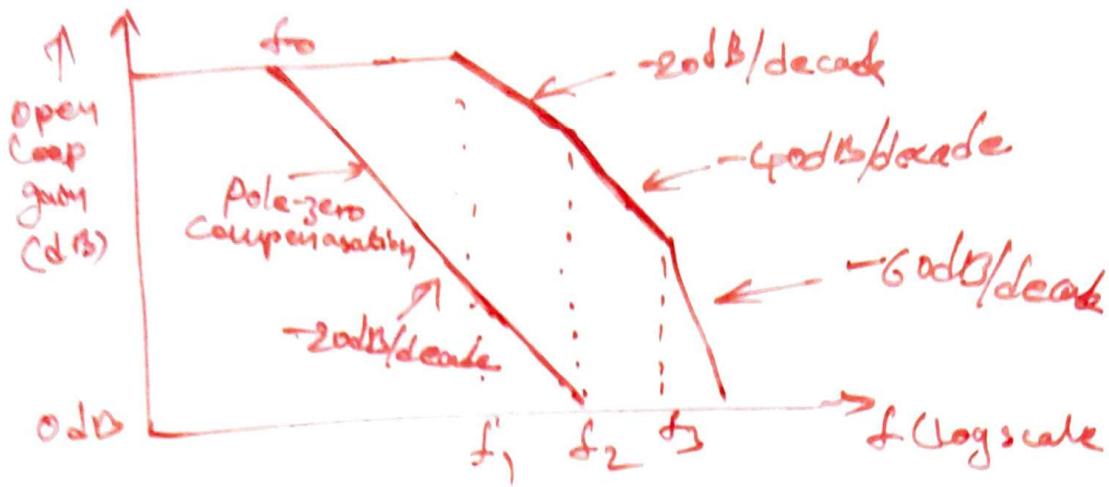


$$\begin{aligned}
 A' &= \frac{V_o}{V_i} = \frac{V_o}{V_2} \cdot \frac{V_2}{V_i} = A \cdot \frac{R_2}{R_1 + R_2} \cdot \frac{1 + j\frac{f}{f_1}}{1 + j\frac{f}{f_0}} \\
 &= \frac{A_{OL}}{(1 + j\frac{f}{f_1})(1 + j\frac{f}{f_2})(1 + j\frac{f}{f_3})} \cdot \frac{R_2}{R_1 + R_2} \cdot \frac{1 + j\frac{f}{f_1}}{1 + j\frac{f}{f_0}} \\
 &= \frac{A_{OL}}{(1 + j\frac{f}{f_0})(1 + j\frac{f}{f_2})(1 + j\frac{f}{f_3})}
 \end{aligned}$$

with $0 < f_0 < f_1 < f_2 < f_3$

$\Rightarrow R_2 \gg R_1$, so that $\frac{R_2}{R_1 + R_2} \approx 1$

Internally compensated Op-amp

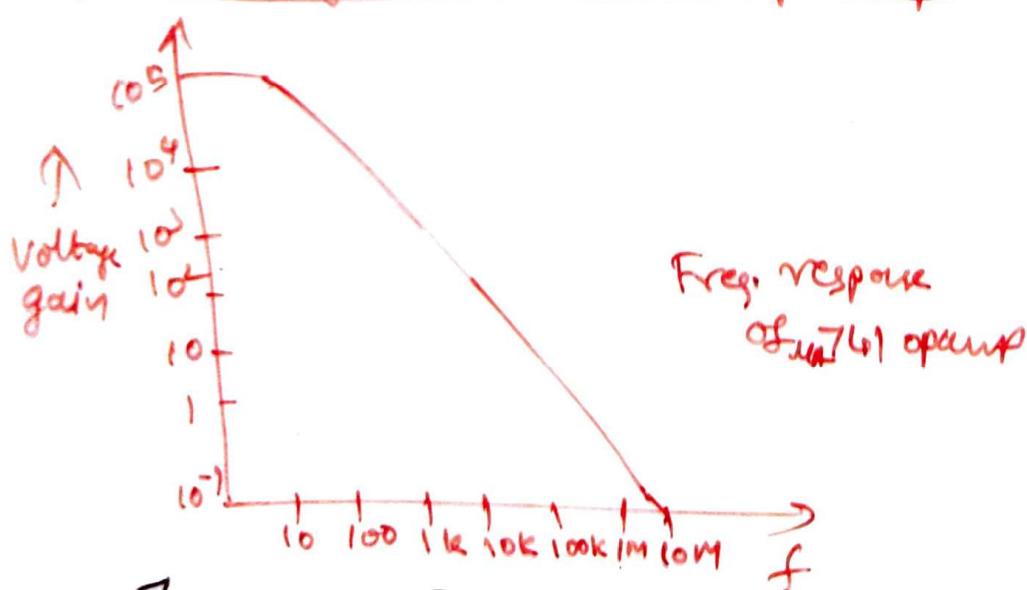

→ The op-amp IC 741 contains a capacitance C_1 of $\frac{30}{PR}$ pF that internally shorts off signal capacitive current f thus reduces the op signal at higher freq's

Slew Rate


20

- Slew rate is defined as the max. rate of change of o/p voltage caused by a step i/p voltage & is specified in V/us.
- A 1V/us slew rate means that the o/p rises or falls by 1V in 1us.
- An ideal slew rate is infinite which means that op-amp's o/p voltage should change instantaneously in response to i/p step voltage.
- Practical LC op-amps have slew rates from 0.1V/us to above 1000 V/us.
- Slew rate improves with higher closed loop gain & dc supply voltage.
- It is also a function to temp. & decreases with an increase in temp.
- A capacitor within or outside an op-amp prevents the o/p voltage from responding immediately to a fast changing i/p.
- The rate at which voltage across capacitor increases is given by,
$$\frac{dV_c}{dt} = \frac{I}{C}$$
 where I is the max. current to capacitor C
- So for obtaining faster slew rate, op-amp should have either a higher current or a small compensating capacitor.
- For 741C, max internal capacitor charging current limited to about 15mA

$$SR = \frac{dV_c}{dt}_{\text{max}} = \frac{I_{\text{max}}}{C} = \frac{15 \mu\text{A}}{30 \mu\text{F}} = 0.5 \text{V/us}$$

Slew Rate

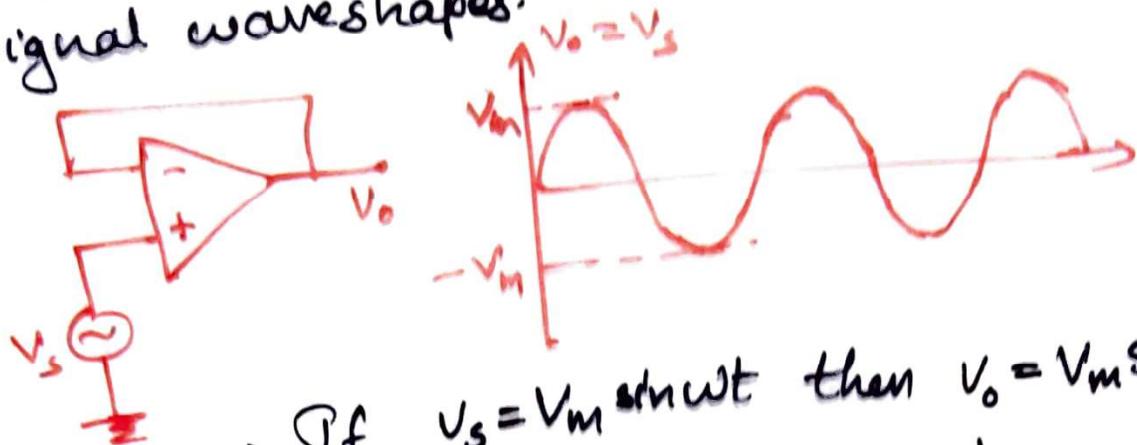→ Slew rate limits the response speed of all large signal waveshapes.



$$\rightarrow \text{If } V_s = V_m \sin \omega t \text{ then } V_o = V_m \sin \omega t$$

→ Rate of change of o/p is given by

$$\frac{dV_o}{dt} = V_m \omega \cos \omega t$$

→ Max. rate of change of o/p occurs when $\cos \omega t = 1$

$$SR = \left. \frac{dV_o}{dt} \right|_{\text{max}} = \omega V_m$$

$$\therefore \text{Slew Rate} = 2\pi f V_m \text{ V/s}$$

$$= \frac{2\pi f V_m}{10^6} \text{ V/us}$$

where $f = \text{i/p freq. (Hz)}$

$V_m = \text{peak o/p amplitude}$

→ If freq. or amplitude of i/p signal is increased to exceed slew rate of op-amp, the o/p will be distorted.

→ So the max. i/p freq. f_{max} at which we can obtain an undistorted o/p voltage of peak value

$$V_m \text{ is given by } f_{\text{max}} (\text{Hz}) = \frac{\text{Slew Rate}}{6.28 \times V_m} \times 10^6$$

→ f_{max} is also called full power response