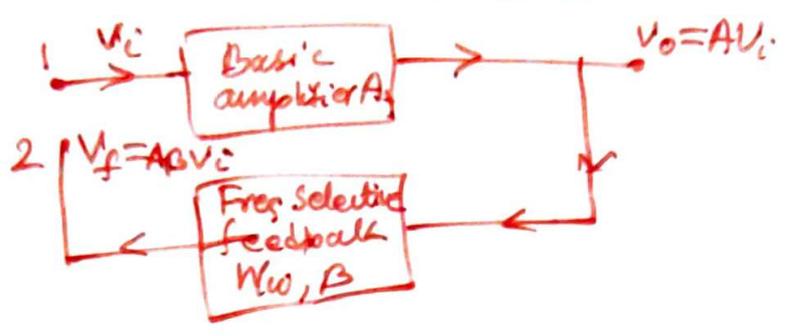


# Basic Principle of Sine Wave Oscillators



$$V_o = AV_i$$

$$V_f = BV_o = ABV_i$$

∴ The quantity  $AB$  represents loop gain of system

→ If  $A$  &  $B$  are adjusted so that  $AB=1$ , the feedback signal  $V_f$  will be identically equal to externally applied signal  $V_i$

→ Barkhausen criterion for oscillations

$$|AB| = 1$$


$$\angle AB = 0^\circ \text{ or multiples of } 2\pi$$


→ There are different types of sine wave oscillators

↳ RC-phase shift oscillators can provide freq's varying from a few Hz to several hundred kHz

↳ LC oscillators are suitable for high freq's up to hundreds of MHz.

## RC-Phase Shift Oscillator

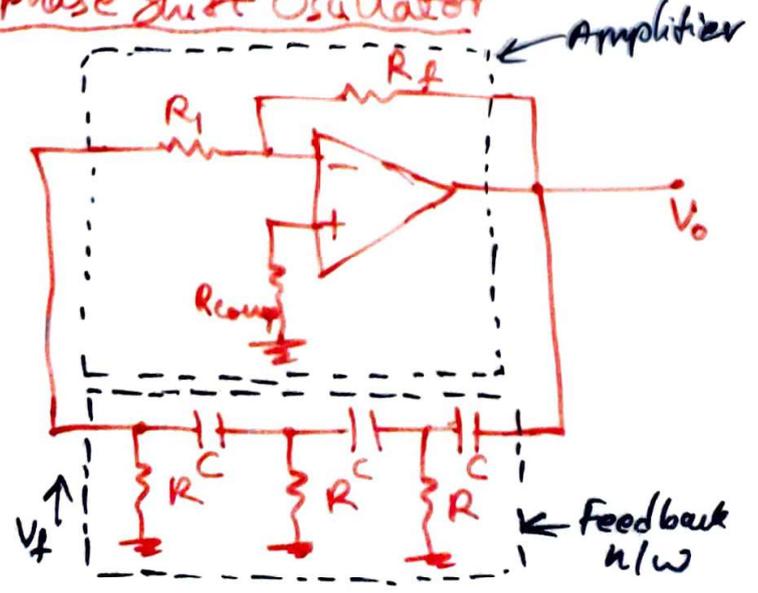

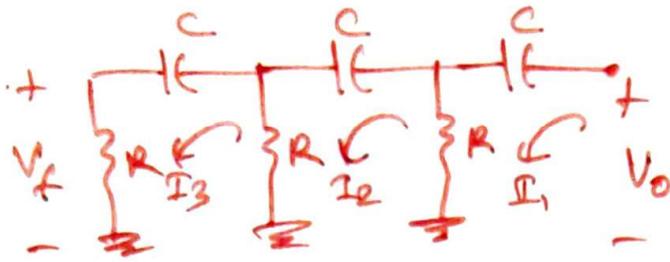

- Op-amp is used in inverting mode therefore provides  $180^\circ$ .
- Additional phase of  $180^\circ$  is provided by RC feedback  $\eta_w$  to obtain total phase shift of  $360^\circ$ .
- Each of the RC stage provides a  $60^\circ$  phase shift so that the total phase shift due to feedback  $\eta_w$  is  $180^\circ$ .

$$I_1 \left( R + \frac{1}{sC} \right) - I_2 R = V_o \quad \text{--- (1)}$$

$$-I_1 R + I_2 \left( 2R + \frac{1}{sC} \right) - I_3 R = 0 \quad \text{--- (2)}$$

$$0 - I_2 R + I_3 \left( 2R + \frac{1}{sC} \right) = 0 \quad \text{--- (3)}$$

$$\& V_f = I_3 R$$

→ Solving (1), (2) & (3) for  $I_3$

$$I_3 = \frac{V_o R^2 s^3 C^3}{1 + 5sRC + 6s^2 C^2 R^2 + s^3 C^3 R^3}$$

$$V_f = I_3 R = \frac{V_o R^3 s^3 C^3}{1 + 5sRC + 6s^2 C^2 R^2 + s^3 C^3 R^3}$$

$$\Rightarrow \frac{V_f}{V_o} = \frac{1}{1 + \frac{5}{sRC} + \frac{6}{s^2 C^2 R^2} + \frac{1}{s^3 C^3 R^3}}$$

→ Replacing  $s = j\omega$   $s^2 = -\omega^2$  &  $s^3 = -j\omega^3$

$$B = \frac{1}{1 + \frac{5}{j\omega RC} - \frac{6}{\omega^2 C^2 R^2} + \frac{1}{j\omega^3 C^3 R^3}}$$

$$= \frac{1}{(1 - 5\alpha^2) + j\alpha(6 - \alpha^2)}$$

where  $\alpha = \frac{1}{\omega RC}$

→ For  $A\beta = 1$ ,  $\beta$  should be real, so imaginary term must be zero

$$\alpha(6 - \alpha^2) = 0$$

$$\Rightarrow \alpha^2 = 6$$

$$\Rightarrow \alpha = \sqrt{6}$$

$$\Rightarrow \frac{1}{\omega RC} = \sqrt{6}$$

→ The freq. of oscillation  $f_0$  is  $f_0 = \frac{1}{2\pi RC\sqrt{6}}$

→ For  $\alpha^2 = 6$ ,  $\beta = -\frac{1}{29}$  (-ve sign indicates feedback produces 180° phase shift)


$$|\beta| = \frac{1}{29}$$

$$|A\beta| \geq 1$$

→ Therefore for sustained oscillations,  $|A| \geq 29$

$$R_f = 29R_1$$

Wein Bridge Oscillator

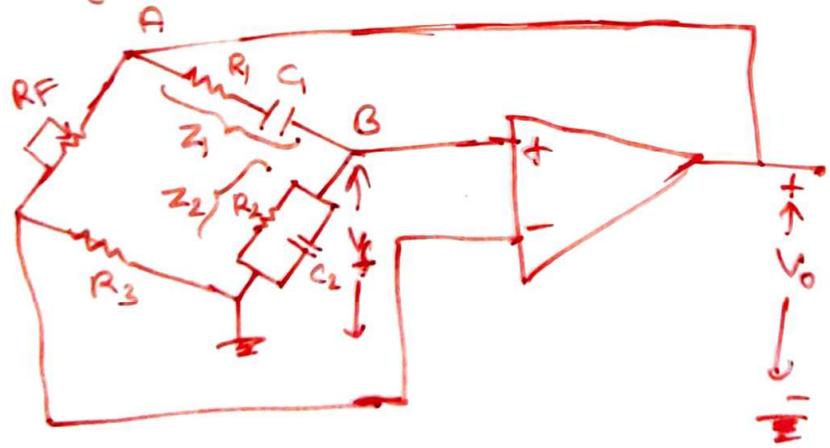


$$A = 1 + \frac{R_f}{R_3}$$

$$\beta = \frac{V_f}{V_0} = \frac{Z_2}{Z_1 + Z_2}$$

$$Z_1 = R_1 + \frac{1}{sC_1} = \frac{sCR_1 + 1}{sC_1}$$

$$Z_2 = \frac{R_2}{1 + sR_2C_2}$$

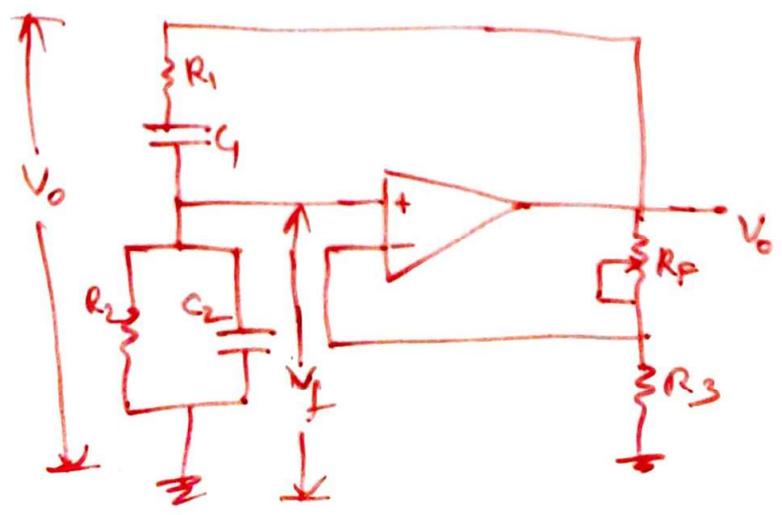

$$\beta = \frac{R_2 / (1 + sR_2C_2)}{\frac{1 + sR_1C_1}{sC_1} + \frac{R_2}{1 + sR_2C_2}} = \frac{sR_2C_1}{1 + s(R_1C_1 + R_2C_2 + R_2C_1) + s^2R_1R_2C_1C_2}$$

→ Put  $s = j\omega$

$$\beta = \frac{j\omega R_2 C_1}{1 + j\omega(R_1 C_1 + R_2 C_2 + R_2 C_1) - \omega^2 R_1 R_2 C_1 C_2}$$

→ For  $\beta$  to be a real quantity

$$1 - \omega^2 R_1 R_2 C_1 C_2 = 0$$

→ Freq. of oscillation

$$f_0 = \frac{1}{2\pi \sqrt{R_1 R_2 C_1 C_2}}$$

$$\& \beta = \frac{R_2 C_1}{R_1 C_1 + R_2 C_2 + R_2 C_1}$$

→ For  $R_1 = R_2 = R$  &  $C_1 = C_2 = C$

$$f_0 = \frac{1}{2\pi RC}$$

$$\& \beta = \frac{1}{3}$$

→ Since  $|A\beta| \geq 1$  for sustained oscillation

$$|A| \geq 3$$

→ Since  $A = 1 + \frac{R_F}{R_3}$

$$3 = 1 + \frac{R_F}{R_3} \Rightarrow R_F = 2R_3$$

... ..