
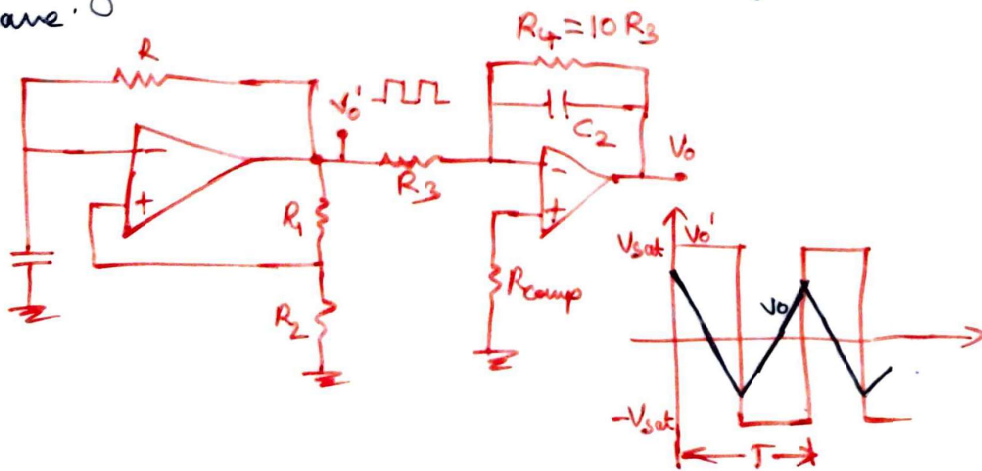


Triangular Wave Generator

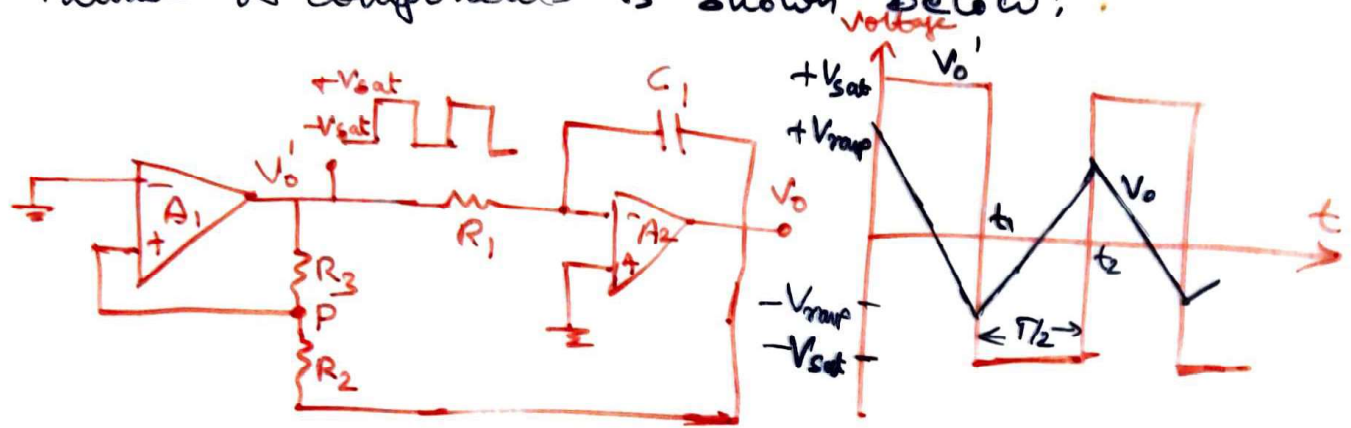→ A triangular wave can be obtained by integrating a square wave.



- The amplitude of triangular wave will decrease as freq. increases because reactance of C_2 in feedback \downarrow at high freq.'s.
- A resistance R_f is connected across C_2 to avoid the saturation problem at low freq.'s as in case of practical integrator.
- Another triangular wave generator using lesser number of components is shown below:



- It consists of a two level comparator followed by an integrator.
- Consider that op of comparator A_1 is at $+V_{sat}$, the op of integrator A_2 will be a -ve going ramp.
- At time $t=t_1$, when -ve going ramp attains a value of $-V_{ramp}$, effective voltage at point becomes slightly less than $0V$. This switches the op of A_1 from +ve saturation to -ve saturation level $-V_{sat}$.
- The effective voltage at point P during the time when op of A_1 is at $+V_{sat}$ level is given by

$$-V_{ramp} + \frac{R_2}{R_2 + R_3} [+V_{sat} - (-V_{ramp})]$$
- At $t=t_1$ the voltage at point P becomes equal to zero

$$\therefore -V_{ramp} = -\frac{R_2}{R_3} (+V_{sat})$$
- Similarly at $t=t_2$, when op of A_1 switches from $-V_{sat}$ to $+V_{sat}$

$$V_{ramp} = \frac{-R_2}{R_3} (-V_{sat}) = \frac{R_2}{R_3} (V_{sat})$$

∴ peak to peak amplitude of triangular wave

$$\text{is } V_o(\text{PP}) = +V_{\text{ramp}} - (-V_{\text{ramp}}) = 2 \frac{R_2}{R_3} V_{\text{sat}}$$

→ Op switches from $-V_{\text{ramp}}$ to $+V_{\text{ramp}}$ in half the time period $T/2$

$$V_o = -\frac{1}{RC} \int V_i dt$$

$$V_o(\text{PP}) = -\frac{1}{R_1 C_1} \int_0^{T/2} (-V_{\text{sat}}) dt = \frac{V_{\text{sat}}}{R_1 C_1} \left(\frac{T}{2}\right)$$



$$\Rightarrow T = 2 R_1 C_1 \frac{V_o(\text{PP})}{V_{\text{sat}}}$$

$$\therefore T = 4 \frac{R_1 C_1 R_2}{R_3}$$

→ Hence, freq. of oscillation f_o is

$$f_o = \frac{1}{T} = \frac{R_3}{4 R_1 C_1 R_2}$$

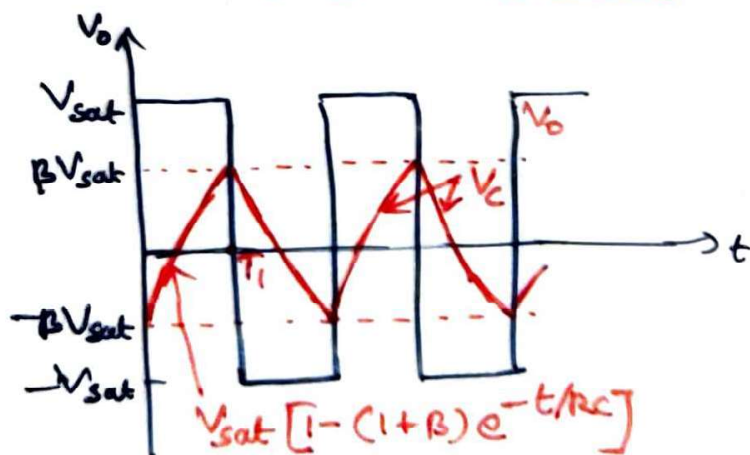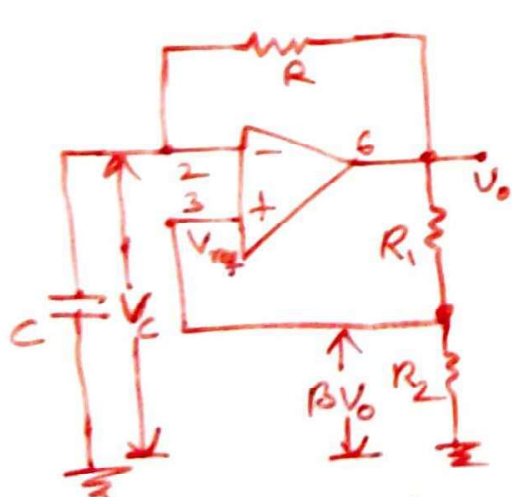Square Wave Generator (Astable Multivibrator)



→ Also called free running oscillator.

→ Principle of generation of square wave is to force an op-amp to operate in saturation region.

→ In astable multivibrator both states are quasi-stable.

→ Consider an instant of time when op is at $+V_{\text{sat}}$. The capacitor starts charging towards $+V_{\text{sat}}$ through resistance.

→ This continues as the charge on C rises, until it has exceeded $+BV_{sat}$, reference voltage

→ When the voltage at (-) i/p terminal becomes just greater than ref. voltage, the op is driven to $-V_{sat}$

→ At this instant, voltage on capacitor is $+BV_{sat}$. It begins to discharge through R toward $-V_{sat}$

→ Freq. is determined by time it takes for capacitor to change from $-BV_{sat}$ to $+BV_{sat}$ & vice versa

→ Voltage across the capacitor as a function of time is given by $V_c(t) = V_f + (V_i - V_f)e^{-t/RC}$

where final value, $V_f = +V_{sat}$

& initial value, $V_i = -BV_{sat}$

$$\therefore V_c(t) = V_{sat} + (-BV_{sat} - V_{sat})e^{-t/RC}$$

$$\Rightarrow V_c(t) = V_{sat} - V_{sat}(1+B)e^{-t/RC}$$

→ At $t = T_1$, voltage across capacitor reaches BV_{sat} & switching takes place

$$\therefore V_c(T_1) = BV_{sat} = V_{sat} - V_{sat}(1+B)e^{-T_1/RC}$$

$$\Rightarrow T_1 = RC \ln \frac{1+B}{1-B}$$

→ This gives only half of the period

→ Total time period, $T = 2T_1 = 2RC \ln \frac{1+B}{1-B}$

& op waveform is symmetrical

→ If $R_1 = R_2$, then $B = 0.5$ & $T = 2RC \ln 3$

→ For $R_1 = 1.16R_2$, $T = 2RC \Rightarrow f_0 = \frac{1}{2RC}$

Sawtooth Wave Generator

Voltage

$$f_0 = \frac{1}{2RC}$$