

Active Filters

→ A freq. selective electric circuit that passes electric signals of specified band of freq.'s & attenuates the signals of freq.'s outside the band is called an electric filter.

→ Filters are widely used in communication & signal processing

→ Filters can be built from (i) passive RLC components, (ii) crystals, or (iii) resistors, capacitors & op-amps (active filters)


→ Most commonly used filters are:

Low Pass Filter (LPF)


High Pass Filter (HPF)

Band Pass Filter (BPF)

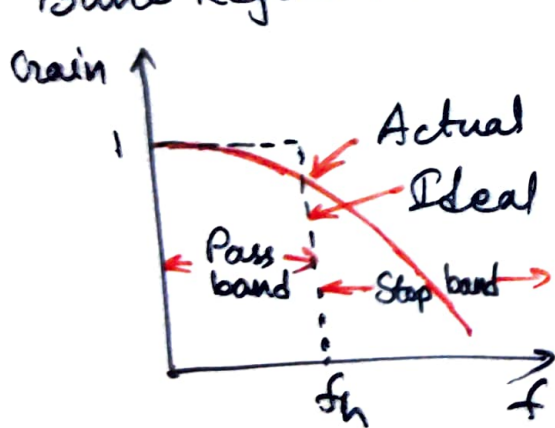
Band Reject Filter or Band Stop Filter (BSF)




Low pass Filter

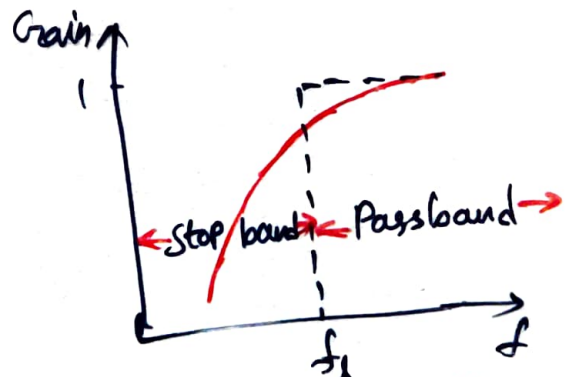

High pass Filter

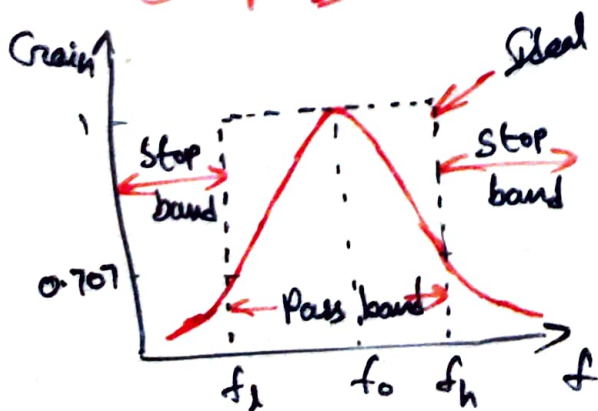

Band Pass Filter

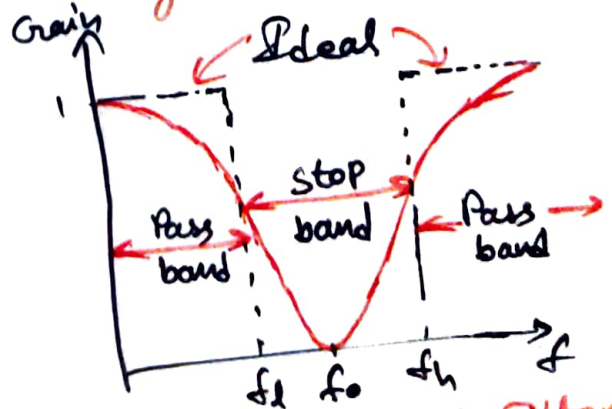


Band Reject Filter

→ Active filters are specified by voltage transfer function

$$H(s) = V_o(s) / V_i(s)$$

First Order Low Pass Filter

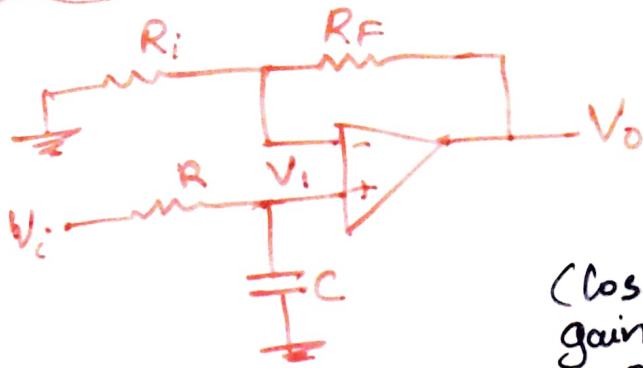

$$V_1(s) = \frac{1/sC}{R + 1/sC} V_i(s)$$

$$\frac{V_1(s)}{V_i(s)} = \frac{1}{RCs + 1}$$

(closed loop gain of op-amp)

$$A_0 = \frac{V_o(s)}{V_1(s)} = 1 + \frac{R_F}{R_i}$$

→ Overall transfer function

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{V_o(s)}{V_1(s)} \cdot \frac{V_1(s)}{V_i(s)}$$

$$= \frac{A_0}{RCs + 1}$$

$$H(s) = \frac{V_o(s)}{V_i(s)}$$

$$= \frac{A_0}{\frac{s}{\omega_h} + 1} = \frac{A_0 \omega_h}{s + \omega_h}$$

where $\omega_h = \frac{1}{RC}$

→ To determine freq. response put $s = j\omega$

$$H(j\omega) = \frac{A_0}{1 + j\omega RC} = \frac{A_0}{1 + j(f/f_h)} \quad \text{where } f_h = \frac{1}{2\pi RC}$$

$$\& f = \frac{\omega}{2\pi}$$

→ At very high freq, i.e. $f \gg f_h$

$$|H(j\omega)| \ll A_0 \approx 0$$

→ At very low freq, i.e. $f \ll f_h$

$$|H(j\omega)| \approx A_0$$

→ At $f = f_h$ $|H(j\omega)| = \frac{A_0}{\sqrt{2}} = 0.707 A_0$

