

PART-A*(Answer 05 questions. Each question carries 2 marks)***[5x2= 10]**

Q.No	Question	Marks	Bloom's Level
Q.1	a) List the advantages and disadvantages of full wave rectifier.	[2]	L1
	b) Define base width modulation.	[2]	L1
	c) Explain about biasing MOSFET.	[2]	L2
	d) How fast can the output of an op-amp change by 10V, if its slew rate is 1V/ μ s.	[2]	L2
	e) What are the advantages of active filters?	[2]	L1

END OF PART A**PART-B***(Answer 05 full questions. Each question carries 12 marks)*

Q.No	Question	Marks	Bloom's Level
Q.2(a)	Explain the V-I characteristics of Zener diode and also explain Zener breakdown.	[06]	L2
(b)	A sinusoidal voltage whose $V_m=26V$ is applied to half wave rectifier. The diode may be considered to be ideal and $R_L=1.2K\Omega$ is connected as load. Find out peak value of current, r.m.s value of current, dc value of current and ripple factor.	[06]	L3
OR			
Q.3(a)	The voltage across a Si diode at room temperature of 300K is 0.71V when 2.5mA current flows through it. If the voltage increases to 0.8V, estimate the new current.	[06]	L3
(b)	Illustrate the operation of negative clamper with neat sketch.	[06]	L2
OR			
Q.4(a)	Explain input and output characteristics of common base configuration of BJT.	[06]	L2
(b)	Compare the characteristics of CB, CE and CC configurations of transistors.	[06]	L4
OR			
Q.5(a)	Summarize in detail how BJT acts as an amplifier.	[06]	L2
(b)	Define stability parameters S , S_β and S_v and derive the expression for stability factor S .	[06]	L2

<i>Q.6(a)</i>	Explain the characteristics of depletion mode MOSFET.	[06]	L2
<i>(b)</i>	Explain the common drain configuration of MOSFET and derive for A_v , R_i and R_o .	[06]	L2
OR			
<i>Q.7(a)</i>	Explain the common gate configuration of MOSFET and derive for A_v , R_i and R_o .	[06]	L2
<i>(b)</i>	Derive expressions for voltage divider biasing in MOSFET.	[06]	L2
<i>Q.8(a)</i>	Compare Class A and Class B power amplifiers.	[06]	L4
<i>(b)</i>	Explain ideal characteristics of an Op-amp.	[06]	L2
OR			
<i>Q.9(a)</i>	Describe the operation of class A series fed amplifier and calculate efficiency.	[06]	L2
<i>(b)</i>	Discuss the factors input offset voltage, input bias and input offset currents.	[06]	L2
<i>Q.10(a)</i>	Derive the expression for RC phase shift oscillator using op-amp.	[06]	L2
<i>(b)</i>	Explain the circuit operation to generate square waveform with neat sketches using 741IC.	[06]	L2
OR			
<i>Q.11(a)</i>	Derive the equation for time period T in a monostable multivibrator using 741IC.	[06]	L2
<i>(b)</i>	Using functional diagram , explain how low and high regulation done in IC723 with figures.	[06]	L4