

**PART-A***(Answer 05 questions. Each question carries 2 marks)***[5x2= 10]**

<b>Q.No</b>	<b>Question</b>	<b>Marks</b>	<b>Bloom's Level</b>
<b>Q.1</b>	a) What is clamper and how it operates?	[2]	L-1
	b) Compare CE, CB and CC configurations.	[2]	L-2
	c) Why we call FET as a Voltage Controlled Device?	[2]	L-4
	d) List the non-ideal DC characteristics of an op-amp.	[2]	L-1
	e) Define CMRR.	[2]	L-1

***END OF PART A*****PART-B***(Answer 05 full questions. Each question carries 12 marks)****Marks***

<b>Q.2(a)</b>	Derive the expression for PN junction diode current.	[06]	L-2
<b>(b)</b>	A full wave rectifier is fed from a transformer having a center-tapped secondary winding. The RMS voltage from either end of secondary to center-tap is 30V. If the diode forward resistance is $2\Omega$ for a load of $1\text{ K}\Omega$ , calculate: (i) power delivered to load (ii) rectifier efficiency (iii) % regulation	[06]	L-5
	<b>OR</b>		
<b>Q.3(a)</b>	With a neat circuit diagram and necessary wave forms explain the operation of full wave rectifier. Also derive the efficiency for full wave rectifier.	[06]	L-2
<b>(b)</b>	With help of neat circuit diagrams and waveforms explain the operation of following shunt circuits: (i) positive clipper with reference voltage (ii) negative clipper	[06]	L-1

<i>Q.4(a)</i>	Explain the input and output characteristics of a transistor in CB configuration.	[06]	L-1
<i>(b)</i>	A CE amplifier is drawn by a voltage source of internal resistance $R_S = 800\Omega$ and load impedance $R_L = 1K\Omega$ . The h-parameters are $h_{ie}=1K\Omega$ , $h_{re} = 2 \times 10^{-4}$ , $h_{fe} = 50$ and $h_{oe} = 25 \mu A/V$ . Compute $A_I$ , $R_I$ , $A_V$ and $R_O$ .	[06]	L-5
<b>OR</b>			
<i>Q.5(a)</i>	Explain in detail how BJT acts as a switch.	[06]	L-4
<i>(b)</i>	Derive the operating point using AC and DC load lines.	[06]	L-3
<i>Q.6(a)</i>	Describe the construction and working principle of enhancement mode MOSFET and draw its characteristics.	[06]	L-1
<i>(b)</i>	Draw and explain the MOSFET small signal model. Also derive transconductance from this model.	[06]	L-2
<b>OR</b>			
<i>Q.7(a)</i>	Describe the operation of common drain MOSFET amplifier and derive the equation for $A_V$ , $R_i$ and $R_o$ .	[06]	L-2
<i>(b)</i>	Explain the constructional features of a P-channel MOSFET and its basic operation.	[06]	L-2
<i>Q.8(a)</i>	Draw the circuit diagram of complementary symmetry class B amplifier and explain its operation. Also find its conversion efficiency.	[06]	L-2
<i>(b)</i>	List and explain in detail ideal characteristics of an op-amp.	[06]	L-1
<b>OR</b>			
<i>Q.9(a)</i>	Show that the transformer coupled class A amplifier maximum efficiency is 50%.	[06]	L-4
<i>(b)</i>	Define slew rate. How fast can the output of an op-amp change by 10V, if its slew rate is $1V/\mu s$ ?	[06]	L-4
<i>Q.10(a)</i>	Explain and draw the output waveforms of the ideal integrator circuit when the input is (i) sine wave (ii) square wave (iii) step input.	[06]	L1
<i>(b)</i>	Construct a Schmitt trigger using op-amp and explain its operation.	[06]	L-6
<b>OR</b>			
<i>Q.11(a)</i>	Design a second order low pass Butterworth filter using op-amp.	[06]	L-6
<i>(b)</i>	Explain the operation of triangular waveform generator using op-amp.	[06]	L-3