

Difference-mode & Common-mode Gains

$$V_{cm} = \frac{V_1 + V_2}{2}$$

$$V_o = A_1 V_1 + A_2 V_2$$

where A_1 is the voltage amplification from i/p 1 to the o/p with i/p 2 grounded

A_2 is the voltage amplification from i/p 2 to the o/p with i/p 1 grounded.

→ Since $V_{cm} = (V_1 + V_2)/2$ & $V_d = (V_1 - V_2)$

$$V_1 = V_{cm} + \frac{1}{2} V_d$$

$$V_2 = V_{cm} - \frac{1}{2} V_d$$

→ So

$$V_o = A_{DM} V_d + A_{CM} V_{cm}$$

where $A_{DM} = \frac{1}{2} (A_1 - A_2)$

and $A_{CM} = A_1 + A_2$

A_{DM} → voltage gain for difference signal


A_{CM} → voltage gain for common-mode signal

Common-Mode Rejection Ratio

→ Relative sensitivity of an op-amp to a differential signal as compared to a common-mode signal is called common-mode rejection ratio

→ CMRR gives the figure of merit ρ for differential amplifiers

→ So CMRR is given by $\rho = \left| \frac{A_{DM}}{A_{CM}} \right|$

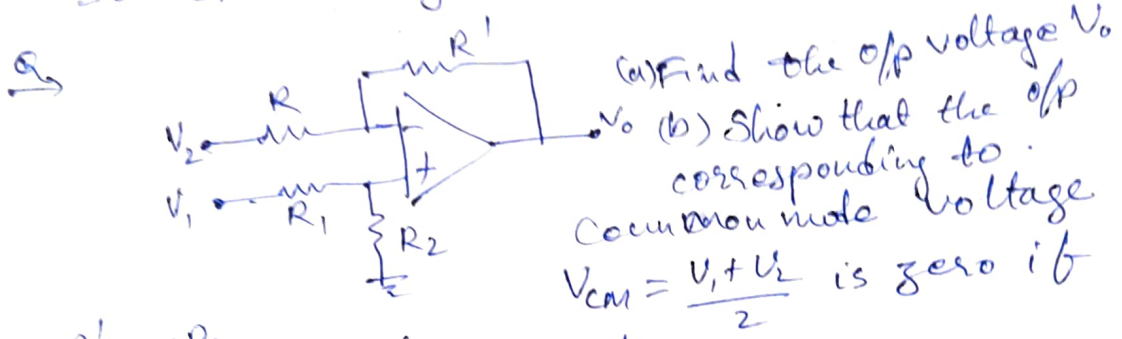

$\frac{R'}{R} = \frac{R_2}{R_1}$. Find V_o in this case

(c) Find CMRR of amplifier if $\frac{R'}{R} \neq \frac{R_2}{R_1}$

(a) $V_o = -\frac{R'}{R} V_2 + \left(\frac{R+R'}{R} \right) \left(\frac{R_2}{R_1+R_2} V_1 \right)$

(b) $V_{cm} = \frac{1}{2} (V_1 + V_2)$ $\left\{ \begin{array}{l} V_1 = V_{cm} + \frac{V_d}{2} \\ V_2 = V_{cm} - \frac{V_d}{2} \end{array} \right.$

$V_o = -\frac{R'}{R} \left(V_{cm} - \frac{V_d}{2} \right) + \left(\frac{R+R'}{R} \right) \left(\frac{R_2}{R_1+R_2} \right) \left(V_{cm} + \frac{V_d}{2} \right)$

$= V_{cm} \left[\left(\frac{R+R'}{R} \right) \left(\frac{R_2}{R_1+R_2} \right) - \frac{R'}{R} \right] + \frac{V_d}{2} \left[\frac{R'}{R} + \left(\frac{R+R'}{R} \right) \left(\frac{R_2}{R_1+R_2} \right) \right]$

If $\frac{R'}{R} = \frac{R_2}{R_1} \Rightarrow \frac{R'}{R} + 1 = \frac{R_2}{R_1} + 1$

$\Rightarrow \frac{R'+R}{R} = \frac{R_2+R_1}{R_1}$ then $V_{cm} = 0$

So $V_o = \frac{V_d}{2} \left[\frac{R'}{R} + \frac{R_2}{R_1} \right] = \left(\frac{R_2}{R_1} \right) V_d$

(c) $CMRR = \frac{A_{DM}}{A_{CM}}$

$A_{DM} = \frac{V_o}{V_d}$ by putting $V_{cm} = 0$

$= \frac{1}{2} \left[\frac{R'}{R} + \left(\frac{R+R'}{R} \right) \left(\frac{R_2}{R_1+R_2} \right) \right] = \frac{1}{2} \left[\frac{R'R_1 + 2R'R_2 + RR_2}{R(R_1+R_2)} \right]$

$$A_{cm} = v_o/v_{cm} \text{ by putting } v_d = 0$$

$$= \left[\left(\frac{R+R'}{R} \right) \left(\frac{R_2}{R_1+R_2} \right) - \frac{R'}{R} \right] = \left[\frac{R R_2 - R' R_1}{R(R_1+R_2)} \right]$$

$$CMRR = \frac{A_{DM}}{A_{cm}} = \frac{1}{2} \left[\frac{R' R_1 + 2 R R_2 + R R_2}{R R_2 - R' R_1} \right]$$

→ Determine the o/p voltage of a differential amplifier for the i/p voltages of $300\mu\text{V}$ & $240\mu\text{V}$. The differential gain of the amplifier is 5000 & the value of CMRR is i) 100 & ii) 10^5

i) $\text{CMRR} = 100$

$$V_d = V_1 - V_2 = 60\mu\text{V}$$

$$V_{\text{CM}} = \frac{V_1 + V_2}{2} = 270\mu\text{V}$$

$$CMRR = \frac{A_{DM}}{A_{CM}} \Rightarrow 100 = \frac{5000}{A_{CM}} \Rightarrow A_{CM} = 50$$

$$V_o = A_{DM} V_d + A_{CM} V_{CM}$$

$$\begin{aligned} \Rightarrow V_o &= 5000 \times 60 \mu + 50 \times 270 \mu \\ &= 313500 \mu V = 0.3135 V \end{aligned}$$

$$ii) CMRR = 10^5$$

$$10^5 = \frac{5000}{A_{CM}} \Rightarrow A_{CM} = 0.05$$

$$\begin{aligned} V_o &= 5000 \times 60 \mu + 0.05 \times 270 \mu \\ &= 300013.5 \mu V = 0.3 V \end{aligned}$$