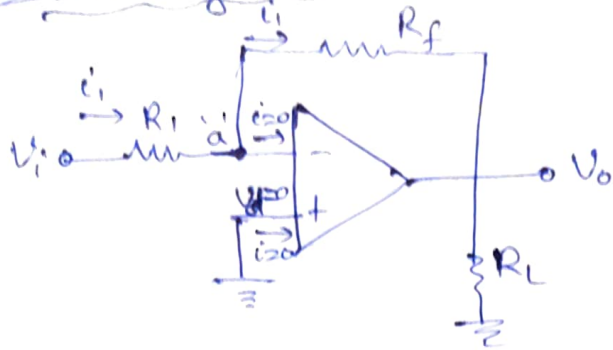


Inverting Amplifiers



→ for simplicity, assume an ideal op-amp

→ As $V_a = 0$, node 'a' is at ground potential & the current i_i through R_1 is

$$i_i = \frac{V_i}{R_1}$$

→ Since op-amp draws no current, all the current flowing through R_1 must flow through R_f

→ The o/p voltage

→ The ^{gain of} inverting amplifier (also referred as closed loop gain) is

$$V_o = -i_i R_f = -V_i \frac{R_f}{R_1}$$

$$A_{CL} = \frac{V_o}{V_i} = -\frac{R_f}{R_1}$$

→ The negative sign indicates a phase shift of 180° between V_i and V_o

→ Since inverting i/p terminal is at virtual ground, the effective i/p impedance is R_1

$$\frac{V_a - V_i}{R_1} + \frac{V_a - V_o}{R_f} = 0$$

$$-\frac{V_i}{R_1} + \frac{-V_o}{R_f} = 0$$

$$\Rightarrow \frac{V_o}{V_i} = A_{CL} = -\frac{R_f}{R_1}$$

→ If resistances R_1 and R_f are replaced by impedances!

Z_1 and Z_f respectively then the voltage gain, A_{CL} will be $A_{CL} = -\frac{Z_f}{Z_1}$

→ This expression for voltage gain ~~of -10~~ it will be used in op-amp applications, such as integrator, differentiator, etc.

Q Design an amplifier with a gain of -10 and i/p resistance equal to $10k\Omega$

$$R_1 = 10k\Omega$$

$$A_{CL} = -10$$

$$R_f = -A_{CL} R_1 = -(-10) \times 10k = 100k\Omega$$

Q → In an inverting op-amp circuit, $R_1 = 10\text{ k}\Omega$, $R_f = 100\text{ k}\Omega$, $V_i = 1\text{ V}$. A load of $25\text{ k}\Omega$ is connected to o/p terminal. Calculate (i) i_i , (ii) V_o , (iii) i_L and (iv) total current i_o into the o/p pin

$$(a) \quad i_i = \frac{V_i}{R_1} = \frac{1\text{ V}}{10\text{ k}\Omega} = 0.1\text{ mA}$$

$$(b) \quad V_o = -\frac{R_f}{R_1} V_i = -\frac{100\text{ k}\Omega}{10\text{ k}\Omega} \times 1 = -10\text{ V}$$

$$(c) \quad i_L = \frac{V_o}{R_L} = \frac{10\text{ V}}{25\text{ k}\Omega} = 0.4\text{ mA} \quad (\uparrow)$$

$$(d) \quad i_o = i_i + i_L = 0.5\text{ mA} \quad (\leftarrow)$$