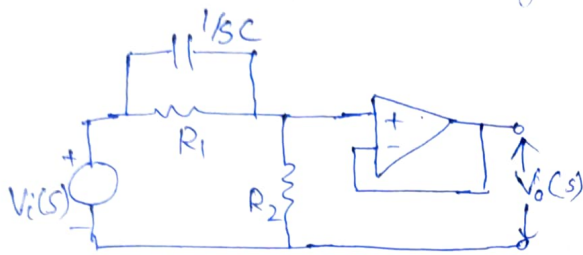


# Lead / Lag Compensator using Op-Amp

## Op-Amp Lag Compensator

- A lag compensator adds a pole to the system & is used to improve the steady state response of the system.
- A lag compensator provides phase lag (negative phase) in the freq. response of system.



Op-Amp Lead Compensator


$$V_o(s) = V_i(s) \cdot \frac{R_2}{R_2 + R_1 + \frac{1}{sC}}$$

$$\frac{V_o(s)}{V_i(s)} = \frac{R_2 (1 + sCR_1)}{R_2 (1 + sCR_1) + R_1}$$

- Hence the phase added to the system is

$$\tan^{-1}(\omega CR_1) - \tan^{-1}\left(\omega CR_1 \frac{R_2}{R_1 + R_2}\right)$$

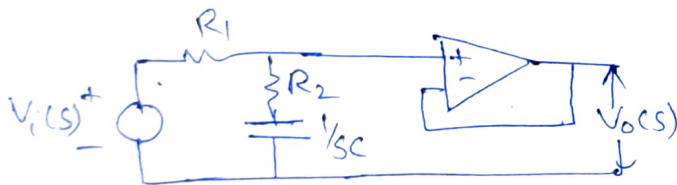- Since  $R_1 > \frac{R_1 R_2}{R_1 + R_2}$ , phase added is positive (phase lead)



Op-Amp Lag Compensator

$$V_o(s) = V_i(s) \cdot \frac{R_2 + \frac{1}{sC}}{R_1 + R_2 + \frac{1}{sC}}$$

$$\frac{V_o(s)}{V_i(s)} = \frac{sCR_2 + 1}{sC(R_1 + R_2) + 1}$$

- Hence phase added to the system is

$$\tan^{-1}(\omega CR_2) - \tan^{-1}(\omega C(R_1 + R_2))$$

- Since  $R_2 < R_1 + R_2$ , phase added is negative (phase lag)

## Op-Amp Lead Compensator

- A Lead compensator adds a zero to the system & is used to improve transient response of the system.
- A Lead compensator provides Phase Lead (positive phase) in the freq. response of the system.