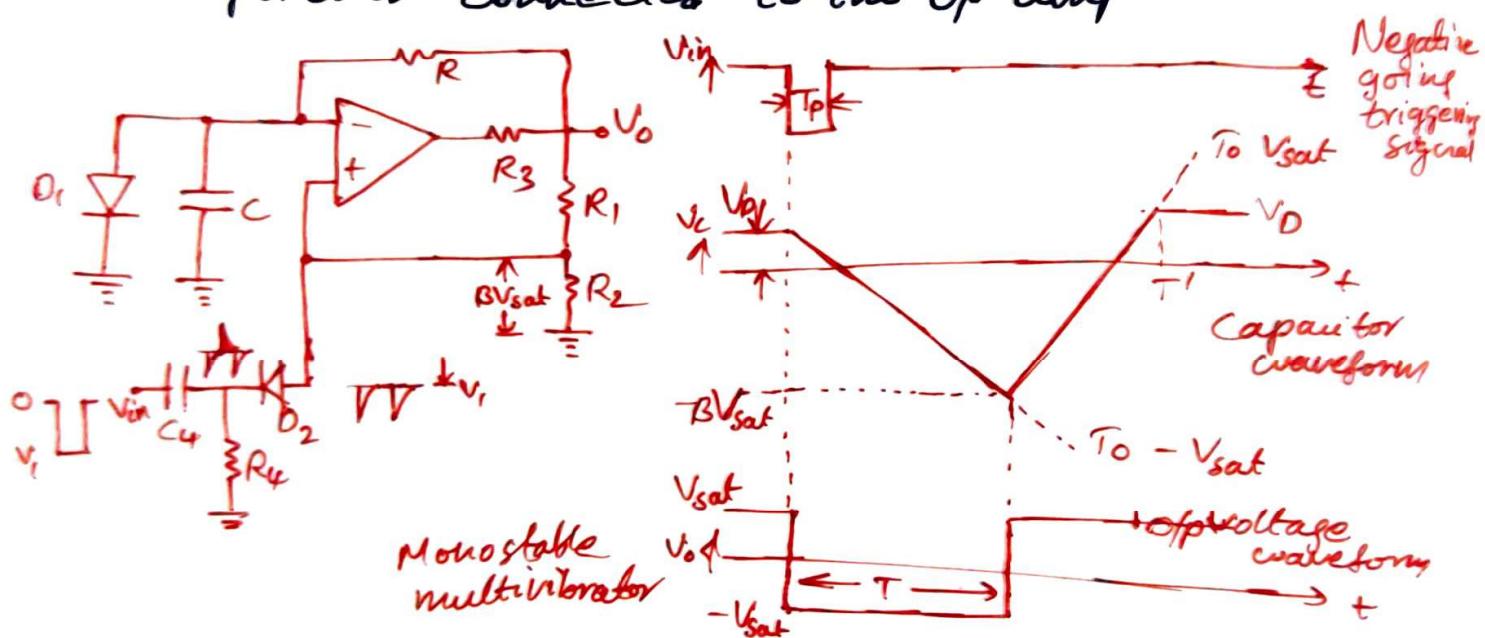


## Monostable Multivibrator

- It has one stable state & the other is quasi stable state
- The circuit is useful for generating single op pulse of adjustable time duration in response to a triggering signal.
- The width of op pulse depends only on external components connected to the op-amp.



- Let us assume that in the stable state the op  $V_o$  is at  $+V_{sat}$
- The diode  $D_1$  conducts &  $V_c$  the voltage across the capacitor  $C$  gets clamped to  $0.7V$ .
- Now, if a negative trigger of magnitude  $V_t$  is applied to + ip terminal so that the effective signal at this terminal is less than  $0.7V$  i.e.,  $[BV_{sat} + (-V_t)] < 0.7V$
- So the op of the op-amp will switch from  $+V_{sat}$  to  $-V_{sat}$ .
- Now diode -get reverse biased & the capacitor starts discharging exponentially to  $-V_{sat}$  through the resistance  $R$ .

- The voltage at the + op terminal is now  $-\beta V_{sat}$
- When the capacitor voltage  $V_c$  becomes just more negative than  $-\beta V_{sat}$ , the op of the op-amp switches back to  $+V_{sat}$ .

$$V_c = V_f + (V_i - V_f) e^{-t/RC}$$

- For the ckt  $V_f = -V_{sat}$  &  $V_i = V_0$  (diode forward voltage)

$$V_c = -V_{sat} + (V_0 + V_{sat}) e^{-t/RC}$$

- At  $t = T$   $V_c = -\beta V_{sat}$

$$\therefore -\beta V_{sat} = -V_{sat} + (V_0 + V_{sat}) e^{-T/RC}$$

- After simplification, pulse width  $T$  is obtained as

$$T = RC \ln \left( \frac{1 + V_0/V_{sat}}{1 - \beta} \right)$$

where  $\beta = R_2/R_1 + R_2$


- If  $V_{sat} \gg V_0$  &  $R_1 = R_2$  so that  $\beta = 0.5$ , then

$$T = 0.69 RC$$


- For monostable operation, the trigger pulse width  $T_p$  should be much less than  $T$ , the pulse width of the monostable multivibrator.
- The diode  $D_2$  is used to avoid malfunctioning by blocking the positive noise spikes that may be present at the differentiated trigger op.

### Regenerative Comparator (Schmitt Trigger)

- Regen

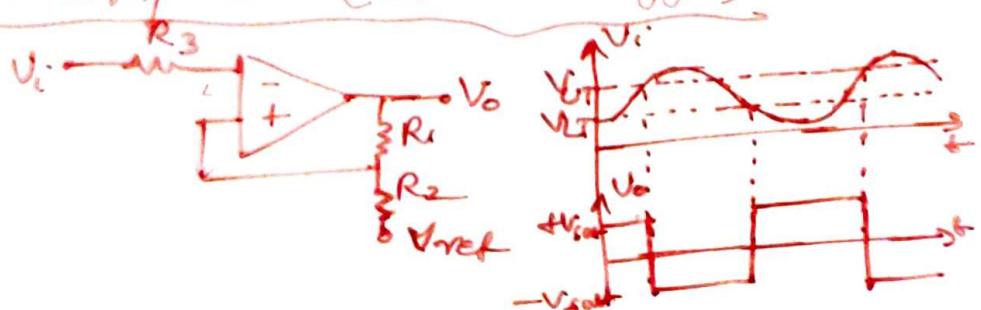

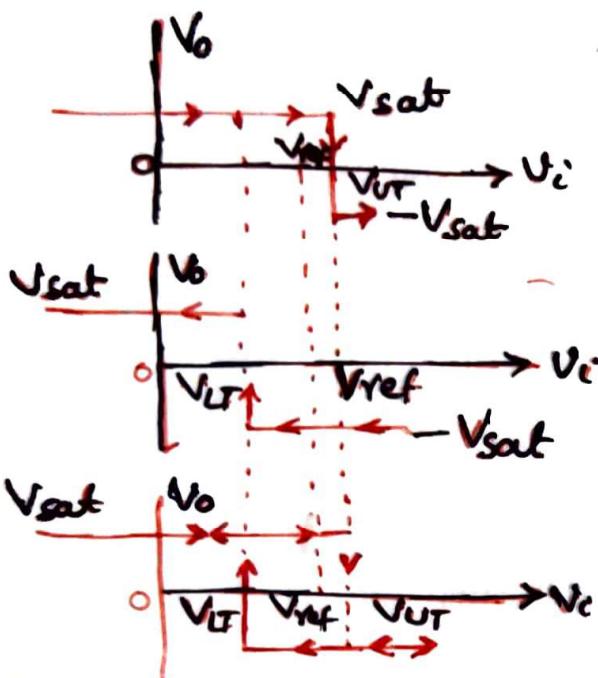- The rip voltage  $V_i$  triggers the o/p  $V_o$  every time it exceeds certain voltage levels.
- These voltage levels are called upper threshold voltage ( $V_{UT}$ ) & lower threshold voltage ( $V_{LT}$ )



- The hysteresis width is the difference between these two threshold voltages i.e.  $V_{UT} - V_{LT}$
- For  $V_o = +V_{sat}$ , the voltage at +i/p terminal is

$$V_{UT} = \frac{V_{ref} R_1}{R_1 + R_2} + \frac{R_2 V_{sat}}{R_1 + R_2}$$

This is called upper threshold voltage  $V_{UT}$

- As long as  $V_i$  is less than  $V_{UT}$ , the o/p  $V_o$  remains const at  $+V_{sat}$
- When  $V_i$  is just greater than  $V_{UT}$ , the o/p regeneratively switches to  $-V_{sat}$  & remains at this level as long as  $V_i > V_{LT}$
- For  $V_o = -V_{sat}$ , the voltage at +i/p terminal is

$$V_{LT} = \frac{V_{ref} R_1}{R_1 + R_2} - \frac{R_2 V_{sat}}{R_1 + R_2}$$

This voltage is called lower threshold voltage  $V_{LT}$

- The i/p voltage  $V_i$  must become lesser than  $V_{LT}$  in order to cause  $V_o$  to switch from  $-V_{sat}$  to  $+V_{sat}$ .
- Note that  $V_{LT} < V_{UT}$

- Hysteresis width,  $V_H = V_{UT} - V_{LT} = \frac{2 R_2 V_{sat}}{R_1 + R_2}$

Because of the hysteresis, the o/p triggers at a higher voltage for increasing signals than for decreasing ones