

Binary Adder-Subtractor

Half Adder

→ The most basic arithmetic operation is the addition of two binary digits.

- This simple addition consists of four possible elementary operations: $0+0=0$, $0+1=1$, $1+0=1$, and $1+1=10$.
- The first three operations produce a sum of one digit, but when both augend and addend bits are equal to 1, the binary sum (~~of one~~) consists of two digits.
- The higher significant bit of this result is called a carry.
- A combinational circuit that performs the addition of two bits is called a half-adder.
- One that performs the addition of three bits (two significant bits and a previous carry) is a full adder.
- A binary adder-subtractor is a combinational circuit that performs the arithmetic operations of addition and subtraction with binary numbers.
- We will develop this circuit by means of a hierarchical design.
- The half-adder design is carried out first, from which we develop the full adder.
- Connecting n full adders in cascade produces a binary adder for two n -bit numbers.
- The subtraction circuit is included in a complementary circuit.

Half Adder



- This circuit needs two binary inputs and two binary outputs.
- The input variables designate the augend and addend bits; the output variables produce the sum and carry.
- We assign symbols x and y to the two inputs and s (for sum) and c (for carry) to the outputs.

x	y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0



$$S = x'y + xy'$$


$$C = xy$$

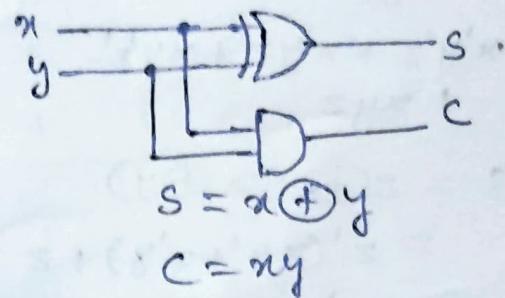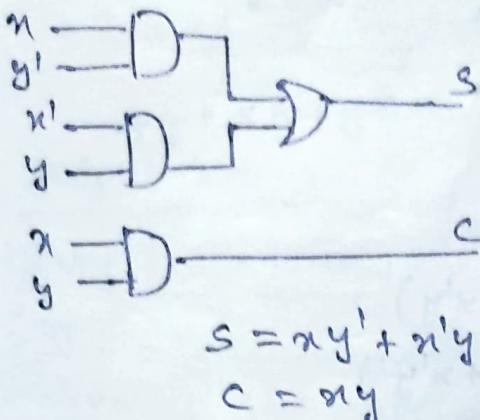

Full Adder

- Addition of n-bit binary numbers requires the use of a full adder, and the process of addition proceeds on a bit-by-bit basis, right to left, beginning with the least significant bit.
- After the least significant bit, addition at each position adds not only the respective bits of the words, but also consider a possible carry bit from addition at the previous position.
- A full adder is a combinational circuit that forms the arithmetic sum of three bits.
- It consists of three inputs and two outputs
- Two of the input variables, denoted by x and y , represent the two significant bits to be added. The third input, z represents the carry from the previous lower significant position.
- The two outputs are designated by the symbols s for sum and c for carry.

x	y	z	c	s
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

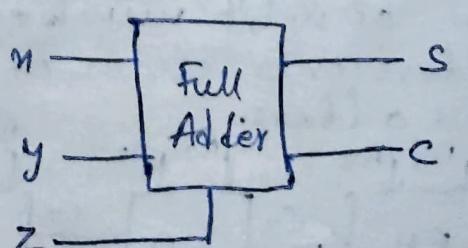

$x \backslash yz$	00	01	11	10
0	m_0	m_1	m_3	m_2
1	m_6	m_5	m_7	m_4
$x \backslash z$	m_0	m_1	m_3	m_2

$x \backslash yz$	00	01	11	10
0	m_0	m_1	m_3	m_2
1	m_6	m_5	m_7	m_4
$x \backslash z$	m_0	m_1	m_3	m_2

$$S = x'y'z + x'y'z' + xy'z' \\ + xyz$$




$$S = z \oplus (x \oplus y)$$

$$= z'(xy' + x'y) + z(xy' + x'y)'$$

$$= z'(xy' + x'y) + z(xy + x'y')$$


$$= xy'z' + x'y'z' + xyz + x'y'z$$
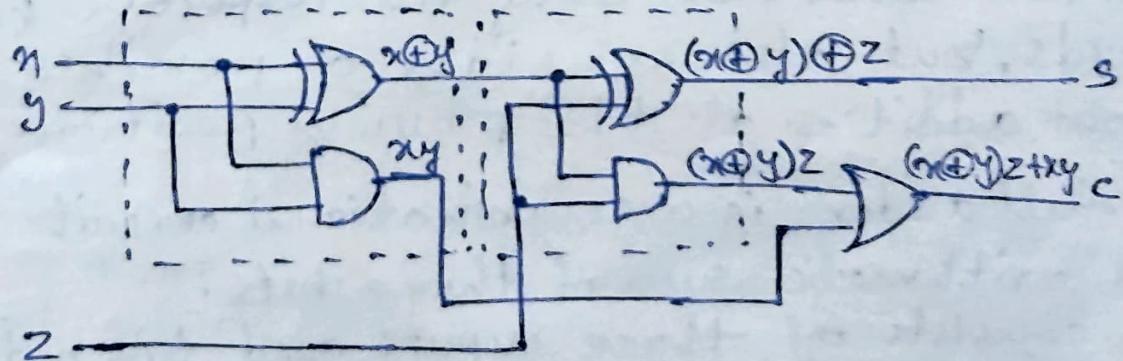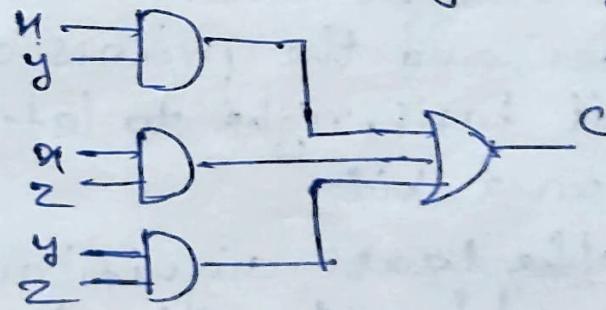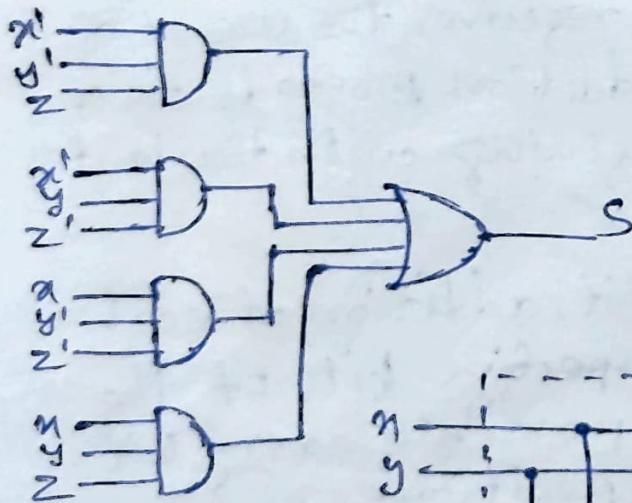
$$C = z(xy' + x'y) + xy = xy'z + x'y'z + xy$$



Binary Adder

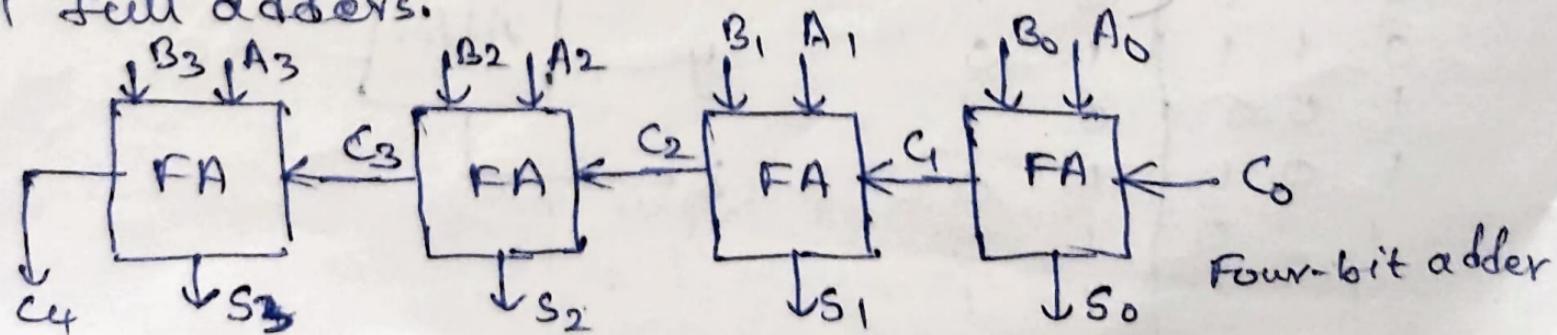- A binary adder is a digital circuit that produces the arithmetic sum of two binary numbers.
- It can be constructed with full adders connected in cascade, with the output carry from each full adder connected to the input carry of the next full adder in the chain.
- Addition of n-bit numbers requires a chain of n full adders or a chain of one-half adder and $n-1$ full adders.



Subscript i: 3 2 1 0

Input carry 0 1 1 0 c_i

Augend 1 0 1 1 A_i

Addend 0 0 1 1 B_i

sum 1 1 1 0 s_i

Output Carry 0 0 1 1 c_{i+1}
