

0 1

* Bcd Adder:

Combinational ckt which adds two decimal digits in BCD form, together with an i/p carry from a previous stage

Design 4-bit Bcd adder

Step 1: No. of i/ps = 2 decimal digits

or 9 bits
- 4 bits each from 2 decimal nos.
- 1 bit from prev carry

No. of o/ps = 4 S_8, S_4, S_2, S_1

step 2: Truth table

Each ^{digit} ~~digit~~ does not exceed 9, the o/p sum cannot be greater than $9+9+1=19$
 ↳ i/p carry

15/2/20
 62/ 64/ 67/ 69/ 70/ 71/ 72/ 76/ 81/ 83/ 87/ 88/ 95/ 99/ A0/
 A2/ A3/ A6/ B0/ B2/ C0/ LE-9
 17-237/ 17-84
 ↓
 gah?

Case (i): Total is less than or equal to 9

eg:

$$\begin{array}{r} 1 \rightarrow 0001 \\ +5 \rightarrow 0101 \\ \hline 6 \quad 0110 \end{array}$$

Up to 9 → Both BCD ~~addition~~ & Binary are going to be same

Case (ii): Total > 9

Ex:

$$\begin{array}{r} 5 \quad 0101 \\ 6 \quad 0110 \\ \hline 11 \quad 1011 \end{array}$$

BCD

$$\begin{array}{r} 0101 \\ 0110 \\ \hline 1011 \\ + 0110 \\ \hline 10001 \end{array}$$

001 | 0001
 ↳ 1 1

If value is ≥ 9 i.e; 1001 \Rightarrow add 0110⁽⁶⁾ to that value. (5)



Binary Sum					BCD Sum					Decimal
K	Z ₈	Z ₄	Z ₂	Z ₁	C	S ₈	S ₄	S ₂	S ₁	
0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	2
0	0	0	1	1	0	0	0	1	1	3
0	0	1	0	0	0	0	1	0	0	4
0	0	1	0	1	0	0	1	0	1	5
0	0	1	1	0	0	0	1	1	0	6
0	0	1	1	1	0	0	1	1	1	7
0	1	0	0	0	0	1	0	0	0	8
0	1	0	0	1	0	1	0	0	1	9
0	1	0	1	0	1	0	0	0	0	10
0	1	0	1	1	1	0	0	0	1	11
0	1	1	0	0	1	0	0	1	0	12
0	1	1	0	1	1	0	0	1	1	13
0	1	1	1	0	1	0	1	0	0	14
0	1	1	1	1	1	0	1	0	1	15
1	0	0	0	0	1	0	1	1	0	16
1	0	0	0	0	1	0	1	1	1	17
1	0	0	0	1	1	0	1	0	0	18
1	0	0	1	1	1	0	0	0	1	19

K Map for c

5-Variable K-Map

K=0

K=1

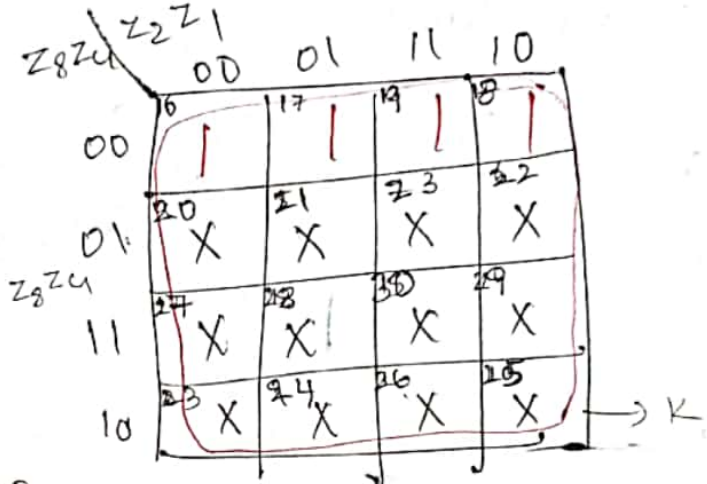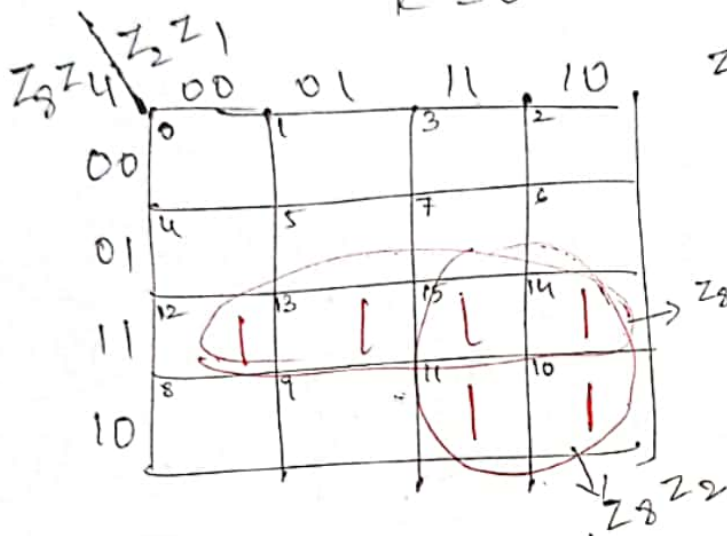

From 20 to 30 → don't care conditions.

$$C = K + Z_8 Z_4 + Z_8 Z_2$$

Step 4:

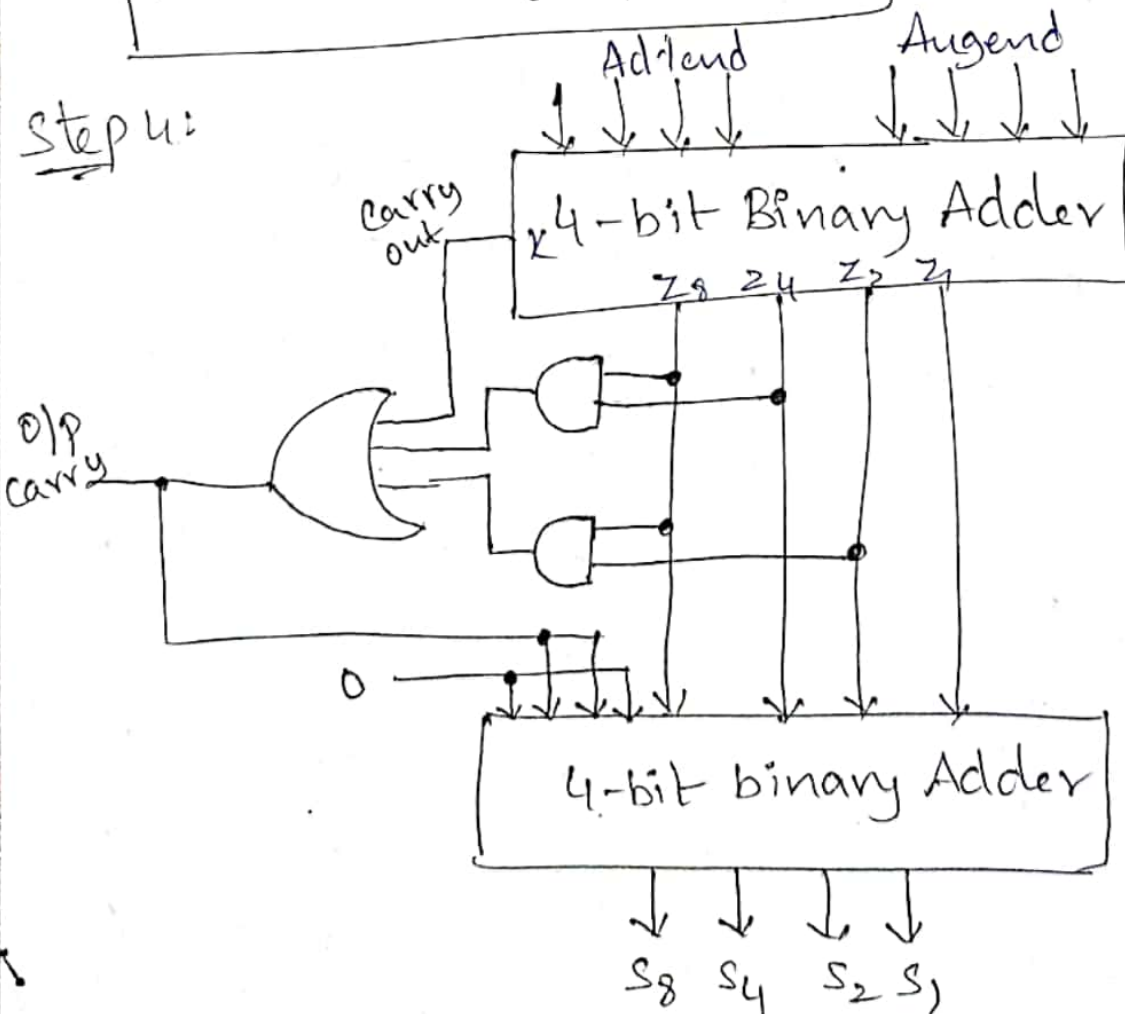


Fig: Block diagram of a BCD adder.