 


| Subscript $i$ : | 3 | 2 | 1 | 0 |           |
|-----------------|---|---|---|---|-----------|
| Input carry     | 0 | 1 | 1 | 0 | $C_i$     |
| Augend          | 1 | 0 | 1 | 1 | $A_i$     |
| Addend          | 0 | 0 | 1 | 1 | $B_i$     |
| sum             | 1 | 1 | 1 | 0 | $S_i$     |
| Output Carry    | 0 | 0 | 1 | 1 | $C_{i+1}$ |

### Carry Propagation

- In any combinational circuit, the signal must propagate through the gates before the correct output is available in the output terminals.
- The total propagation time is equal to the propagation delay of a typical gate, times the number of gate levels in the circuit.
- The longest propagation delay time in adder is the time it takes the carry to propagate through the full adders.
- Since each bit of the sum output depends on the value of the input carry, the value of  $S_i$  at any given stage in the adder will be in its steady-state final value only after the input carry to that stage has been propagated.
- The input and output variables use the subscript  $i$  to denote a typical stage of the adder.



- The signals at  $P_i$  and  $G_i$  settle to their steady-state values after they propagate through their respective gates.
- These two signals are common to all half adders and depend on only the input augend and addend bits.
- The signal from the input carry  $C_i$  to the output carry  $C_{i+1}$  propagates through an AND gate and an OR gate, which constitute two gate levels.

- For an n-bit adder, there are 2n gate levels for the carry to propagate from input to output.
- The most widely used technique for reducing the carry propagation time in a parallel adder employs the principle of carry lookahead logic.

$$P_i = A_i \oplus B_i$$

$$G_i = A_i \cdot B_i$$

$$S_i = P_i \oplus C_i$$

$$C_{i+1} = G_i + P_i \cdot C_i$$


- $G_i$  is called a carry generate, and it produces a carry of 1 when both  $A_i$  and  $B_i$  are 1, regardless of the input carry  $C_i$ .
- $P_i$  is called a carry propagate, because it determines whether a carry into stage  $i$  will propagate into stage  $i+1$ .

$$C_0 = \text{input carry}$$


$$C_1 = G_0 + P_0 C_0$$

$$C_2 = G_1 + P_1 C_1 = G_1 + P_1 (G_0 + P_0 C_0) = G_1 + P_1 G_0 + P_1 P_0 C_0$$
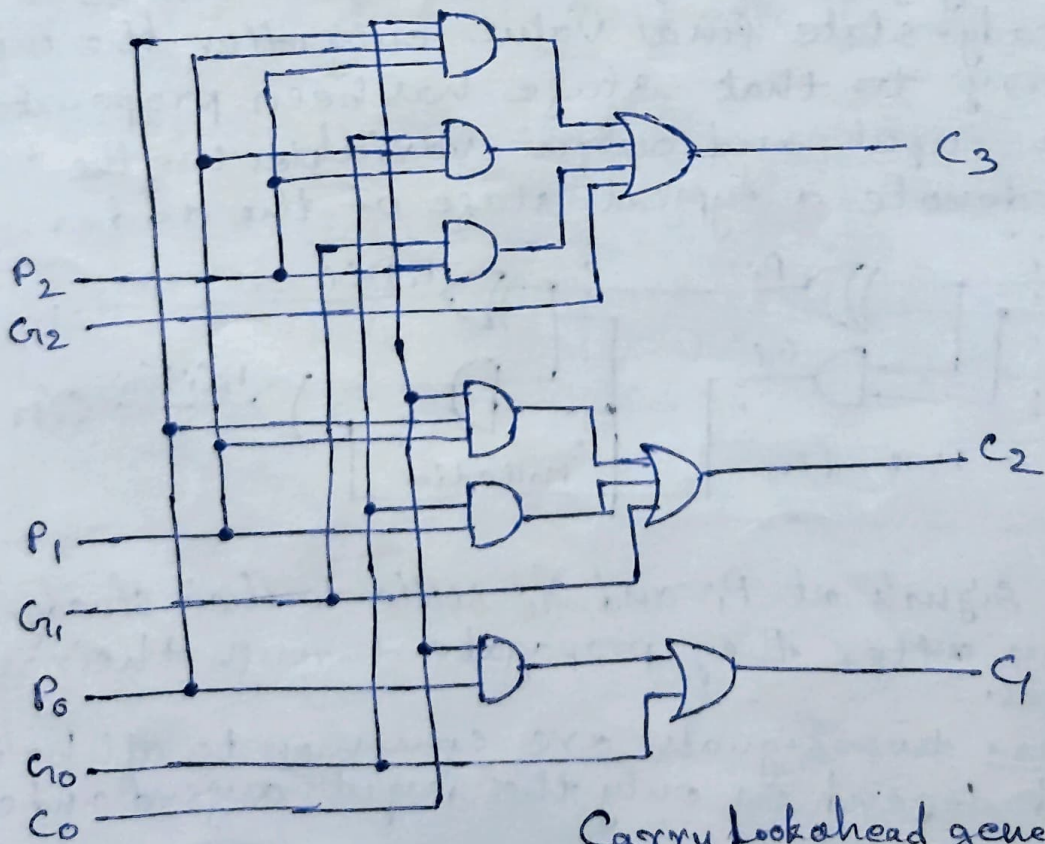
$$C_3 = G_2 + P_2 C_2 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$$



Carry Lookahead generator

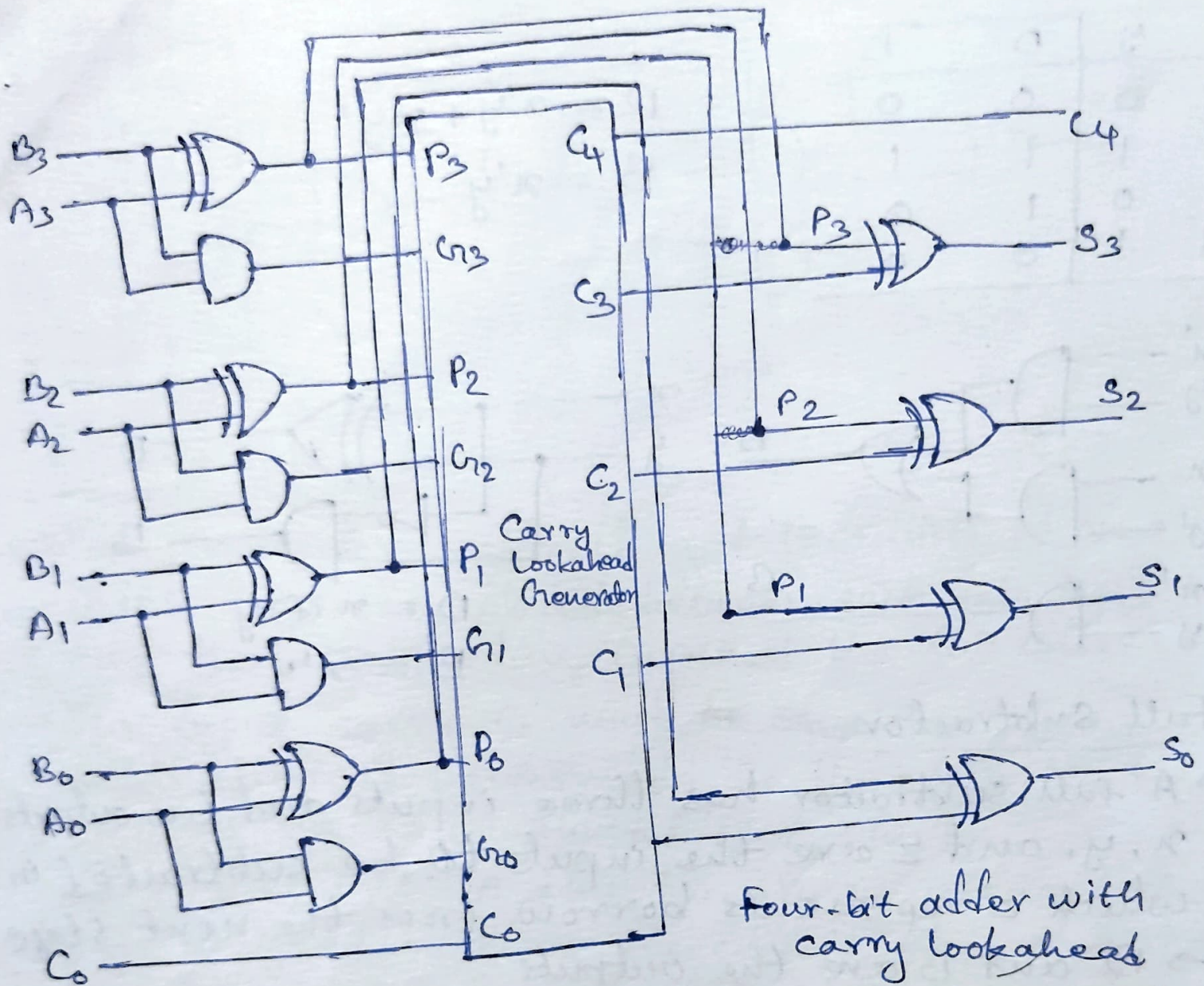

- Each sum output requires two exclusive-OR gates.
- The output of the first exclusive-OR gate generates the  $P_i$  variable, and the AND gate generates the  $G_i$  variable.
- The carries are propagated through the carry lookahead generator and applied as inputs to the second exclusive-OR gate.
- All output carries are generated after a delay through two levels of gates. Thus, outputs have equal propagation delay times.