

4.16.1 Design of a 4-bit Binary-to-Gray Code Converter

The input to the 4-bit binary-to-Gray code converter circuit is a 4-bit binary and the output is a 4-bit Gray code. There are 16 possible combinations of 4-bit binary input and all of them are valid. Hence no don't cares. The 4-bit binary and the corresponding Gray code are shown in the conversion table (Figure 4.32a). From the conversion table, we observe that the expressions for the outputs G_4 , G_3 , G_2 , and G_1 are as follows:

$$G_4 = \Sigma m(8, 9, 10, 11, 12, 13, 14, 15)$$

$$G_3 = \Sigma m(4, 5, 6, 7, 8, 9, 10, 11)$$

$$G_2 = \Sigma m(2, 3, 4, 5, 10, 11, 12, 13)$$

$$G_1 = \Sigma m(1, 2, 5, 6, 9, 10, 13, 14)$$

The K-maps for G_4 , G_3 , G_2 , and G_1 and their minimization are shown in Figure 4.32b. The minimal expressions for the outputs obtained from the K-map are:

$$G_4 = B_4$$

$$G_3 = \bar{B}_4 B_3 + B_4 \bar{B}_3 = B_4 \oplus B_3$$


$$G_2 = \bar{B}_3 B_2 + B_3 \bar{B}_2 = B_3 \oplus B_2$$

$$G_1 = \bar{B}_2 B_1 + B_2 \bar{B}_1 = B_2 \oplus B_1$$

So, the conversion can be achieved by using three X-OR gates as shown in the logic diagram in Figure 4.32c.

4-bit binary				4-bit Gray			
B_4	B_3	B_2	B_1	G_4	G_3	G_2	G_1
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	0
0	1	0	1	0	1	1	1
0	1	1	0	0	1	0	1
0	1	1	1	0	1	0	0
1	0	0	0	1	1	0	0
1	0	0	1	1	1	0	1
1	0	1	0	1	1	1	1
1	0	1	1	1	1	1	0
1	1	0	0	1	0	1	0
1	1	0	1	1	0	1	1
1	1	1	0	1	0	0	1
1	1	1	1	1	0	0	0

(a) Conversion table

 

(c) Logic diagram

Figure 4.32 4-bit binary-to-Gray code converter (Contd.)

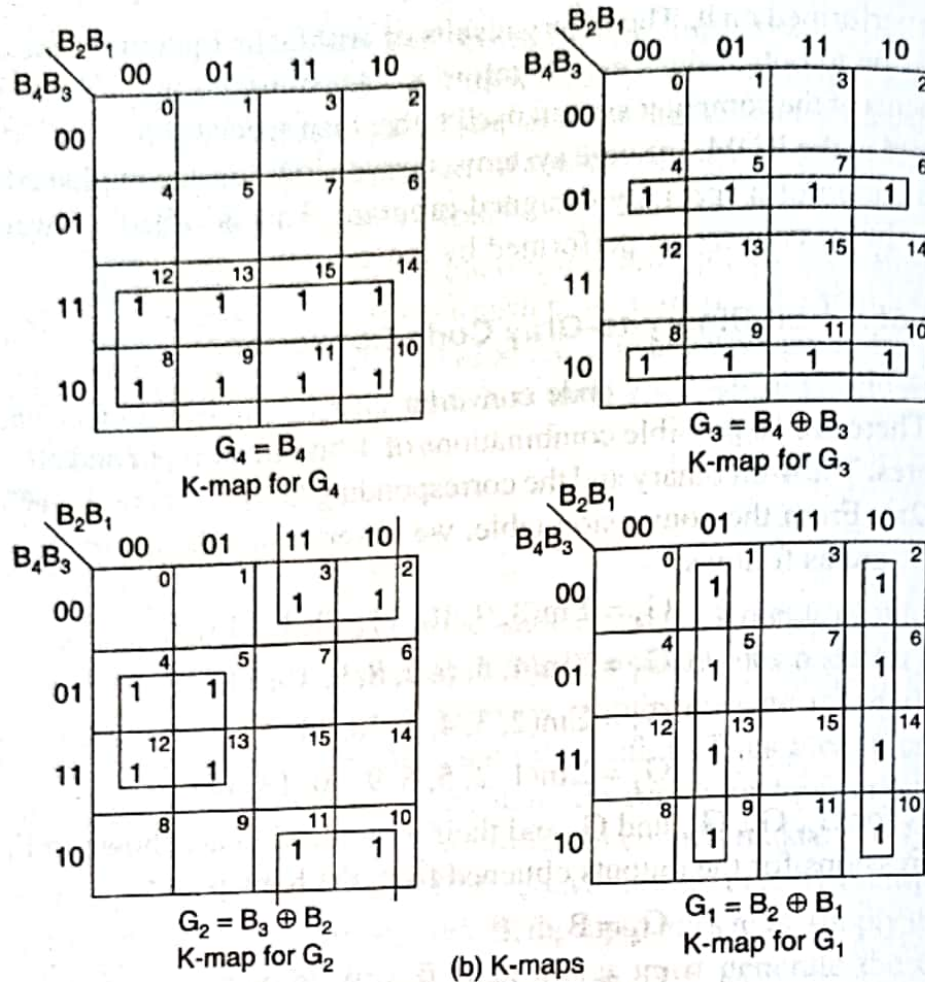


Figure 4.32 4-bit binary-to-Gray code converter.

4.16.2 Design of a 4-bit Gray-to-Binary Code Converter

The input to the 4-bit Gray-to-binary code converter circuit is a 4-bit Gray code and the output is a 4-bit binary. There are 16 possible combinations of 4-bit Gray input and all of them are valid. Hence no don't cares. The 4-bit input Gray code and the corresponding output binary numbers are shown in the conversion table of Figure 4.33a. From the conversion table we observe that the expressions for the outputs B_4 , B_3 , B_2 and B_1 are:

$$B_4 = \sum m(12, 13, 15, 14, 10, 11, 9, 8) = \sum m(8, 9, 10, 11, 12, 13, 14, 15)$$

$$B_3 = \sum m(6, 7, 5, 4, 10, 11, 9, 8) = \sum m(4, 5, 6, 7, 8, 9, 10, 11)$$

$$B_2 = \sum m(3, 2, 5, 4, 15, 14, 9, 8) = \sum m(2, 3, 4, 5, 8, 9, 14, 15)$$

$$B_1 = \sum m(1, 2, 7, 4, 13, 14, 11, 8) = \sum m(1, 2, 4, 7, 8, 11, 13, 14)$$

Drawing the K-maps for B_4 , B_3 , B_2 and B_1 in terms of G_4 , G_3 , G_2 , and G_1 as shown in Figure 4.33b and simplifying them, the minimal expressions for the outputs are as follows:

$$B_4 = G_4$$

$$B_3 = \bar{G}_4 G_3 + G_4 \bar{G}_3 = G_4 \oplus G_3$$

$$B_2 = \bar{G}_4 G_3 \bar{G}_2 + \bar{G}_4 \bar{G}_3 G_2 + G_4 \bar{G}_3 \bar{G}_2 + G_4 G_3 G_2$$

$$= \bar{G}_4 (G_3 \oplus G_2) + G_4 (G_3 \oplus G_2) = G_4 \oplus G_3 \oplus G_2 = B_3 \oplus G_2$$


$$B_1 = \bar{G}_4 \bar{G}_3 \bar{G}_2 G_1 + \bar{G}_4 \bar{G}_3 G_2 \bar{G}_1 + \bar{G}_4 G_3 G_2 G_1 + \bar{G}_4 G_3 \bar{G}_2 \bar{G}_1 + G_4 G_3 \bar{G}_2 G_1 + G_4 G_3 G_2 \bar{G}_1 + G_4 \bar{G}_3 G_2 G_1 + G_4 \bar{G}_3 \bar{G}_2 \bar{G}_1$$

$$\begin{aligned}
 &= \bar{G}_4 \bar{G}_3 (G_2 \oplus G_1) + G_4 G_3 (G_2 \oplus G_1) + \bar{G}_4 G_3 (\overline{G_2 \oplus G_1}) + G_4 \bar{G}_3 (\overline{G_2 \oplus G_1}) \\
 &= (G_2 \oplus G_1)(\bar{G}_4 \oplus G_3) + (G_2 \oplus G_1)(G_4 \oplus G_3) \\
 &= G_4 \oplus G_3 \oplus G_2 \oplus G_1 \\
 &= B_2 \oplus G_1
 \end{aligned}$$


Based on the above expressions, a logic circuit can be drawn as shown in Figure 4.33c.

4-bit Gray				4-bit binary			
G ₄	G ₃	G ₂	G ₁	B ₄	B ₃	B ₂	B ₁
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	1	0	0	1	0
0	0	1	0	0	0	1	1
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	1
0	1	0	1	0	1	1	0
0	1	0	0	0	1	1	1
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	1
1	1	1	1	1	0	1	0
1	1	1	0	1	0	1	1
1	0	1	0	1	1	0	0
1	0	1	1	1	1	0	1
1	0	0	1	1	1	1	0
1	0	0	0	1	1	1	1


(a) Conversion table

 


(c) Logic diagram

 


B₄ = G₄
K-map for B₄

 

B₃ = G₄ ⊕ G₃
K-map for B₃

 

B₂ = G₄ ⊕ G₃ ⊕ G₂
K-map for B₂

 

B₁ = G₄ ⊕ G₃ ⊕ G₂ ⊕ G₁
K-map for B₁

(b) K-maps

Figure 4.33 4-bit Gray-to-binary code converter.

4.16.3 Design of a 4-bit Binary-to-BCD Code Converter

The input is a 4-bit binary. There are 16 possible combinations of 4-bit binary inputs (representing 0–15) and all are valid. Hence there are no don't cares. Since the input is of 4 bits (i.e. a maximum of 2 decimal digits), the output has to be an 8-bit one; but since the first three bits will all be a 0 for all combinations of inputs, the output can be treated as a 5-bit one. The conversion is shown in the conversion table in Figure 4.34a. From the conversion table, we observe that the expressions for BCD outputs are as follows:

$$A = \Sigma m(10, 11, 12, 13, 14, 15)$$

$$B = \Sigma m(8, 9)$$

$$C = \Sigma m(4, 5, 6, 7, 14, 15)$$

$$D = \Sigma m(2, 3, 6, 7, 12, 13)$$

$$E = \Sigma m(1, 3, 5, 7, 9, 11, 13, 15)$$

Drawing the K-maps for the outputs and minimizing them as shown in Figure 4.34c the minimal expressions for the BCD outputs A, B, C, D, and E in terms of the 4-bit binary inputs $B_4, B_3, B_2,$ and B_1 are as follows:

$$A = B_4 B_3 + B_4 B_2$$

$$B = B_4 \bar{B}_3 \bar{B}_2$$

$$C = \bar{B}_4 B_3 + B_3 B_2$$


$$D = B_4 B_3 \bar{B}_2 + \bar{B}_4 B_2$$

$$E = B_1$$

A logic diagram can be drawn based on the above minimal expressions.

Decimal	4-bit binary				BCD output				
	B_4	B_3	B_2	B_1	A	B	C	D	E
0	0	0	0	0	0	0	0	0	0
1	0	0	0	1	0	0	0	0	1
2	0	0	1	0	0	0	0	1	0
3	0	0	1	1	0	0	0	1	1
4	0	1	0	0	0	0	1	0	0
5	0	1	0	1	0	0	1	0	1
6	0	1	1	0	0	0	1	1	0
7	0	1	1	1	0	0	1	1	1
8	1	0	0	0	0	1	0	0	0
9	1	0	0	1	0	1	0	0	1
10	1	0	1	0	1	0	0	0	0
11	1	0	1	1	1	0	0	0	1
12	1	1	0	0	1	0	0	1	0
13	1	1	0	1	1	0	0	1	1
14	1	1	1	0	1	0	1	0	0
15	1	1	1	1	1	0	1	0	1

(a) Conversion table

 

(b) Block diagram

Figure 4.34 4-bit binary-to-BCD code converter (Contd.)

 


Figure 4.34 4-bit binary-to-BCD code converter.

4.16.4 Design of a 4-bit BCD-to-XS-3 Code Converter

BCD means 8421 BCD. The 4-bit input BCD code ($B_4 B_3 B_2 B_1$) and the corresponding output XS-3 code ($X_4 X_3 X_2 X_1$) numbers are shown in the conversion table in Figure 4.35a. The input combinations 1010, 1011, 1100, 1101, 1110, and 1111 are invalid in BCD. So they are treated as don't cares.

8421 code				XS-3 code			
B_4	B_3	B_2	B_1	X_4	X_3	X_2	X_1
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0

(a) Conversion table

$$X_4 = \sum m(5, 6, 7, 8, 9) + d(10, 11, 12, 13, 14, 15)$$

$$X_3 = \sum m(1, 2, 3, 4, 9) + d(10, 11, 12, 13, 14, 15)$$

$$X_2 = \sum m(0, 3, 4, 7, 8) + d(10, 11, 12, 13, 14, 15)$$

$$X_1 = \sum m(0, 2, 4, 6, 8) + d(10, 11, 12, 13, 14, 15)$$

The minimal expressions are

$$X_4 = B_4 + B_3B_2 + B_3B_1$$

$$X_3 = B_3\bar{B}_2\bar{B}_1 + \bar{B}_3B_1 + \bar{B}_3B_2$$

$$X_2 = \bar{B}_2\bar{B}_1 + B_2B_1$$

$$X_1 = \bar{B}_1$$

(b) Minimal expressions

Figure 4.35 4-bit BCD-to-XS-3 code converter (Contd.)

	B_2B_1				
	00	01	11	10	
B_4B_3	00	0	1	3	2
	01	4	5	7	6
	11	12	13	15	14
	10	8	9	11	10
		1	1	x	x

$$X_4 = B_4 + B_3B_2 + B_3B_1$$

K-map for X_4

	B_2B_1				
	00	01	11	10	
B_4B_3	00	0	1	3	2
	01	4	5	7	6
	11	12	13	15	14
	10	8	9	11	10
		1	x	x	

$$X_3 = B_3\bar{B}_2\bar{B}_1 + \bar{B}_3B_1 + \bar{B}_3B_2$$

K-map for X_3

	B_2B_1				
	00	01	11	10	
B_4B_3	00	1	3	2	
	01	4	5	7	6
	11	12	13	15	14
	10	8	9	11	10
		1	x	x	

$$X_2 = \bar{B}_2\bar{B}_1 + B_2B_1$$

K-map for X_2

	B_2B_1				
	00	01	11	10	
B_4B_3	00	1	3	2	
	01	4	5	7	6
	11	12	13	15	14
	10	8	9	11	10
		1	x	x	

$$X_1 = \bar{B}_1$$

K-map for X_1

(c) K-maps

Figure 4.35 4-bit BCD-to-XS-3 code converter.

The expressions for the outputs X_4 , X_3 , X_2 and X_1 are shown in Figure 4.35b. Drawing K-maps for the outputs X_4 , X_3 , X_2 and X_1 in terms of the inputs B_4 , B_3 , B_2 , and B_1 and simplifying them, as shown in Figure 4.35c the minimal expressions for X_4 , X_3 , X_2 , and X_1 are as shown in Figure 4.35b. A logic diagram can be drawn based on those minimal expressions.

4.16.5 Design of a BCD-to-Gray Code Converter

The BCD to Gray code conversion table is shown in Figure 4.36a. For a 4-bit BCD code minterms 10, 11, 12, 13, 14, and 15 are don't cares. So the expressions for the Gray code outputs in terms of BCD inputs are as follows:

$$G_3 = \sum m(8, 9) + d(10, 11, 12, 13, 14, 15)$$

$$G_2 = \sum m(4, 5, 6, 7, 8, 9) + d(10, 11, 12, 13, 14, 15)$$


$$G_1 = \sum m(2, 3, 4, 5) + d(10, 11, 12, 13, 14, 15)$$

$$G_0 = \sum m(1, 2, 5, 6, 9) + d(10, 11, 12, 13, 14, 15)$$

The K-maps for G_3 , G_2 , G_1 , and G_0 , their minimization, and the minimal expressions obtained from them are shown in Figure 4.37. The logic diagram of the BCD to Gray code converter based on those minimal expressions is shown in Figure 4.36b.

BCD code				Gray code			
B ₃	B ₂	B ₁	B ₀	G ₃	G ₂	G ₁	G ₀
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	0
0	1	0	1	0	1	1	1
0	1	1	0	0	1	0	1
0	1	1	1	0	1	0	0
1	0	0	0	1	1	0	0
1	0	0	1	1	1	0	1

(a) BCD-to-Gray code conversion table

 

(b) Logic diagram

Figure 4.36 BCD-to-Gray code converter.

 
 
 
 


Figure 4.37 K-maps for a BCD-to-Gray code converter.