

Encoders

- An encoder is a digital circuit that performs the inverse operation of a decoder.
- An encoder has 2^n (or fewer) input lines and n output lines
- The output lines, as an aggregate, generate the binary code corresponding to the input value.
- An example of an encoder is the octal-to-binary encoder which has eight inputs (one for each of the octal digits) and three outputs that generate the corresponding binary number.
- It is assumed that only one input has a value of 1 at any given time
- The encoder can be implemented with OR gates whose inputs are determined directly from the truth table

Inputs	Outputs															
	x	y	z													
D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇									
1	0	0	0	0	0	0	0		0	0	0					
0	1	0	0	0	0	0	0		0	0	1					
0	0	1	0	0	0	0	0		0	1	0					
0	0	0	1	0	0	0	0		0	1	1					
0	0	0	0	1	0	0	0		1	0	0					
0	0	0	0	0	1	0	0		1	0	1					
0	0	0	0	0	0	1	0		1	1	0					
0	0	0	0	0	0	0	1		1	1	1					

- Output z is equal to 1 when the input octal digit is 1, 3, 5, or 7.
 - Output y is equal to 1 for the octal digits 2, 3, 6, or 7; and output x is 1 for digits 4, 5, 6, or 7
- $$z = D_1 + D_3 + D_5 + D_7$$
- $$y = D_2 + D_3 + D_6 + D_7$$
- $$x = D_4 + D_5 + D_6 + D_7$$
- The encoder can be implemented with three OR gates.
- The encoder has the limitation that only one input can be active at any given time.
- If two inputs are active simultaneously, the output produces an undefined combination.
- To resolve this ambiguity, encoder circuits must establish an input priority to ensure that only one output is encoded.
- Another ambiguity on the octal-to-binary encoder is that an output with all 0's is generated when all the inputs are 0; but this output is same as when D_0 is equal to 1.
- This discrepancy can be resolved by providing one more output to indicate whether at least one input is equal to 1.

Priority Encoder

- A priority encoder is an encoder circuit that includes the priority function.
- The operation of the priority encoder is such that if two or more inputs are equal to 1 at the same time the input having the highest priority will take precedence.
- In addition to the two outputs x and y , the circuit has a third output designated by V ; this is a valid bit indicator that is set to 1 when one or more inputs are equal to 1.
- If all inputs are 0, there is no valid input and V is equal to 0.
- The other two outputs are not specified when V equals 0 and are specified as don't-care conditions.

Inputs				Outputs		
D_0	D_1	D_2	D_3	x	y	v
0	0	0	0	x	x	0
1	0	0	0	0	0	1
x	1	0	0	0	1	1
x	x	1	0	1	0	1
x	x	x	1	1	1	1


$D_0 D_1 D_2 D_3$	00	01	11	10	D_2
00	x	1	2	3	
01	4	5	7	6	
11	12	13	15	14	
10	8	9	11	10	

$D_0 D_1$	00	01	11	10	D_2
00	x	1	2	3	
01	4	5	7	6	
11	12	13	15	14	
10	8	9	11	10	

$$y = D_3 + D_1 D_2'$$

$D_0 D_1$	00	01	11	10	D_2
00	0	1	2	3	
01	4	5	7	6	
11	12	13	15	14	
10	8	9	11	10	

$$v = D_0 + D_1 + D_2 + D_3$$

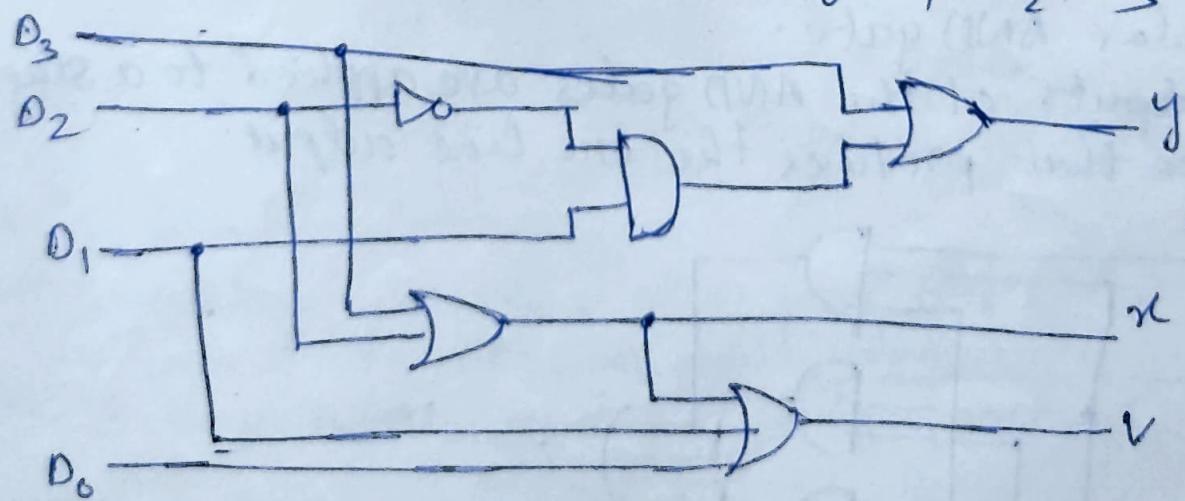

Four-bit
Priority
Encoder