

## • Magnitude Comparator (Comparator)

→ A magnitude comparator is a combinational circuit that compares two numbers  $A$  and  $B$  and determines their relative magnitudes.


→ The outcome of the comparison is specified by three binary variables that indicate whether  $A > B$ ,  $A = B$ , or  $A < B$ .

- Consider two numbers, A and B with four digits each.
- Write the coefficients of the numbers in descending order of significance.

$$A = A_3 A_2 A_1 A_0$$

$$B = B_3 B_2 B_1 B_0$$

- The two numbers are equal if all pairs of significant digits are equal:  $A_3 = B_3, A_2 = B_2, A_1 = B_1, A_0 = B_0$
- When the numbers are binary, the digits are either 1 or 0, and the equality of each pair of bits can be expressed logically with an exclusive-NOR function as  $x_i = A_i B_i + A_i' B_i'$  for  $i = 0, 1, 2, 3$  where  $x_i = 1$  only if the pair of bits in position  $i$  are equal.

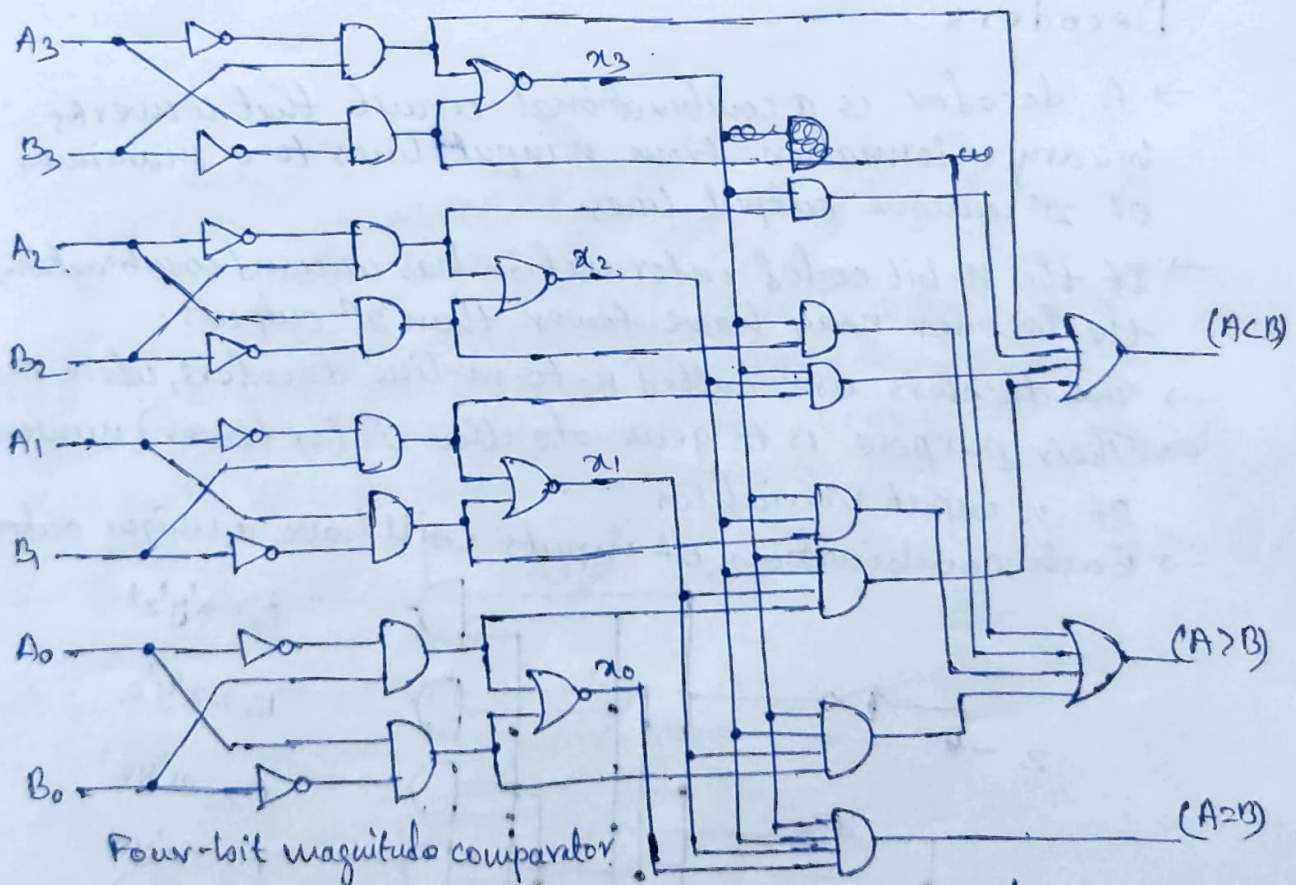

- The equality of the two numbers A and B is displayed in a combinational circuit by an output binary variable that we designate by the symbol  $(A=B)$ .

$$(A=B) = x_3 x_2 x_1 x_0$$

- The binary variable  $(A=B)$  is equal to 1 only if all pairs of the two numbers are equal.
- To determine whether A is greater or less than B, we inspect the relative magnitude of pairs of significant digits, starting from the most significant position.

→ If the two digits of a pair are equal, we compare the next lower significant pair of digits.

→ The comparison continues until a pair of unequal digits is reached.

→ The sequential comparison can be expressed logically by the two Boolean functions:

$$(A > B) = A_3 B_3' + x_3 A_2 B_2' + x_3 x_2 A_1 B_1' + x_3 x_2 x_1 A_0 B_0'$$

$$(A < B) = A_3' B_3 + x_3 A_2' B_2 + x_3 x_2 A_1' B_1 + x_3 x_2 x_1 A_0' B_0$$

→ The symbols  $(A > B)$  and  $(A < B)$  are binary output variables that are equal to 1 when  $A > B$  and  $A < B$ , respectively.