

* Design of Asynchronous Counters:

Design steps:

Step 1: Based on the description of the problem,

determine the required no. of FFs and desired counting sequence

Step 2: Draw state diagram


Step 3: Select the type of FFs to be used and ^{optional} write the truth table ^{with clear signal (Reset signal)} to be

NOTE: Asynchronous counters are designed by only two FFs viz; J-K & T FFs.

~~Step 4:~~

Condition to get toggling action

$$\rightarrow J = K = 1; T = 1$$

 

NOTE: In order to design up counter

\rightarrow Q should be connected with the -ve edge of CLK

$\rightarrow \bar{Q}$ should be connected with the +ve edge of CLK

Step 4: Draw circuit diagram

~~Step 4:~~ ^{optional} obtain

Step 5: Draw timing diagram

minimal expression for R using K-map

NOTE: In order to design down counter

\rightarrow Q should be connected with +ve edge of clock

$\rightarrow \bar{Q}$ should be connected with -ve edge of clock


* Design of a mod-8 asynchronous counter using JK FFs:

$2^n \rightarrow$ no. of bits.
 $2^n \geq N$
 \rightarrow Count No.

Step 1: No. of FFs = 3 ; Up Count.
 No. of states = 8 (000, 001, 010, 011, 100, 101, 110, 111)

All are valid states


Step 2: state diagram

 


Step 3: JK FFs are selected.

J = K = 1 for


CLK Pulses	Q ₃	Q ₂	Q ₁	Decimal equivalent	Reset
0	0	0	0	0	0
1	0	0	1	1	0
2	0	1	0	2	0
3	0	1	1	3	0
4	1	0	0	4	0
5	1	0	1	5	0
6	1	1	0	6	0
7	1	1	1	7	0
8	0	0	0	0	0

 

Step 5: logic diagram

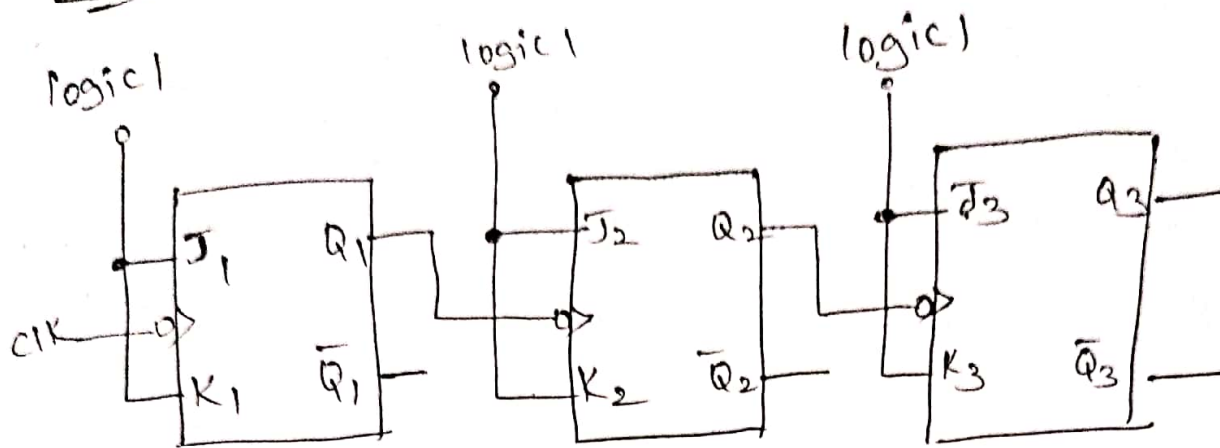

Step 6: Timing diagram

 

* Design of a Mod-10 Asynchronous Counter using


JK FFs:

Step 1: No. of FFs = 4

No. of states = $2^4 = 16$ ie, from 0000 to 1111

Valid states will be from 0000 to 1001.

Step 2: state diagram

 

Step 3: JK FFs are selected ; $J=K=1$ for all FFs


CLK Pulses	state				Reset/clear
	Q_4	Q_3	Q_2	Q_1	R
0	0	0	0	0	0
1	0	0	0	1	0
2	0	0	1	0	0
3	0	0	1	1	0
4	0	1	0	0	0
5	0	1	0	1	0
6	0	1	1	0	0
7	0	1	1	1	0
8	1	0	0	0	0
9	1	0	0	1	0
10	0	0	0	0	1

Step 4: K Map for R


$Q_4 Q_3$ \ $Q_2 Q_1$	00	01	11	10
00				
01				
11	X	X	X	X
10	0	0	X	1

$R = Q_4 Q_2$

Step 5: Logic diagram

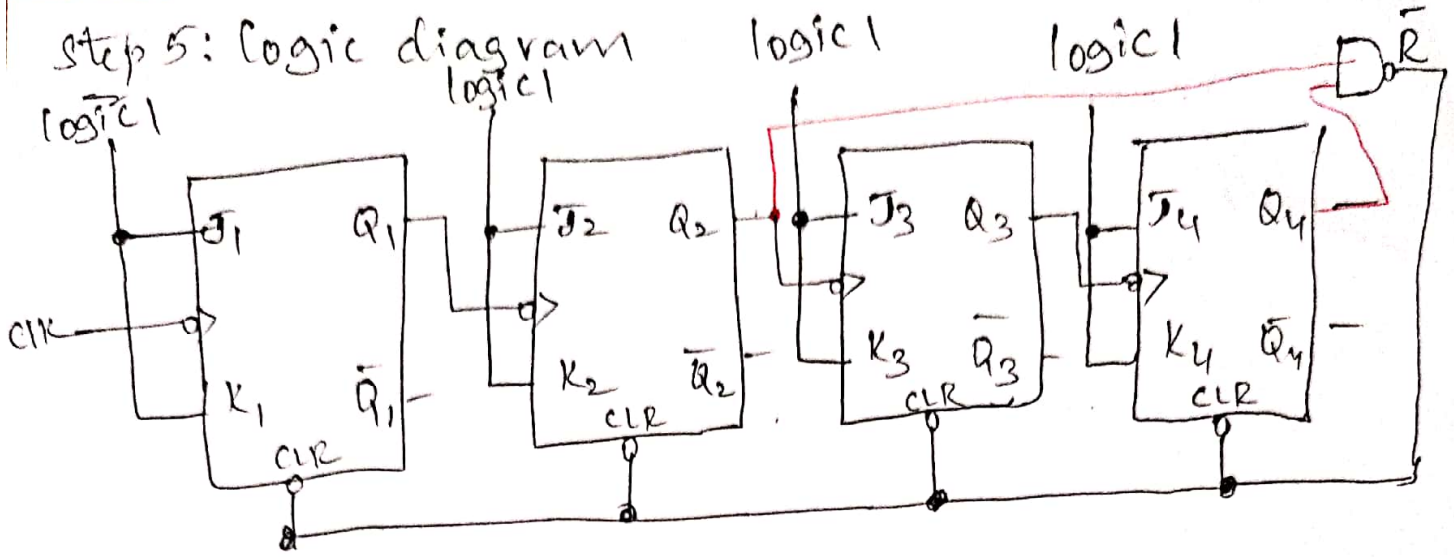

Step 6: Timing Diagram

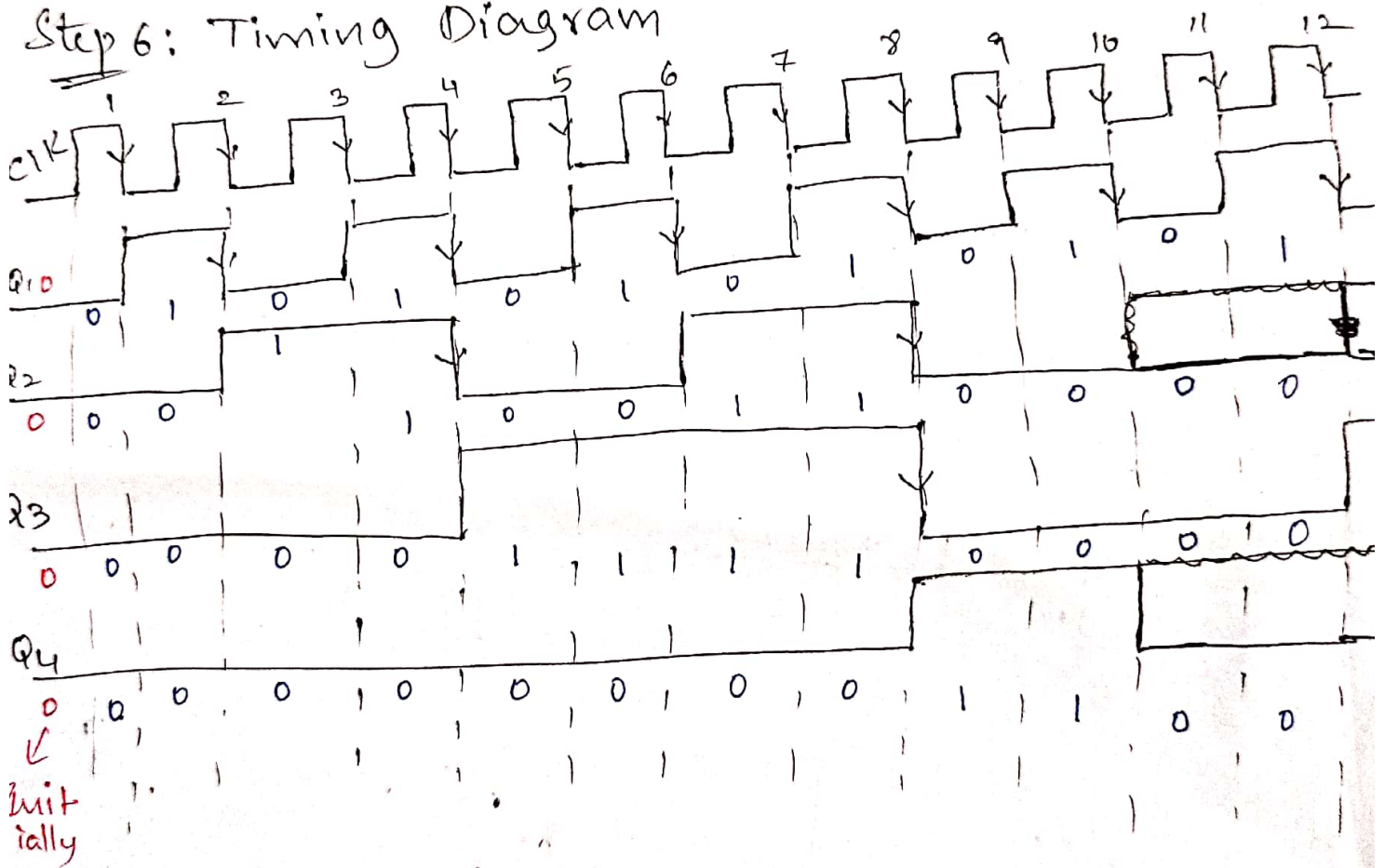


* Design of a mod-6 asynchronous counter using TFFs:

TFFs:

Step 1: No. of FF = 3 ; Up count

No. of states = $2^3 = 8$ (000, 001, 010, 011, 100, 101, 110, 111)
110 & 111 are invalid states.


Step 2: State diagram

 

Step 3: TFFs are selected. $T=1$ for all FFs


Clk Pulses	State			Reset/clk
	Q ₃	Q ₂	Q ₁	R
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	0
4	1	0	0	0
5	1	0	1	0
6	0	0	0	1
7	0	0	1	1

Step 4: KMap for R

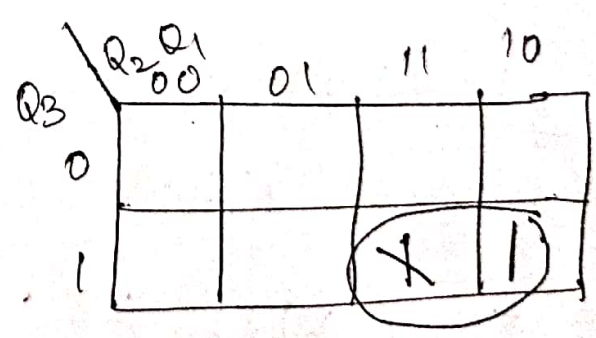


$R = Q_3 \cdot Q_2$

Step 5:

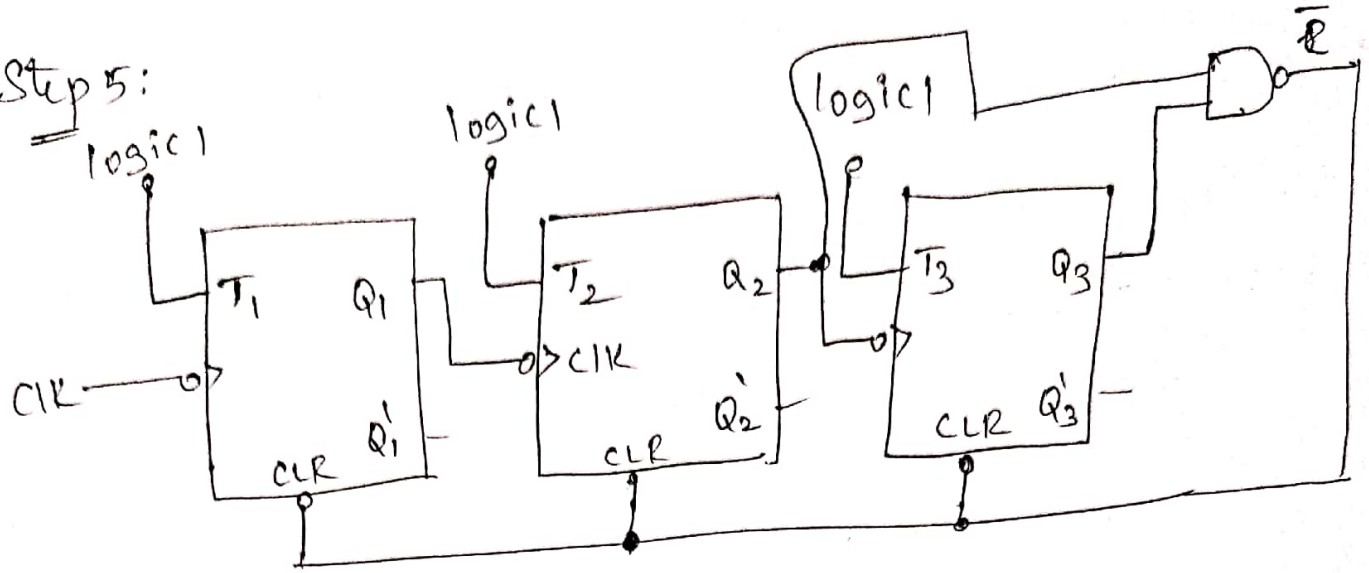

Step 6:

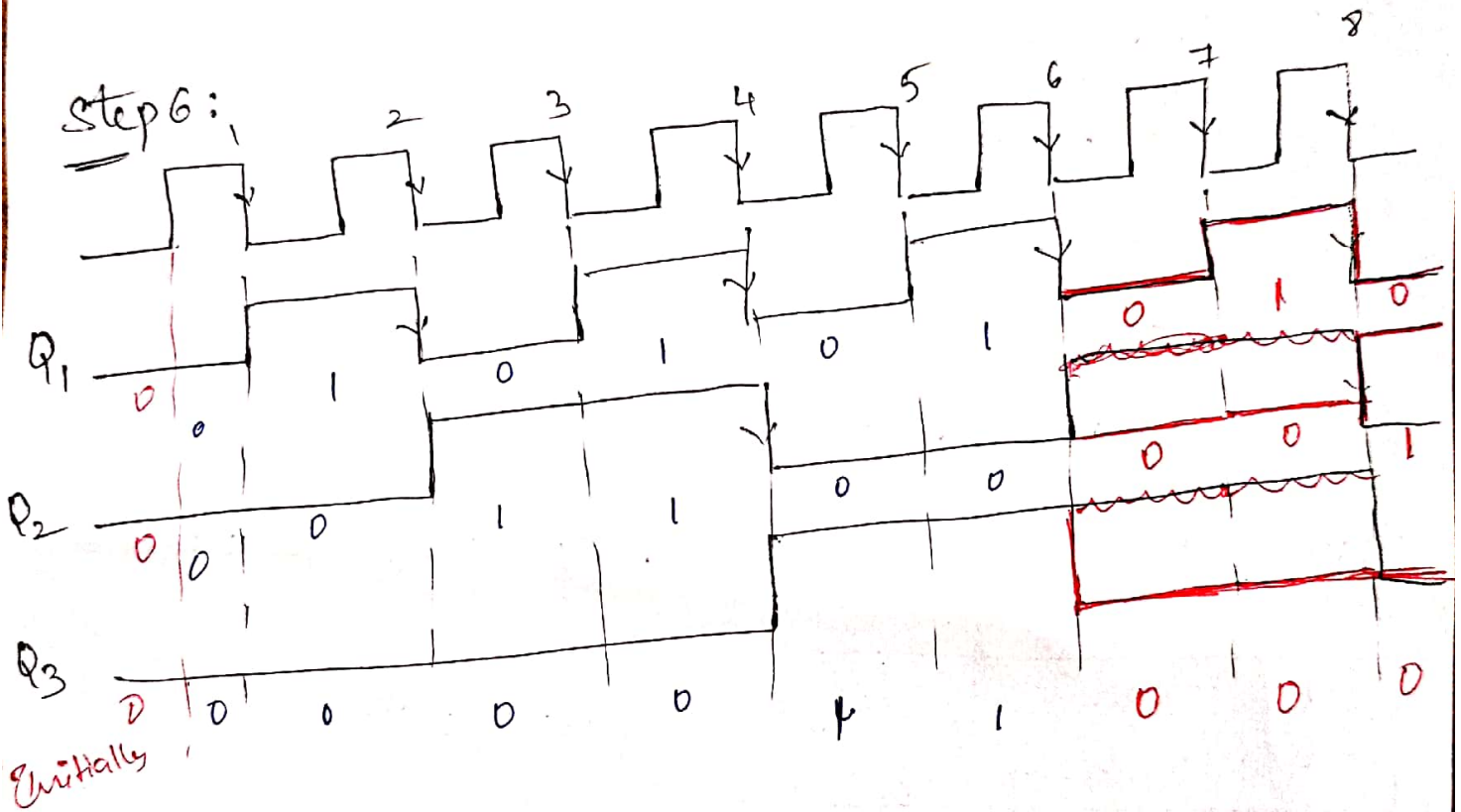


* Two-bit Ripple up-counter using Negative edge-triggered FFs:

Step 1: No. of FFs = 2 ; Up count

No. of states = $2^2 = 4$ (00, 01, 10, 11)

Step 2: state diagram

 


Step 3: JK FFs are selected.

$J = K = 1$ for all FFs.


CLK Pulses	state	
	Q_2	Q_1
0	0	0
1	0	1
2	1	0
3	1	1

Step 4:
Not needed

Step 5: Logic diagram

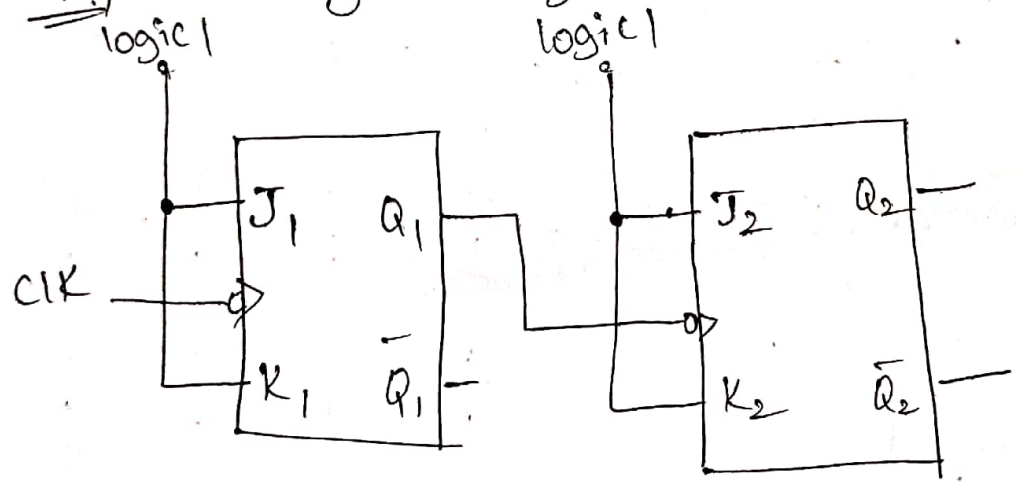

Step 6: Timing Diagram

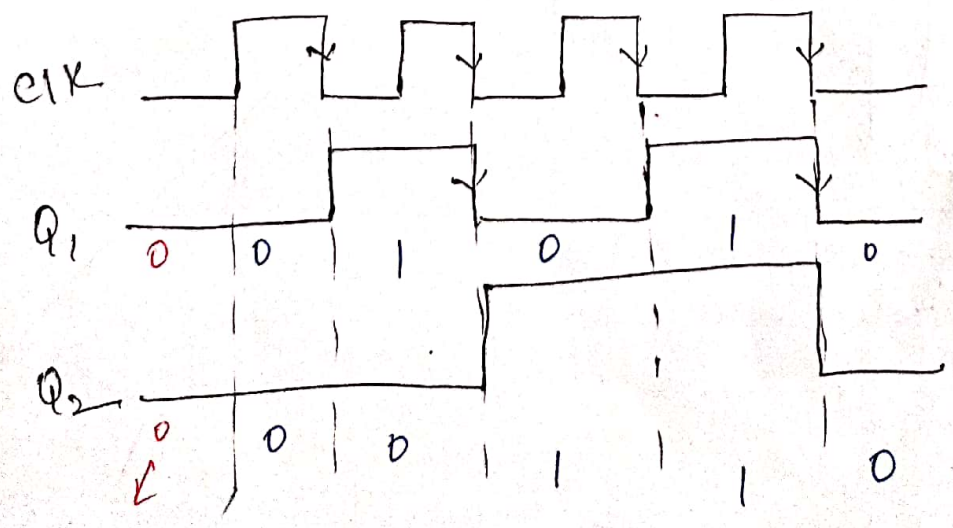


Initially

* Two-bit Ripple Down-Counter Using Negative edge-triggered flip-flops:

Step 1: No. of FFs = 2 ; Down Count
 No. of states = $2^2 = 4$ (00, 01, 10, 11)

Step 2: State diagram

 

Step 3: JK FFs are selected.


Step 4: KMap not needed

CLK	state	state
Pulses	n	n


CLK Pulses	Q_2	Q_1	\bar{Q}_2	\bar{Q}_1
0	1	1	0	0
1	1	0	0	1
2	0	1	1	0
3	0	0	1	1

o/p's to be read at Q_2 & Q_1 .

Step 5: logic diagram

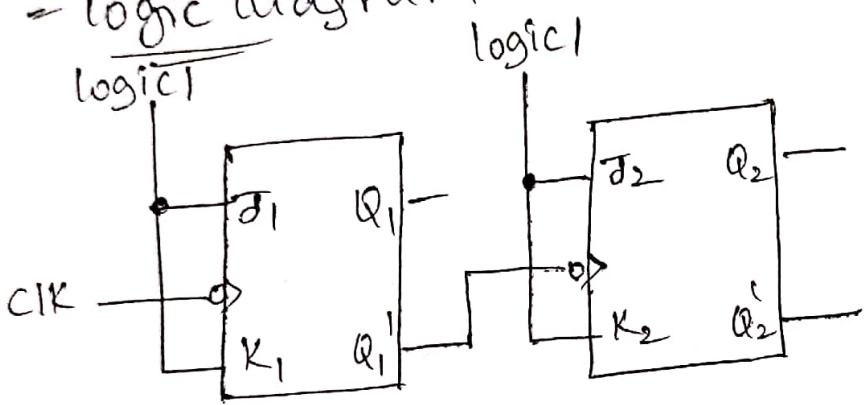

Step 6: Timing diagram

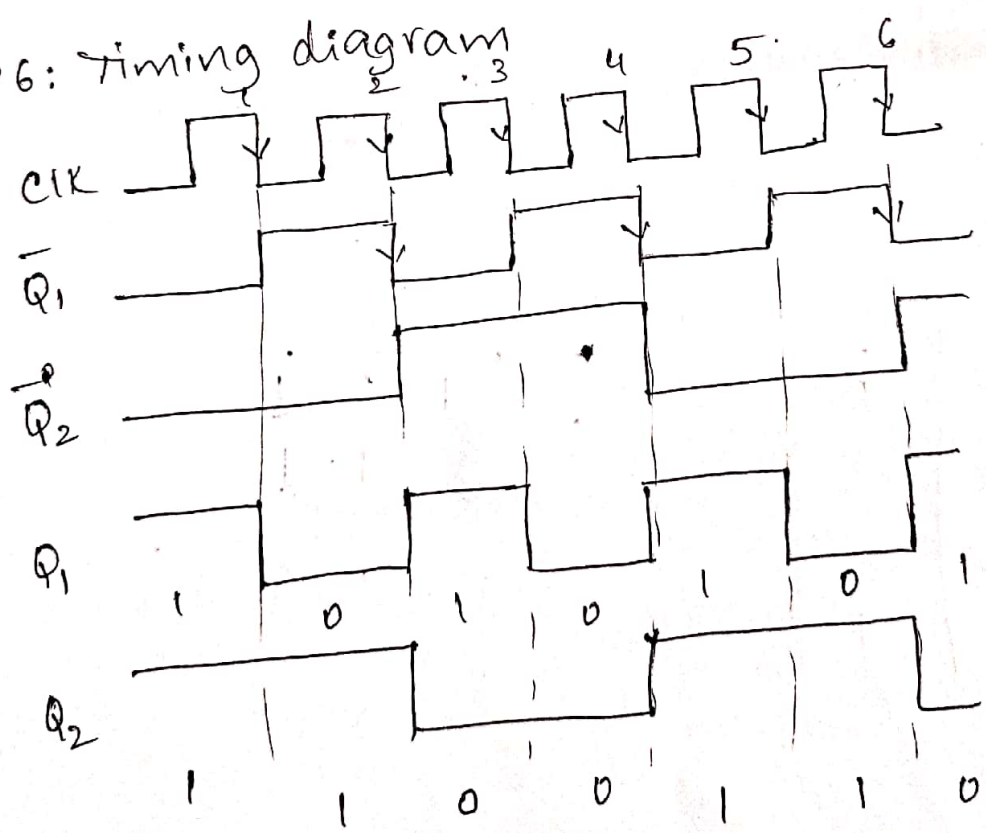

* Two-bit ripple up-down counter:

(20)


Step 1: No. of FFs = 2 ; Up & Down count

let's say, if $M=1$, circuit works as Up Counter

$M=0$, circuit works as Down Counter

Where $M \rightarrow$ Mode signal/control signal


Step 2: State diagram

 

Step 3: JK FFs are selected

$J=K=1$ for all FFs


M	Q	\bar{Q}	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

 


Step 4:

M	Q	Q'	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Step 5: logic diagram $Y = MQ + M'Q'$

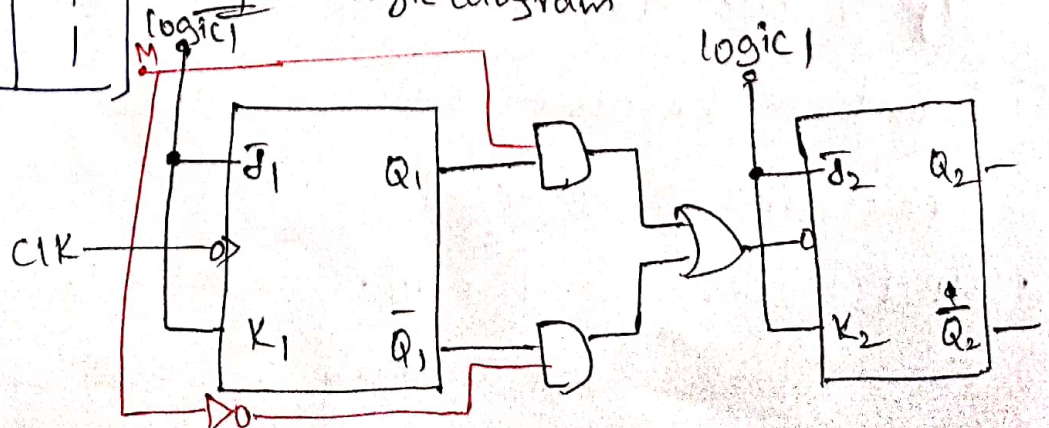

Step 5: Logic diagram

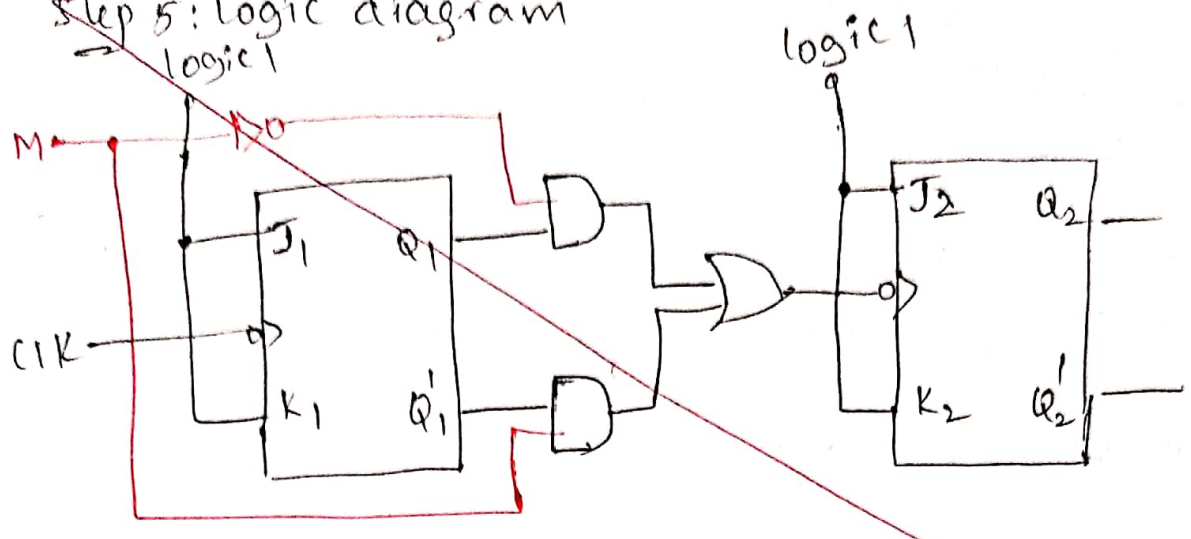

* Shift Register Counter:

↳ Design and operation of Ring Counter

↳ Design and operation of Twisted-Ring Counter

• ~~Design~~ One of the applications of shift registers is that they can be arranged to form several types of counters.

• Shift register counters are obtained from serial-in, serial-out shift registers by providing feedback from the o/p of the last FF to the i/p of the first FF. These devices are called counters because they exhibit a specified sequence of states.

• Most widely used shift register counters are ring counter and twisted ring counter.