


①

UNIT - IV
Registers and Counters

* Introduction:

- Flip-flop is a 1-bit memory cell.
- To increase the storage capacity, a group of flipflops are needed. This group of flipflops is known as REGISTER
- The n-bit register consists of "n" no. of FFs and is capable of storing n-bits.
- A Flip-flop is referred to as single-bit register

 EX: 4-bit register \rightarrow requires 4 FF



- A register is a digital circuit with two basic fns: Data storage and Data Movement
- A shift register provides the data movement function
- A shift register "shifts" its 0/1p once every clock cycle

Definition of a Shift Register:

- A shift register is a group of flip flops set up in a linear function with their i/p and o/p's are connected together in such a way that the data shifted from one device to another when the circuit is active.

Shift Register types:





- ① Serial in Serial out (SISO)
- ② Serial in parallel out (SIPO)
- ③ Parallel in parallel out (PIPO)
- ④ Parallel in serial out (PISO)

Shift Register types w.r.t direction:

- ① Left shift / Right shift → Unidirectional shift register
- ② Bidirectional shift register → shifts both left & right
- ③ Universal shift register
↳ shifts both left & right and also have parallel loading capabilities

Data Movement:

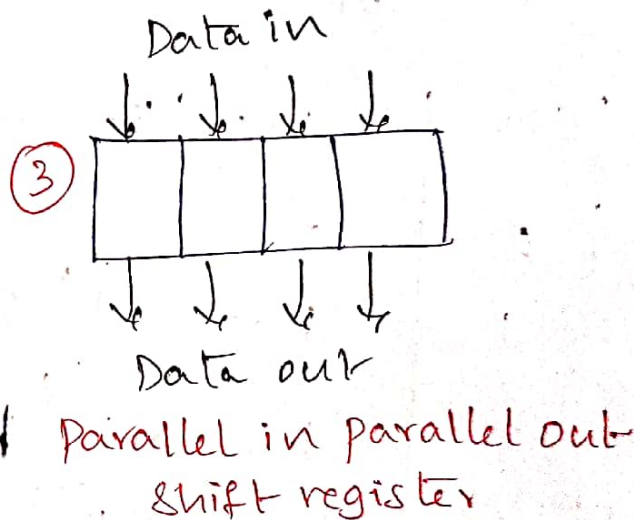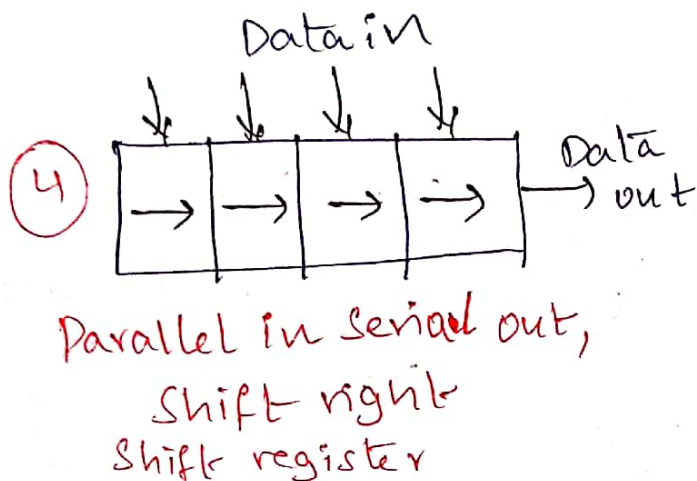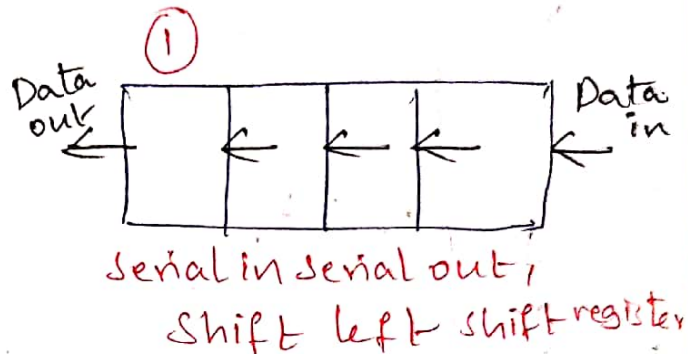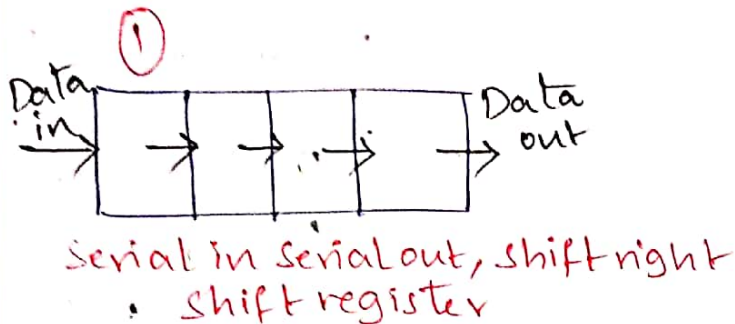The bits in a shift register can move in any of the following manners:



① SISO:

• Serial in serial out

 
 


Fig: SISO, shift right Register
4-bit

CLK	Q ₃	Q ₂	Q ₁	Q ₀
Initially	0	0	0	0
↑	1	0	0	0
↑	1	1	0	0
↑	0	1	1	0
↑	1	0	1	1
↑	-	1	0	1
↑	-	-	1	0
↑	(000)	-	-	1

1 0 1 1
MSB LSB

DFF TT

CLK	D	Q _{int}
0	X	Q _{in}
↑	0	0
↑	1	1

(or)

CLK	Input	Q ₃	Q ₂	Q ₁	Q ₀
0	-	0	0	0	0
1	1	1	0	0	0
2	1	1	1	0	0
3	0	0	1	1	0
4	1	1	0	1	1
5	-	1	1	0	1
6	-	-	-	1	0
7	-	-	-	1	1

(2N-1) clock pulses are required for SISO.

 


Fig: SISO, 4 bit shift left Register

(or)


(3)

Data ↓
1011
MSB LSB

CLK	D ₃	D ₂	D ₁	D ₀	Q ₃	Q ₂	Q ₁	Q ₀
0	0	0	0	0	0	0	0	0
1	1	0	0	0	1	0	0	0
2	1	1	0	0	1	1	0	0
3	0	1	1	0	0	1	1	0
4	1	0	1	1	1	0	1	1
5	0	1	0	1	0	1	0	1
6	0	0	1	0	0	0	1	0
7	0	0	0	1	0	0	0	1

1011
MSB LSB

(2) SISO: Serial in parallel out

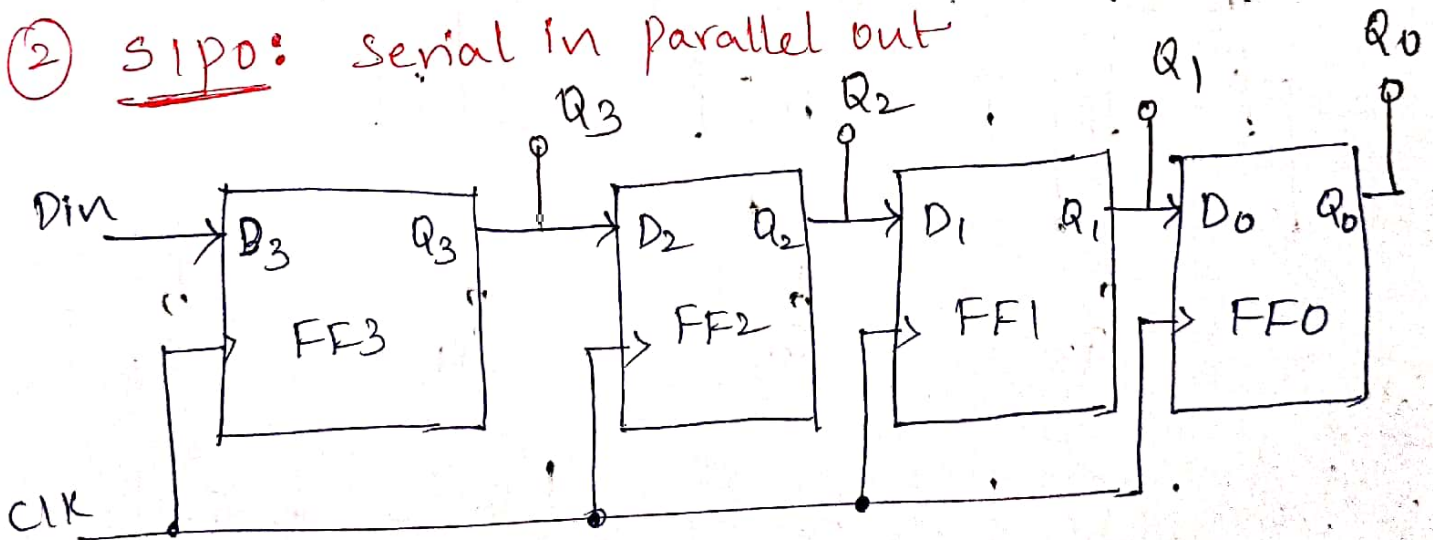

CLK	input	Q ₃	Q ₂	Q ₁	Q ₀
Initially → 0	0	0	0	0	0
1	1	1	0	0	0
2	1	1	1	0	0
3	0	0	1	1	0
4	1	1	0	1	1


1011
MSB LSB

For n bit transmission n clock pulses are required in SISO

CLK	D ₃	D ₂	D ₁	D ₀	Q ₃	Q ₂	Q ₁	Q ₀
0	0	0	0	0	0	0	0	0
1	1	0	0	0	1	0	0	0
2	1	1	0	0	1	1	0	0
3	0	1	1	0	0	1	1	0
4	1	0	1	1	1	0	1	1

Data
1011
MSB LSB


③ PIPO: parallel in parallel out

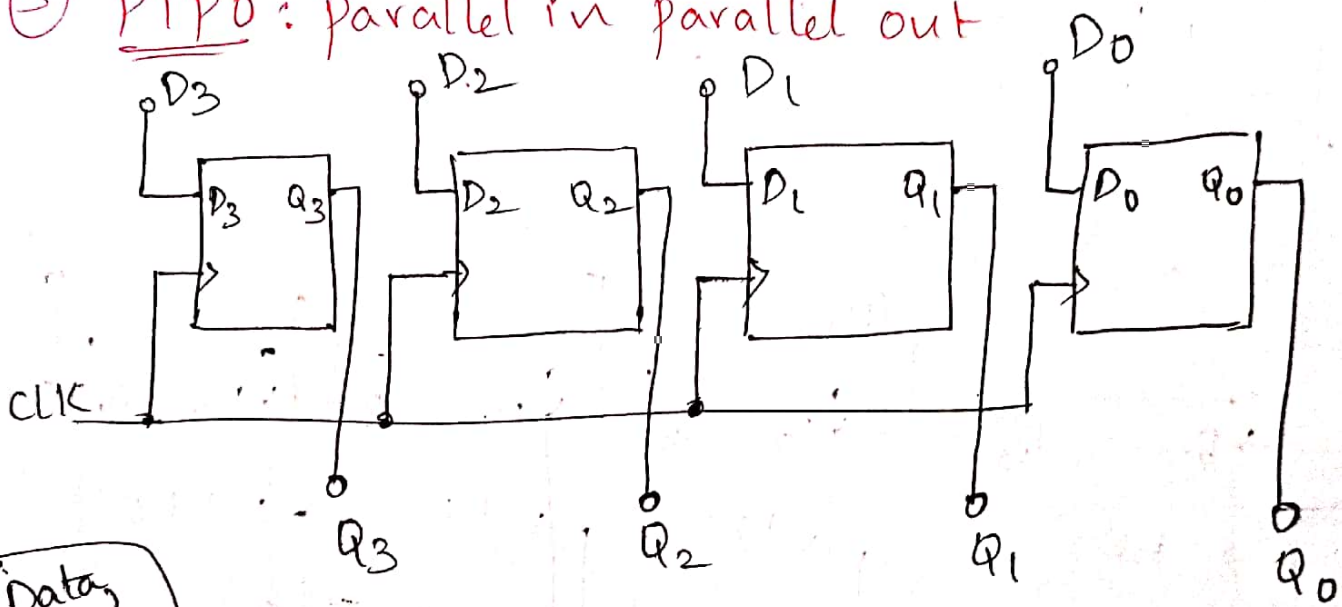

Data
1011
MSB LSB

CLK	D ₃	D ₂	D ₁	D ₀	Q ₃	Q ₂	Q ₁	Q ₀
0	0	0	0	0	0	0	0	0
1	1	0	1	1	1	0	1	1

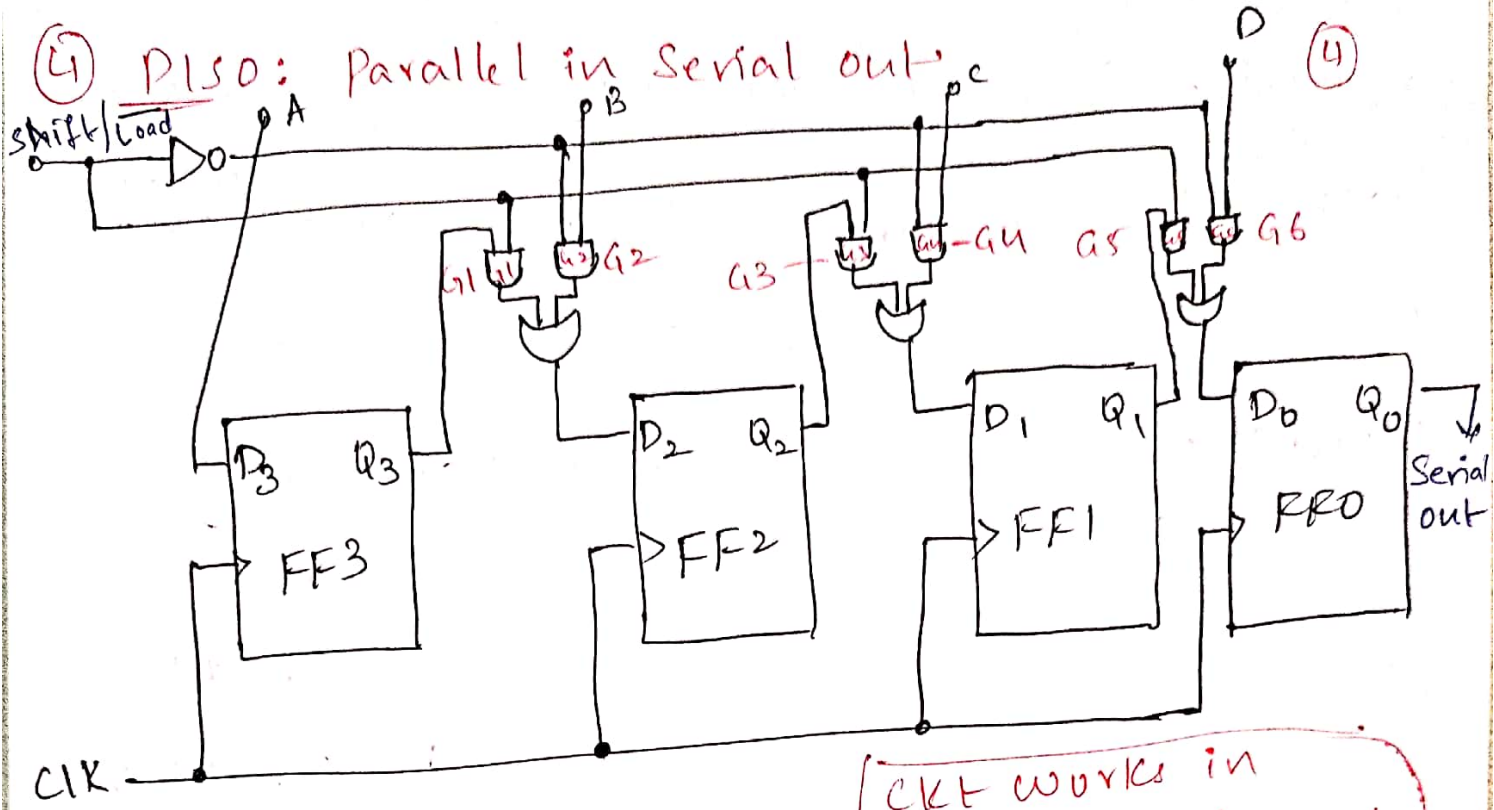In PIPO,
1 clock pulse is required for data transmission



Ckt works in
 - load mode and
 - shift mode

The ~~shift/load~~ allows

- the data to be entered in parallel form into the register and
- the data to be shifted out serially from

terminal Q_0

Case (i): If $\text{shift/load} = 1$

- If $\text{shift/load} = 1$, ckt works in ~~load~~ ^{shift} mode
- AND gates G_2, G_4, G_6 will be disabled and
- AND gates G_1, G_3, G_5 will be operational.

- Now the i/p's of the FFs becomes :
 A for FF3
 B for FF2
 C for FF1
 D for FF0

Case (ii): If $\text{Shift}/\overline{\text{load}} = 0$

- If $\text{Shift}/\overline{\text{load}} = 0$, ckt works in load mode. AND gates G_2, G_4, G_6 will be enabled ~~and~~ ^{whereas} AND gates G_1, G_3, G_5 will be disabled.


Now the i/ps of FFs becomes:

- A for FF3
- B for FF2
- C for FF1
- D for FF0

-
- In parallel-in, serial-out shift register, the data bits are entered simultaneously into their respective stages on parallel lines, rather than on a bit-by-bit basis on one line as with serial data i/ps, but the data bits are transferred out of the register serially, i.e., on a bit-by-bit basis over a single line.

(4) PIPO: Parallel in Serial out

(5)

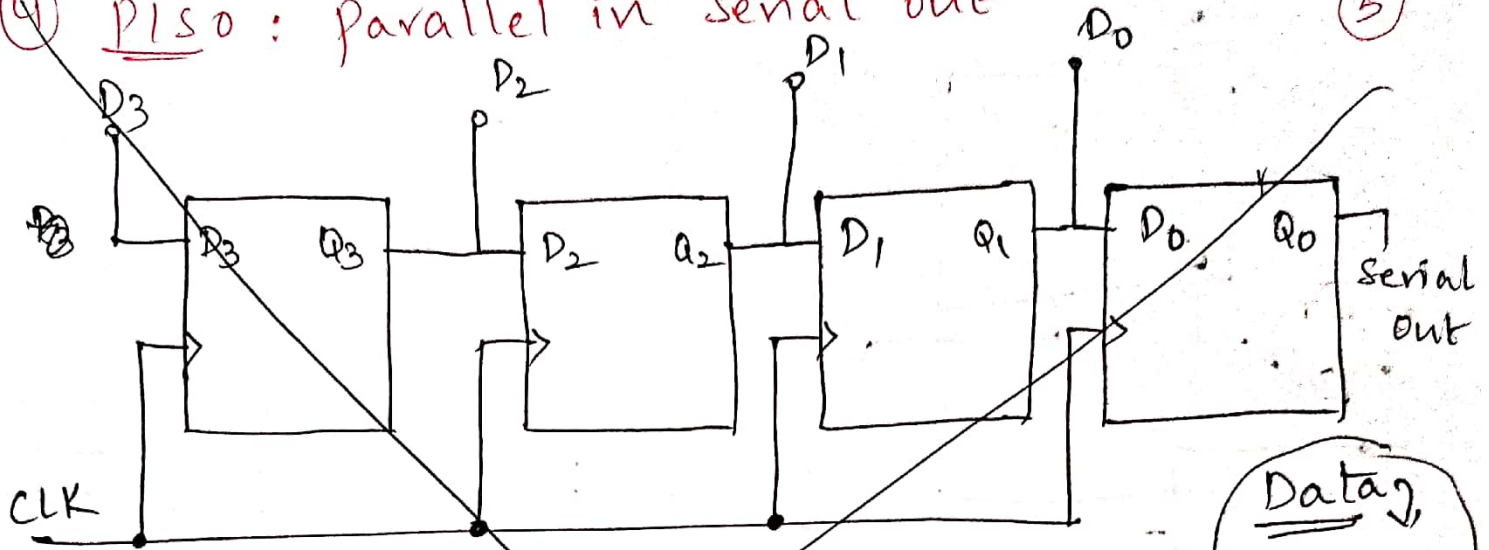

CLK	D ₃	D ₂	D ₁	D ₀	Q ₃	Q ₂	Q ₁	Q ₀
0	0	0	0	0	0	0	0	0
1	1	0	1	1	1	0	1	1
2	0	1	0	1	0	1	0	1
3	0	0	1	0	0	0	1	0
4	0	0	0	1	0	0	0	1

Data
1 0 1 1
MSB LSB

★★


* Bidirectional Shift Registers:

• A bidirectional shift register is one in which the data bits can be shifted from left to right or from right to left

• If (M → Mode Control i/p) logic ckt works as a

↳ M=1 → shift-right shift register

↳ M=0 → shift-left shift register

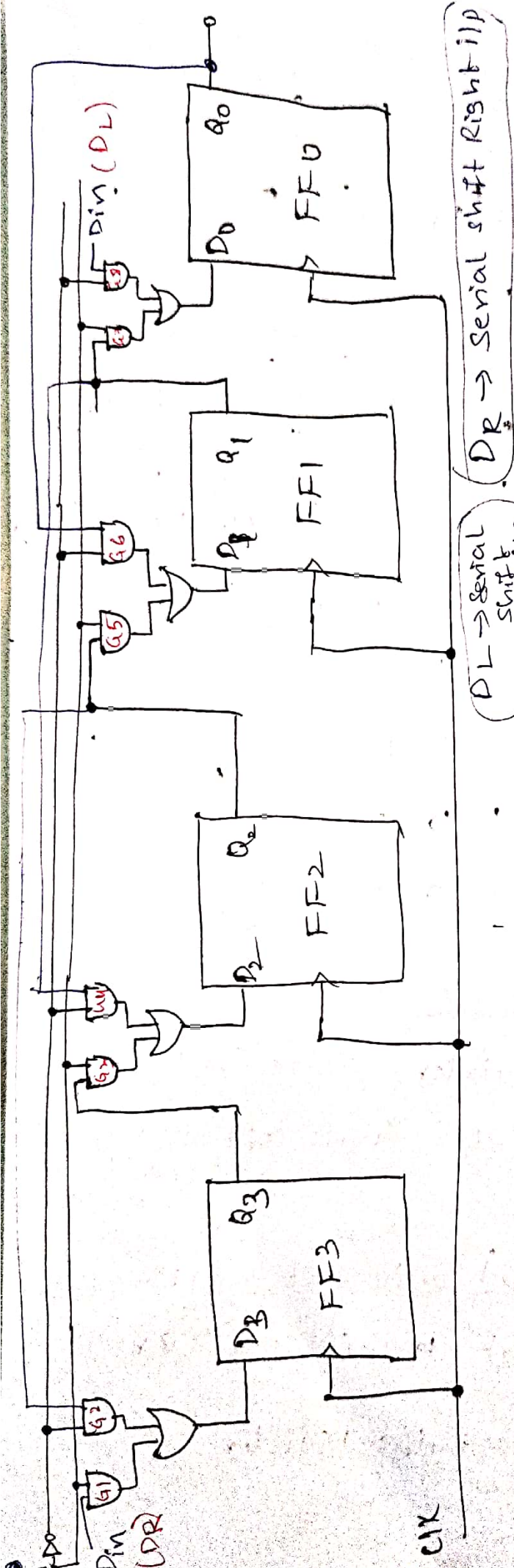

The bidirectional operation is achieved by using mode signal and two AND gates and one OR gate for each stage.

Case (i): $M=1$

If $M=1$, AND gates G_2, G_4, G_6, G_8 will be disabled where as AND gates G_1, G_3, G_5, G_7 will be enabled.

- Now, the ilps of the FFs ~~from right~~ will be:
- D_R for FF3
 - Q_3 for FF2
 - Q_2 for FF1
 - Q_1 for FF0

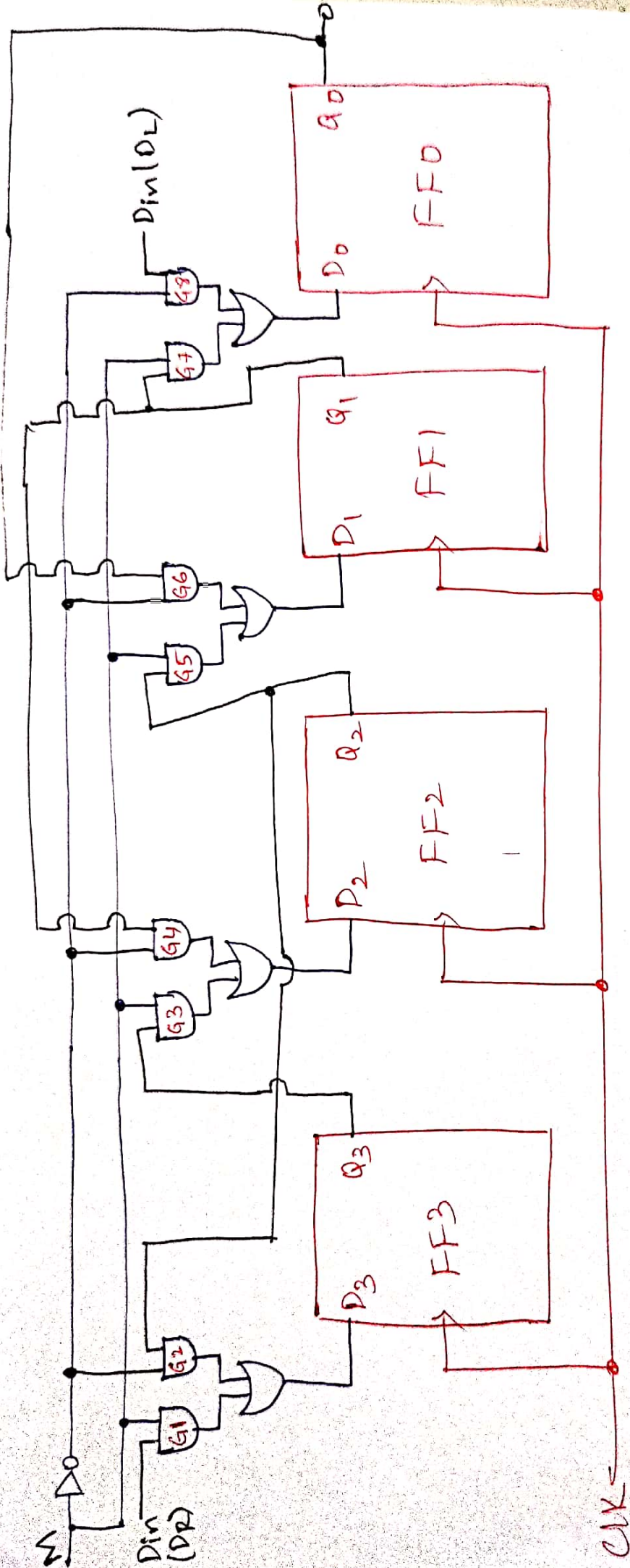


Fig: Logic diagram of a 4-bit bidirectional shift register

$D_L \rightarrow$ serial shift left i/p } \rightarrow Din
 $D_R \rightarrow$ serial shift right i/p }

- (6)
- The data is first stored in FF3, then FF2, FF1, and FF0. i.e; data is getting shifted from right to left i.e; shift-right operation

Case (ii): $M=0$

- Now AND gates G_2, G_4, G_6, G_8 are operational where as AND gates G_1, G_3, G_5, G_7 will be disabled
- The i/p's of the FFs will be:
 D_L for FF0
 Q_0' for FF1
 Q_1 for FF2
 Q_2 for FF3
- Here, the data is first stored in FF0; then FF1, FF2 and FF3. i.e; data is shifting ^{to} left side so. shift-left operation