

## Diode Clippers

The dkt <sup>with</sup> which the waveform is shaped by removing (or clipping) a portion of the i/p signal without disturbing the remaining part of the alternating waveform is called a clipper.

→ Clipping circuits are also referred to as voltage (or current) limiters, amplitude selectors, or slicers.

→ There are four categories of clippers (i) positive clipper (ii) negative clipper (iii) biased clipper (iv) combination clipper




### Positive clipper

→ In series positive clipper, when the i/p voltage is +ve, the diode does not conduct & acts as an open dkt, hence the +ve half cycle does not appear at the o/p, i.e., +ve half cycle is clipped off.

→ When the i/p signal is -ve, the diode conducts & acts as a closed switch, -ve half cycle appears at the o/p.

→ In shunt positive clipper, when i/p voltage is +ve, diode conducts & acts as short dkt & hence there is zero signal at the o/p, i.e., +ve half cycle is clipped off.

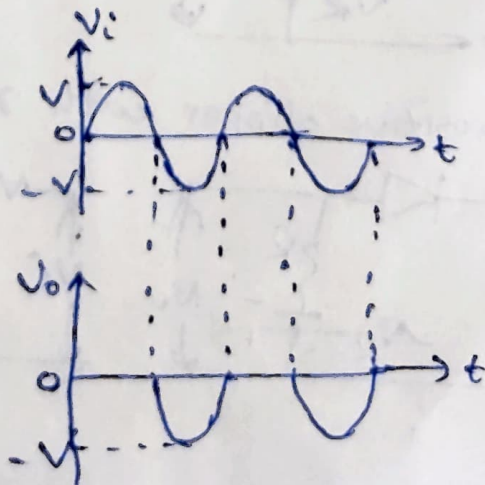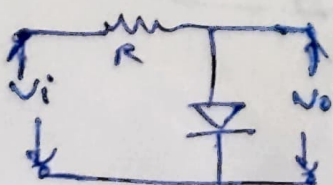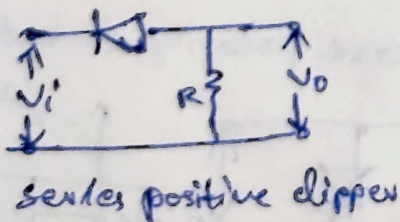→ When the i/p signal is -ve, diode does not conduct & acts as an open switch, -ve half cycle appears at the o/p.








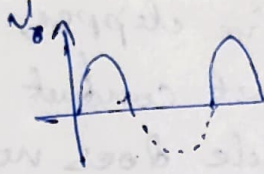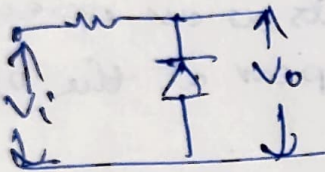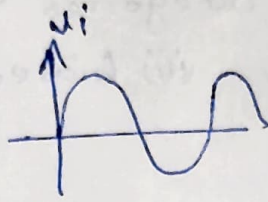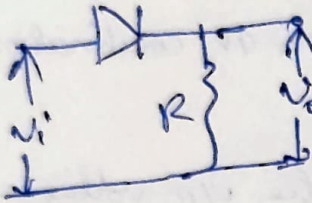
## Negative Clipper




→ In the series negative clipper, during the +ve half cycle of the i/p signal, the diode conducts & acts as a short-ckt & hence the +ve half cycle of the i/p signal will appear at the op.

→ During the -ve half cycle of the i/p signal, diode does not conduct & acts as an open ckt. The -ve half cycle will not appear at the op, i.e., -ve half cycle is clipped off.





## Biased Clipper

a) Biased positive clipper

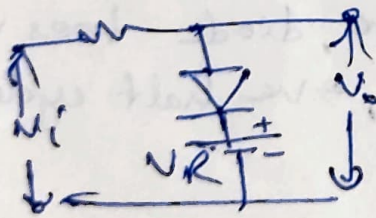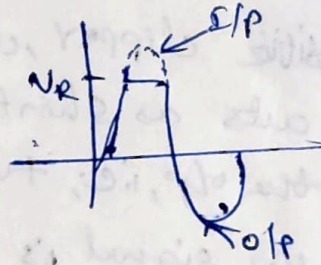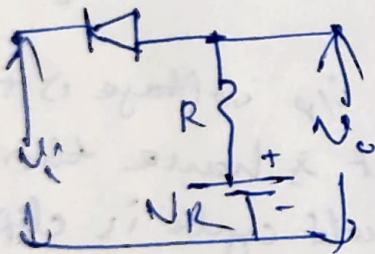


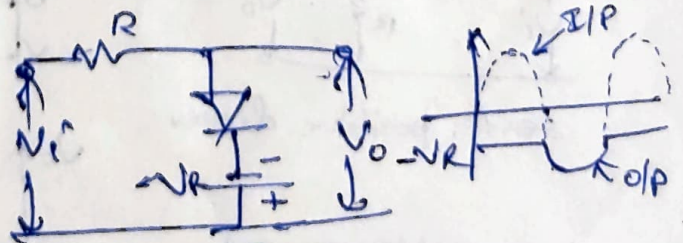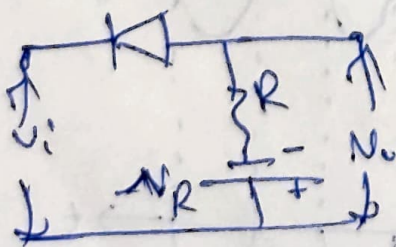b) Biased positive clipper with reverse polarity of battery \$V\_R\$







**Biased negative clipper**

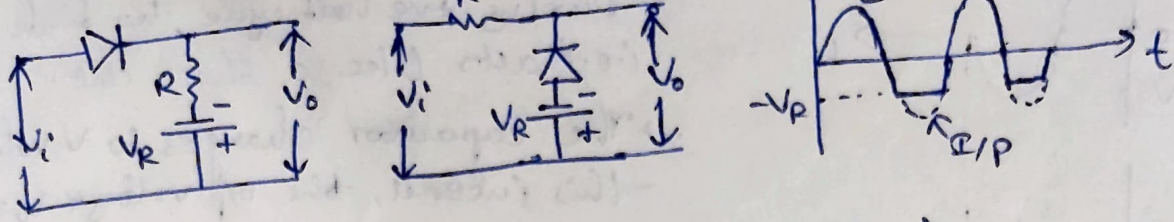

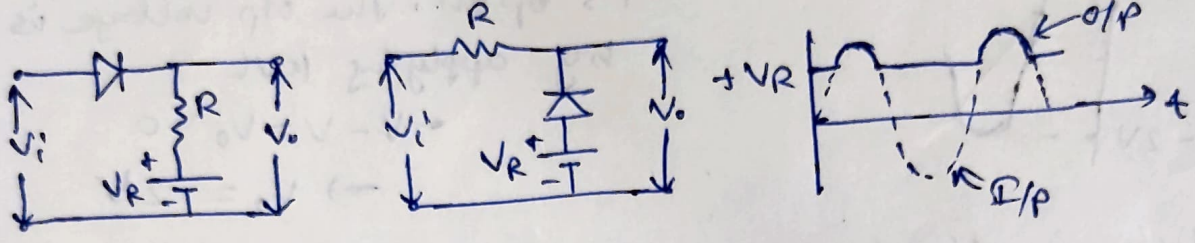
**d) Biased negative clipper with reverse polarity of battery VR**



**Combination Clipper**

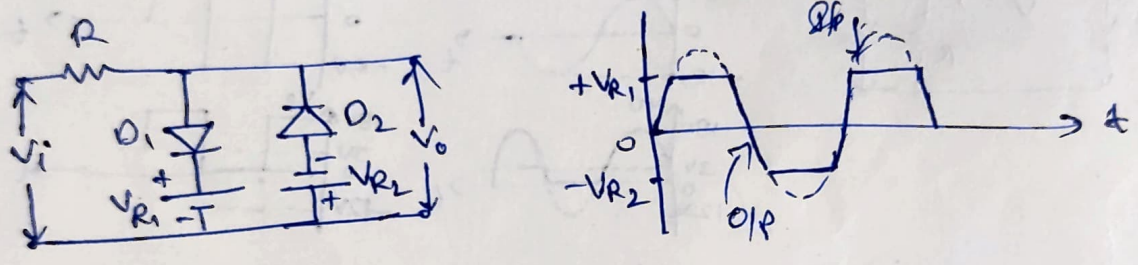

**Two level slicer**

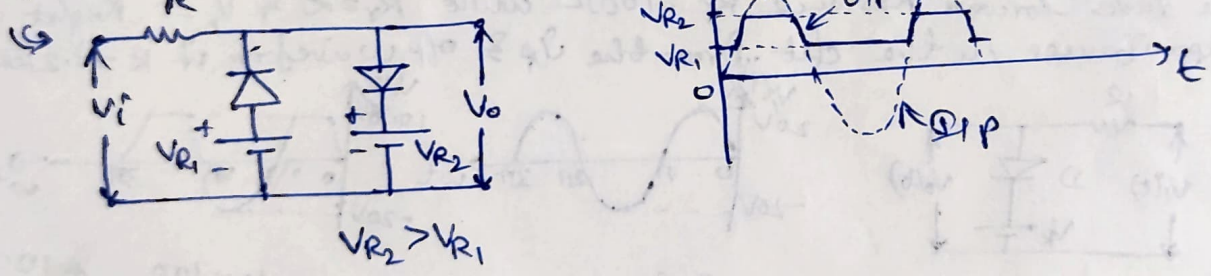


**Clampers**


Clamping n/w shifts (clamps) a signal to a different d.c. level, i.e., it introduces a dc level to an ac signal. Hence, the clamping n/w is also known as d.c. restorer.

→ The clamping n/w has circuit components like a diode, a capacitor & a resistor.

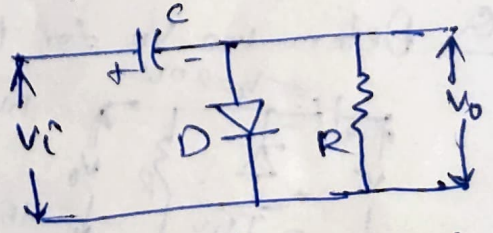The time const. for the chkt  $T = RC$  must be large so that the voltage across the capacitor does not discharge significantly when diode is not conducting.










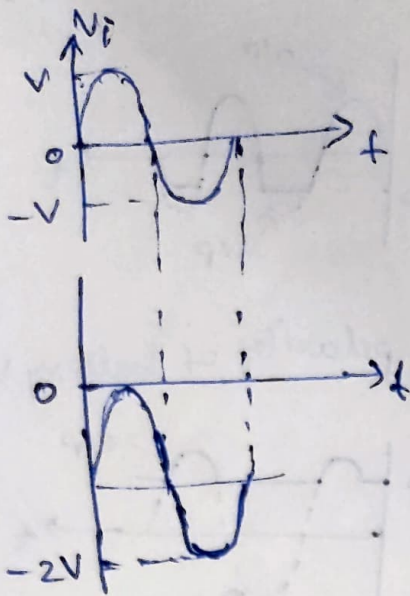


→ During +ve half cycle, the diode conducts, i.e. it acts like a short ckt.  
 → The capacitor charges to V volts. During this interval, the o/p voltage  $V_o = 0V$   
 → During -ve half cycle, the diode is open. The o/p voltage is found by applying KVL  
 $-V - V - V_o = 0$   
 $\Rightarrow V_o = -2V$

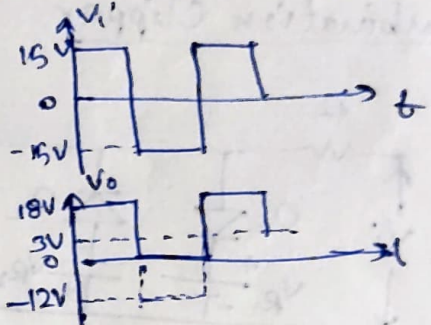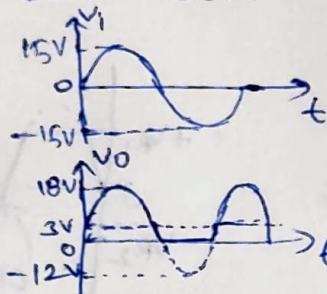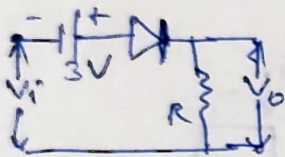Q → Determine the o/p waveform for the i/p sinusoidal & square wave forms. Assume the diode is ideal.



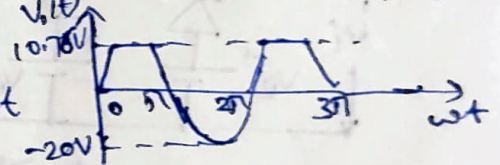
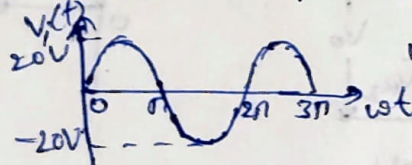
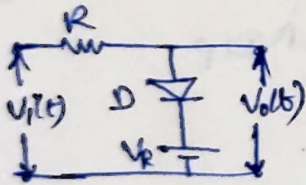
Q → In the diode positive peak limiting ckt,  $V_R = 10V$ ,  $V_i(t) = 20\sin 2\pi ft$  & the diode forward resistance  $R_f = 100\Omega$  while  $R_r = \infty$  &  $V_f = 0$ . Neglect all capacitances in the ckt. Draw the i/p & o/p waveform if  $R = 1.2k\Omega$



$$V_o(t) = (V_i(t) - V_R) \frac{R_f}{R_f + R_r}$$

$$V_o(t)_{\text{max}} = \frac{10 \times 100}{100 + 1200} + 10 = \frac{10}{13} + 10 = 10.76V$$

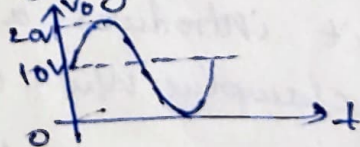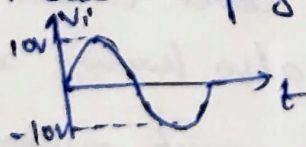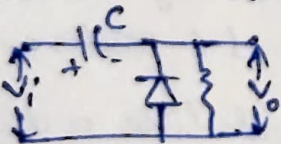Q → Determine  $V_o$  for the clamping ckt for given sinusoidal i/p signal



Q → Determine  $V_o$  for the u/w

