

For Ge diode, the reverse saturation current is 2 mA at a reverse voltage of 0.26 V. Calculate forward & reverse dynamic resistance values if forward biased voltage is also 0.26 V at room temp.

$$n = 1$$

$$I_0 = 2 \text{ mA}$$

$$V = 0.26 \text{ V for forward biased}$$

$$= -0.26 \text{ V for reverse biased}$$

$$V_T = 26 \text{ mV at room temp.}$$

$$\text{Forward dynamic resistance } r_f = \frac{n V_T}{I_0 e^{V/T}} = 0.591 \Omega$$

$$\text{Reverse dynamic resistance } r_r = \frac{n V_T}{I_0 e^{-V/T}} = 286.34 \Omega$$

The reverse saturation current of a Ge diode is 100 mA at room temp. of 27°C. Calculate the current in forward biased condition if forward bias voltage is 0.2 V at room temp. If temp. is increased by 20°C, calculate the reverse saturation current & forward current, for same forward voltage, at new temp.

$$\text{At } T_1 = 27^\circ\text{C} = 300^\circ\text{K}, V_T = 26 \text{ mV}$$

$$(I_0)_1 = 100 \text{ mA}, N = 0.2 \text{ V}$$

$$I = I_0 (e^{V/T} - 1) = 100 \times 10^{-6} [e^{0.2/260} - 1] \\ = 219.04 \text{ mA}$$

$$(I_0)_2 = 2^{\frac{T_2 - T_1}{10}} \times (I_0)_1$$

$$= 2^{20/10} \times (I_0)_1 = 4 \times 100 = 400 \text{ mA}$$

$$\text{At } T_2 = 27 + 20 = 47^\circ\text{C} = 320^\circ\text{K}, (I_0)_2 = 400 \text{ mA}, V = 0.2 \text{ V}$$

$$V_T = \frac{26}{320} = 8.125 \times 10^{-5} \times 320 = 27.584 \text{ mV}$$

$$I = I_0 (e^{V/T} - 1) = 400 \times 10^{-6} [e^{0.2/27.584} - 1] \\ = 563.138 \text{ mA}$$

A Ge diode has a contact potential of 0.2 V, while the concentration of acceptor impurity atoms is $3 \times 10^{20}/\text{m}^3$, calculate for a reverse bias of 0.1 V, the width of depletion region. If the reverse bias is increased to 10 V, calculate the new width of depletion region. Assuming cross-sectional area of junction as 1 mm^2 calculate the transition capacitance value for both the cases. Assume ϵ_r as 16 for Ge.

$$N_A = 3 \times 10^{20}/\text{m}^3 \quad A = 1 \text{ mm}^2 = 10^{-6} \text{ m}^2 \quad \epsilon_r = 16 \text{ for Ge}$$

$$V_0 = 0.2 \text{ V}$$

$$\text{i)} \quad V = -0.1 \text{ V} \quad V_B = V_0 - V = 0.2 - (-0.1) = 0.3 \text{ V}$$

$$V_B = \frac{1}{2} \frac{e N_A W^2}{\epsilon}$$

$$\epsilon = \epsilon_0 \epsilon_r = 8.854 \times 10^{-12} \times 16$$

Q) The Hall effect experiment is used for a silicon bar known to be p-type. The resistivity of the bar is $220 \times 10^3 \Omega\text{-cm}$. The width of the bar is 2 mm & distance b/w the 2 surfaces of the bar is 2.2 mm. The magnetic field used has an intensity of 0.1 Wb/m². If measured values of current & Hall voltage are 5 mA & 28 mV respectively. Calculate the mobility of holes.

$$\rho = 220 \times 10^3 \Omega\text{-cm} = 220 \Omega\text{-m}$$

$$w = 2 \text{ mm} = 2 \times 10^{-3} \text{ m}$$

$$B = 0.1 \text{ Wb/m}^2$$

$$I = 5 \text{ mA}$$

$$V_H = 28 \text{ mV}$$

$$M = \sigma R_H \quad \text{where } R_H = \frac{V_H w}{BI}$$

$$= \frac{1}{\rho} \frac{V_H w}{BI} = \frac{1}{2200} \times \frac{28 \times 10^{-3}}{0.1 \times 5 \times 10^{-3}}$$

$$= 0.05091 \text{ m}^2/\text{V-s} = 50.91 \text{ cm}^2/\text{V-s}$$

Q) A silicon diode has a reverse saturation current of 7.12 nA at room temp. of 27°C. Calculate its forward current if it is forward biased with a voltage of 0.7 V

$$I_0 = 7.12 \text{ nA} = 7.12 \times 10^{-9} \text{ A}$$

$$V = 0.7 \text{ V}$$

$$T = 27^\circ\text{C} = 27 + 273 = 300^\circ\text{K}, N_T = 26 \text{ mV}$$

$$\eta = 2 \text{ for Si}$$

$$I = I_0 (e^{V/\eta N_T} - 1) = 7.12 \times 10^{-9} [e^{0.7/2 \times 0.026} - 1]$$

$$= 4.99 \times 10^{-3} \approx 5 \text{ mA}$$

Q) A Ge diode has a reverse saturation current of 3 mA. Calculate the forward bias voltage at the room temp. of 27°C if 1% of rated current is flowing through the forward biased diode. The diode forward rated current is 1 A

$$I_0 = 3 \text{ mA}$$

$$I_{\text{rated}} = 1 \text{ A}$$

$$T = 27^\circ\text{C} = 300^\circ\text{K}$$

$$I = 1\% \text{ of } I_{\text{rated}}$$

$$\eta = 1$$

$$= 0.01 \text{ A}$$

$$N_T = 26 \text{ mV}$$

$$I = I_0 (e^{V/\eta N_T} - 1)$$

$$\Rightarrow 0.01 = 3 \times 10^{-6} [e^{V/1 \times 0.026} - 1]$$

$$\Rightarrow e^{V/0.026} = 3334.3333$$

$$\Rightarrow \frac{V}{0.026} = \ln [3334.3333] = 8.112$$

$$\Rightarrow V = 0.2109 \text{ V}$$

Q) A certain zener diode exhibits a 50mV change in V_Z for a 2.5mA change in I_Z . What is zener resistance?

$$R_Z = \frac{\Delta V_Z}{\Delta I_Z} = \frac{50 \text{ mV}}{2.5 \text{ mA}} = 20 \Omega$$

Q) A diode whose internal resistance is 20Ω is to supply power to a $1 \text{k}\Omega$ load from a 110V (rms) source of supply. Calculate (a) peak load current (b) dc load current (c) ac load current (d) dc diode voltage (e) total i/p power to the circuit (f) peak inverse voltage (g) percentage regulation from no load to full load

$$V_m = \sqrt{2} \times 110 \text{ V} = 155.56 \text{ V}$$

$$(a) I_{\text{m}} = \frac{V_m}{R_f + R_L} = \frac{155.56}{1020} = 152.5 \text{ mA}$$

$$(b) I_{\text{dc}} = \frac{I_{\text{m}}}{\pi} = 48.54 \text{ mA}$$

$$(c) I_{\text{rms}} = \frac{I_{\text{m}}}{2} = 76.25 \text{ mA}$$

$$(d) V_{\text{dc}} = -\frac{I_{\text{m}} R_L}{\pi} = -I_{\text{dc}} R_L = -48.54 \text{ V}$$

$$(e) P_i = I_{\text{rms}}^2 (R_f + R_L) = 5.33 \text{ W}$$

$$(f) PIV = V_m = 155.56 \text{ V}$$

$$(g) V_{\text{no load}} = \frac{V_m}{\pi} = 49.51 \text{ V}$$

$$V_{\text{full load}} = \frac{V_m}{\pi} - I_{\text{dc}} R_f = 48.54 \text{ V}$$

$$\% \text{ regulation} = \frac{V_{\text{no load}} - V_{\text{full load}}}{V_{\text{full load}}} \times 100 = 1.94\%$$

Q) A half-wave rectifier circuit is supplied from a 230V, 50Hz supply with a step down ratio of 3:1 to a resistive load of $10 \text{k}\Omega$. The diode forward resistance is 75Ω while transformer secondary resistance is 10Ω . Calculate mean, average, rms values of current, DC o/p voltage, efficiency of rectification & ripple factor.

$$R_f = 75 \Omega \quad R = 10 \text{k}\Omega \quad R_s = 10 \Omega$$

Rectifier Efficiency

$$\eta = \frac{\text{dc o/p power}}{\text{ac i/p power}} = \frac{P_{\text{dc}}}{P_{\text{ac}}}$$

$$\eta = \frac{I_{\text{dc}} V_{\text{dc}}}{I_{\text{rms}}^2 (R_f + R_L)} = \frac{I_{\text{dc}}^2 R_L}{I_{\text{rms}}^2 (R_f + R_L)}$$

$$= \frac{I_{\text{dc}}^2 R_L}{I_{\text{rms}}^2 (R_f + R_L) \cdot \frac{1}{4}}$$

$$= \frac{4/\pi^2}{1 + \frac{R_f}{R_L}}$$

$$\text{Since } R_f \ll R_L, \eta = 0.406$$

$$\therefore \eta = 40.6 \text{ for half wave rectifiers}$$

$$\frac{N_1}{N_2} = \frac{3}{1} \Rightarrow \frac{N_2}{N_1} = \frac{1}{3} = \frac{V_s (\text{r.m.s})}{V_p (\text{r.m.s})}$$

$$\Rightarrow \frac{1}{3} = \frac{V_i (\text{r.m.s})}{230} \Rightarrow V_i (\text{r.m.s}) = 76.667 \text{ V}$$

Transformer Utilization Factor (TUF)
The factor which indicates how much is the utilization of transformer in the set

$$V_m = \sqrt{2} V_i (\text{r.m.s}) = 108.423 \text{ V}$$

$$I_m = \frac{V_m}{R_f + R_s + R_L} = 10.75 \text{ mA}$$

$$I_{dc} = \frac{I_m}{\pi} = 3.422 \text{ mA}$$

$$I_{rms} = \frac{I_m}{2} = 5.375 \text{ mA}$$

$$V_{dc} = I_{dc} R_L = 34.122 \text{ V}$$

$$P_{dc} = V_{dc} I_{dc} = 0.1171 \text{ W}$$

$$P_{ac} = I_{rms}^2 (R_f + R_s + R_L) = 0.2913 \text{ W}$$

$$\% \eta = \frac{P_{dc}}{P_{ac}} \times 100 = 40.19 \%$$

$$\gamma = \sqrt{\left(\frac{I_{rms}}{I_{dc}}\right)^2 - 1} = 1.21$$

TUF = DC power delivered to load / AC power rating of transformer

$$= \frac{V_{dc} I_{dc}}{V_{rms} I_{rms}}$$

$$= \frac{I_{dc} R_L}{I_{rms} R_L}$$


$$= \frac{I_{dc} R_L}{I_{rms} R_L}$$

$$= \frac{I_{dc}^2 R_L}{V_m \cdot I_m}$$

$$= \frac{(I_m/\pi)^2 R_L}{\frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{2}}$$

$$= \frac{252}{\pi^2 (1+R_f/R_L)}$$

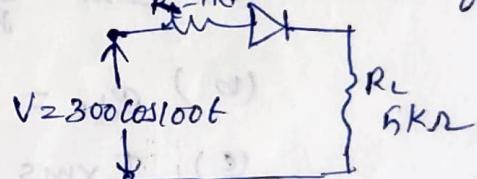if $R_f \ll R_L$, then
 $\text{TUF} = \frac{2\sqrt{2}}{\pi^2} = 0.287$
 for full wave rectifiers



A half wave rectifier with $R_L = 5KR$ is given with an input of 10 V peak from stepdown transformer. Calculate DC voltage & load current for ideal & silicon diode $V = 300 \cos 100t$.
 The rectifier may be represented by ideal diode in series with a resistance of 1 KR. Calculate (i) I_m , (ii) DC Power, (iii) AC power, (iv) Rectifier efficiency & (v) Ripple factor.

$$V = V_m \sin \omega t$$

$$(i) I_m = \frac{V_m}{R + R_L} \quad . \quad V_m = 300 \quad \omega = 100$$

$$> \frac{300}{6K} = 50 \text{ mA}$$

$$(ii) P_{dc} = I_{dc}^2 R_L$$

$$= \frac{I_m^2}{4} (R + R_L)$$

$$= 3.75 \text{ W}$$

$$(iii) I_{dc} = \frac{I_m}{\pi} = 15.915 \text{ mA}$$

$$(iv) \% \eta = \frac{P_{dc}}{P_{ac}} \times 100 = 33.77\%$$

$$(v) \gamma = \sqrt{\left(\frac{I_{rms}}{I_{dc}}\right)^2 - 1} = 1.21$$

TUF for FW Rectifiers

$$= \frac{P_{dc}^2 R_L}{V_{rms} I_{rms}} = \frac{\left(\frac{P_{dc}}{V_{rms}}\right)^2 R_L}{\frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{2}} = \frac{8}{\pi^2} = 0.812$$

TUF of secondary = DC power to load / AC power rating of secondary

$$\text{TUF of primary} = 2 \times \text{TUF of HW Rectifiers} = 2 \times 0.287 = 0.574$$

$$\text{Average TUF of FW rectifiers} = \frac{\text{TUF of primary} + \text{TUF of secondary}}{2} = 0.693$$

A full-wave rectifier ckt is fed from a transformer having a center-tapped secondary winding. The rms voltage from either end of secondary to center tap is 30V. If the diode forward resistance is 2Ω & that of half secondary is 8Ω , for a load of $1k\Omega$. Calculate.

- power delivered to load
- % regulation at full load
- efficiency of rectification
- TUF of secondary

$$V_{rms} = 30V \quad R_f = 2\Omega \quad R_s = 8\Omega \quad R_L = 1k\Omega$$

$$V_m = 30\sqrt{2} = 42.426V$$

$$I_m = \frac{V_m}{R_f + R_s + R_L} = 42mA$$

$$I_{dc} = \frac{2I_m}{\pi} = 26.74mA$$

$$a) \text{Power delivered to load} = I_{dc}^2 R_L = 0.715W$$

$$b) V_{dc \text{ at no load}} = V_{NL} = \frac{2V_m}{\pi} = 27V$$

$$V_{dc \text{ at full load}} = V_{FL} = I_{dc} R_L = 26.74V$$

$$\% \text{ regulation} = \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100 = 0.97\%$$

$$c) \text{Efficiency of rectification} \eta = \frac{P_{dc}}{P_{ac}} \times 100$$

d) transformer secondary rating

$$\approx V_{rms} I_{rms} = 0.89W$$

$$= \frac{8}{\pi^2} \left(\frac{R_f + R_s}{R_L} \right)$$

$$TUF = \frac{P_{dc}}{\text{ac rating}} = 0.902$$

$$= 80.2\%$$

For a full-wave rectifier shown below is a sinusoidal voltage. If the maximum allowable average d.c. current in each diode is 1A, calculate the maximum allowable peak-to-peak value of V. Assume two diodes to be identical & neglect diode



$$(I_{dc})_{max} = 1A = \frac{I_m}{2}$$

in the diode

$$= \frac{I_m}{2} = \frac{N_m}{\pi R_L} \text{ as } R_f = 0$$

$$1 = \frac{V_m}{\pi R_L} \Rightarrow V_m = \pi R_L = \pi \times 100 = 314.16V$$
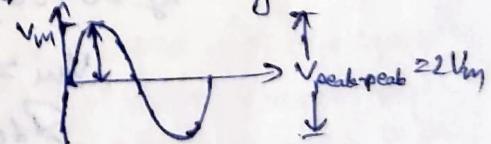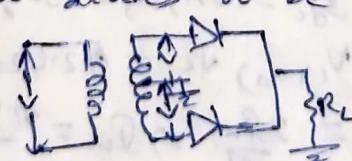
$$V_{peak-to-peak} = 2V_{max} = 628.32V$$



What is the necessary AC i/p power from the transformer secondary used in a half-wave rectifier to deliver 500W of DC power to the load? What would be the AC i/p power for the same load in a full-wave rectifier?

$$P_{dc} = 500W \rightarrow \gamma, n = 40.6\% \text{ for KWR}$$

$$40.6 = \frac{P_{dc}}{P_{ac}} \times 100 \Rightarrow P_{ac} = 1231.627W$$

$$P_{dc} = 500W, \gamma, n = 81.2\%, \text{ for FWR}$$

$$81.2 = \frac{P_{dc}}{P_{ac}} \times 100 \Rightarrow P_{ac} = 615.76355W$$

~~Q.~~ A full wave rectifier uses a diode with forward resistance of 1Ω . The transformer secondary is centre tapped with $10 - 0 - 10V_{rms}$ & has resistance of 5Ω for each half section. Calculate (i) No-load dc voltage (ii) DC op voltage at $100mA$ (iii) % Regulation at $100mA$

$$R_f = 1\Omega, V_{rms} = 10V, R_s = 5\Omega$$

$$V_m = \sqrt{2}V_{rms} = 14.1421V$$

$$(i) V_{dc(NL)} = \frac{2V_m}{\pi} = 9.0031V$$

$$(ii) I_{dc} = 100mA = \frac{2I_m}{\pi}$$

$$I_m = \frac{\pi \times 100mA}{2} = 157.079mA$$

$$I_m = 157.079 \times 10^{-3} = \frac{V_m}{R_f + R_s + R_L} = \frac{14.1421}{1 + R + R_L}$$

$$\Rightarrow R_L = 84.0317\Omega$$

$$V_{dc(FL)} = I_{dc} \cdot R_L = 8.4031V$$

$$(iii) \% \text{ Regulation} = \frac{V_{dc(NL)} - V_{dc(FL)}}{V_{dc(FL)}} \times 100 = 7.14\%$$

~~Q.~~ The 4 semiconductor diodes used in a bridge rectifier, all each having a forward resistance of 0.1Ω & infinite reverse resistance, feed a dc current of $10A$ to a resistive load from a sinusoidally varying alternating supply of $30V$ (rms). Determine the resistance of load & efficiency of circuit

$$R_f = 0.1\Omega, I_{dc} = 10A, R_s = 0\Omega, V_{rms} = 30V$$

$$V_m = V_{rms} \sqrt{2} = 42.4264V$$

$$I_{dc} = \frac{2I_m}{\pi} \Rightarrow I_m = \frac{\pi I_{dc}}{2} = 15.7079A$$

$$I_m = \frac{V_m}{2R_f + R_s + R_L} \Rightarrow R_L = 2.5\Omega$$

$$P_{dc} = I_{dc}^2 R_L = 250W$$

$$P_{ac} = I_m^2 (2R_f + R_s + R_L)$$

$$= \frac{I_m^2}{2} (2R_f + R_s + R_L)$$

$$\% \eta = \frac{P_{dc}}{P_{ac}} \times 100 = 75.06\% = \cancel{33.092W}$$

$$V_{in} = 162 \text{ V}, L = 1000 \text{ mH}, R_s = 100 \Omega, C = 50 \mu\text{F}, R_L = 1 \text{ k}\Omega$$

$$V_{dc(in)} = \text{Op dc voltage to filter}$$

$$= \frac{2V_{in}}{\pi} = 103.132 \text{ V}$$

$$V_{dc(out)} = \frac{V_{dc(in)}}{1 + \frac{R}{R_L}} = 93.7667 \text{ V} = \frac{2V_{in}}{\pi} - \frac{R_s R}{R_L}$$

$$\gamma_2 = \frac{V_2}{B} \times 200 \times \frac{1}{2\pi f} = \frac{1}{6\sqrt{2} \omega L C} \left(\frac{1 + R}{R_L} \right)$$

$$\approx 0.02626 \approx 2.6\%$$


Q Calculate the ripple factors for a π -type filter employing 10H choke & two equal capacitors 16 uF each & fed from a full wave rectifiers & 50Hz mains. The load resistance

$$C_1 = C_2 = 16 \mu\text{F} \quad L = 10 \text{ H} \quad R_L = 4 \text{ k}\Omega \quad f = 50 \text{ Hz}$$

$$\frac{E \times C_1 \times C_2}{R_L} = \sqrt{2} = \frac{\sqrt{2}}{8 \omega^2 L C_1 C_2 R_L} = 1.56 \times 10^{-4}$$

Q Determine minimum & max load currents for which the zener diode will maintain regulation. What's the min. R_L that can be used? $V_Z = 10 \text{ V}$ $I_{Zmin} = 5 \text{ mA}$ & $I_{Zmax} = 80 \text{ mA}$

Assume $\gamma_2 = 20 \Omega$

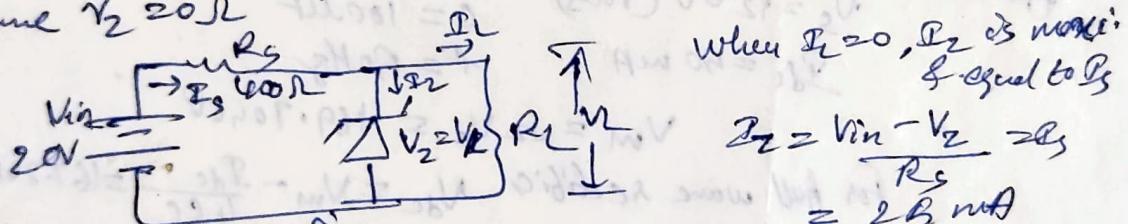

Since I_2 is in range ($I_{Zmin} - I_{Zmax}$) $R_L = 2 \Omega$

$$\therefore I_{Zmin} = 0 \text{ A}$$

$$I_{Zmax} = I_S - I_{Zmin} = 25 \text{ mA} - 5 \text{ mA} = 20 \text{ mA}$$


$$R_{Zmin} = \frac{V_Z}{I_{Zmin}} = 500 \Omega$$

Q In a zener regulator, the op dc is $10 \text{ V} \pm 20\%$. The op requirements are $5 \text{ V}, 20 \text{ mA}$. Assuming I_{Zmin} & I_{Zmax} as 5 mA & 80 mA . Design the zener regulator.

$$V_o = 5 \text{ V} \quad I_L = 20 \text{ mA} \quad R_L = \frac{V_o}{I_L} = 250 \Omega$$

$$I_{Zmin} = 5 \text{ mA}$$

$$I_{Zmax} = 80 \text{ mA}$$

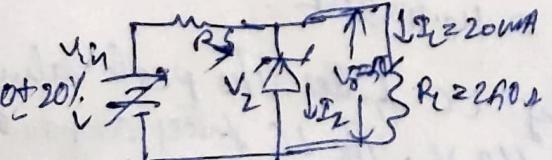

$$V_{in min} = 10 + 0.2 \times 10 = 8 \text{ V}$$

$$V_{in max} = 10 + 0.2 \times 10 = 12 \text{ V}$$

$$I_{Lmax} = I_{Zmin} = 20 \text{ mA}$$

$$R_{Zmax} = \frac{V_{in max} - V_o}{I_{Lmax} + I_{Zmin}} = 120 \Omega$$

$$R_{Zmin} = \frac{V_{in min} - V_o}{I_L + I_{Zmin}} = 70 \Omega$$