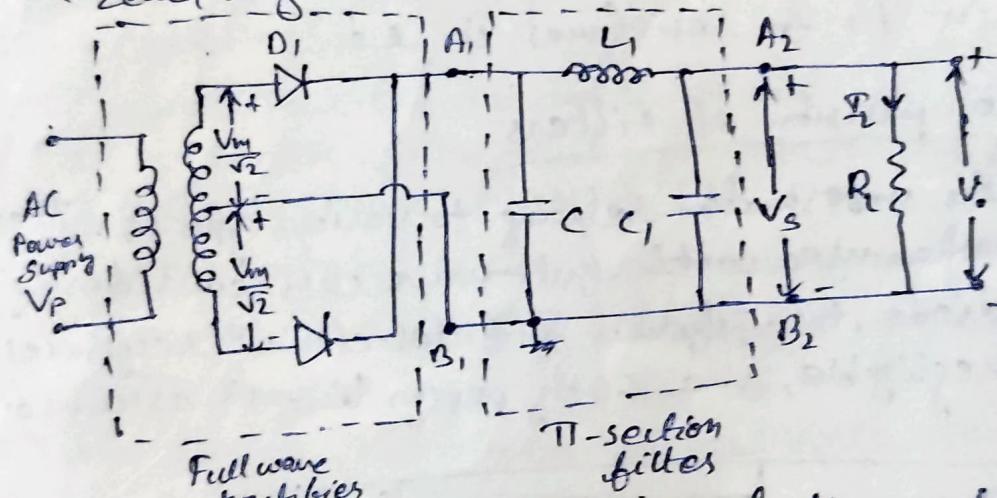


## Voltage Regulation Using Zener Diode

- Zener diodes are specially designed p-n junction diodes with adequate power dissipation capabilities to operate in the breakdown region which are employed as voltage reference or const. voltage devices in the electronic devices or sets.
- A zener diode maintains nearly a const. voltage across its terminals in the breakdown region irrespective of current flowing through the diode.
- This property of zener diodes is used to minimize the voltage fluctuations of a dc power supply obtained by the rectifiers-filter combination.
- So zener diode is sometimes called a voltage regulator diode & the diode circuit in which the zener diodes are used as voltage regulators is called a Zener Voltage regulator or simply a Zener regulator.




- Consider the circuit that consists of a full-wave rectifier followed by a  $\Pi$ -section filter whose o/p is applied to the load resistance  $R_L$ .
- for  $R_L = \infty$  (i.e. under open loop condition), no current flows through the load (i.e.  $I_L = 0$ ) & the dc voltage of the filter o/p is  $V_s = V_m$
- For any finite value of  $R_L$ , a dc current must flow through  $R_L$  & hence  $I_L \neq 0$ .
- Under this condition, discharging will take place through the load resistance & o/p voltage across the load becomes  $V_o = V_m - \frac{I_L}{4fC}$


where  $f$  is the power line freq.  
 $V_m$  is the peak of transformer's secondary co.r.t  
the counter tap ~~at~~

$C$  is the capacitor

- Suppose that  $R_L$  represents the i/p impedance of an instrument which works satisfactorily if a const. dc voltage  $V_L$  is applied across it which results in a const. dc voltage current  $I_L$  (i.e.  $I_L = \frac{V_L}{R_L}$ )
- So we maintain  $V_L = V_0 = V_m - \frac{T_L}{4fC}$  as const.
- for the desired value of  $I_L$  by varying the values of  $V_m$ ,  $C$ , &  $f$ , the instrument must work satisfactorily.
- We can easily choose the desired value of  $C$  which remains const. for all the time.
- Since  $f$  is the power line freq., it is a const. parameter for all the time.
- $V_m$  may not be const. to the desired value for all the time since it depends on the i/p voltage  $V_p$  of the power line to the transformer primary winding.
- Consider a transformer with  $N_1$  &  $N_2$  as the no. of turns in the primary & secondary windings respectively.
- Let  $V_p$  be the rms voltage of the ac power line which is applied to transformer primary, then the total rms voltage of transformer secondary is  $(\frac{N_2}{N_1}) V_p$  which is equal to  $\frac{2V_m}{\sqrt{2}}$  where  $2V_m$  is the peak value of the total transformer secondary voltage.
- Thus the peak voltage is  $V_m = (\frac{N_2}{N_1}) \frac{V_p}{\sqrt{2}}$
- Since the power line voltage  $V_p$  may fluctuate from its desired value to a no. of uncontrollable reasons, there always exists a possibility of fluctuation in  $V_m$ .
- Therefore the circuit does not guarantee that the desired instrument will operate satisfactorily for all the time.

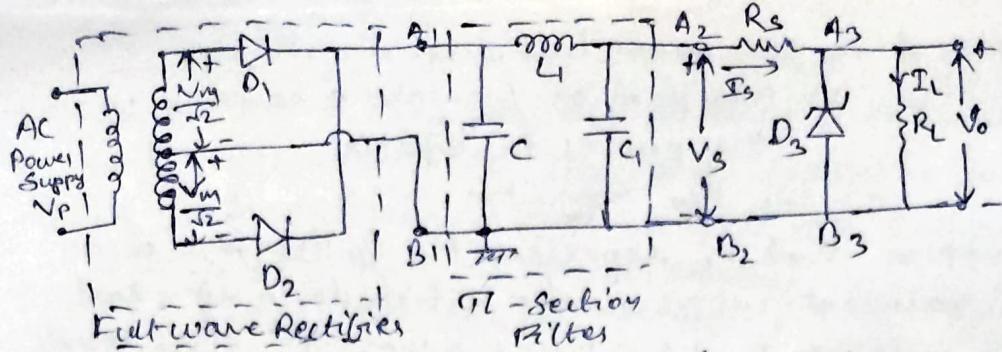

- The difficulties of the previous ckt can be removed by connecting a Zener diode  $D_3$  with breakdown voltage  $V_Z$  & a series resistance  $R_s$ .
- Suppose that  $V_m$  varies b/w  $V_{s\min}$  &  $V_{s\max}$  corresponding to the min. & max. limits of the power line voltage applied to the primary winding of the transformer.
- So  $V_{s\min} \leq V_s \leq V_{s\max}$  i.e. the dc voltage variation in the filter o/p.
- If the breakdown  $V_Z$  is chosen to be equal to the desired voltage  $V_L$  across the instrument with load impedance  $R_L$  such that  $V_{s\min} > V_Z = V_L$ , the filter o/p voltage  $V_s$  reverse biases the zener diode for all the time & hence the diode must operate in breakdown region.
- Under this condition, Zener diode behaves as a battery

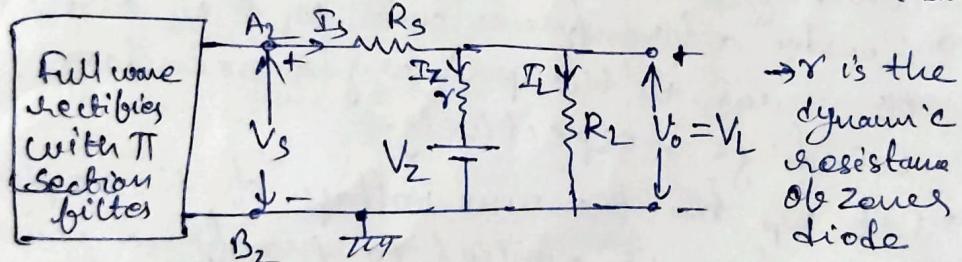

- Let  $I_L$ ,  $I_S$  &  $I_Z$  be the current passing through  $R_L$ ,  $R_s$  & Zener diode respectively.
- The current flowing through load resistance is  $I_L = \frac{V_L}{R_L}$  where  $V_L = V_Z + r I_Z$  — (1)
- provided that zener diode is operated in breakdown region.
- The current flowing through the series resistance  $R_s$  is  $I_S = \frac{V_s - V_L}{R_s}$
- Since  $I_S = I_Z + I_L$ , the Zener current is given by  $I_Z = I_S - I_L = \left(\frac{V_s - V_L}{R_s}\right) - \frac{V_L}{R_L}$  — (2)

$$\rightarrow \text{From } ① \text{ & } ② \quad I_Z = \frac{\left(\frac{V_S - V_Z}{R_S}\right) - \frac{V_Z}{R_L}}{1 + \left(\frac{V_Z}{R_S} + \frac{V_Z}{R_L}\right)}$$

$\rightarrow$  In most of practical circuits,  $V_Z < R_S + R_L$  & hence  
 $1 + \left(\frac{V_Z}{R_S} + \frac{V_Z}{R_L}\right) \approx 1$

$\rightarrow$  Thus the Zener current can approximately be given by  
 $I_Z \approx \left(\frac{V_S - V_Z}{R_S}\right) - \frac{V_Z}{R_L}$

$\rightarrow$  When the effect of  $r$  is neglected,  $V_t \approx V_Z$  which is normally considered in most of the practical cases for designing of Zener diode circuits.

$\rightarrow$  If there is any fluctuation in  $V_S$  due to fluctuation in the power line voltage, the Zener current  $I_Z$  is changed accordingly, whereas the load current  $I_L$  & series current  $I_S$  are unchanged.

$\rightarrow$  Determination of Breakdown Region of Operation of the Zener Diode

$\hookrightarrow I_L = \frac{V_L}{R_L}$  &  $I_Z \approx \left(\frac{V_S - V_Z}{R_S}\right) - \frac{V_Z}{R_L}$  are valid

provided that the Zener diode is operated in the breakdown region.

$\rightarrow$  To ensure the breakdown condition of the diode, we can consider the following two cases:

case-I: Fixed  $V_S$  & Variable  $R_L$

$\rightarrow$  When the diode is in breakdown region  $V_L \approx V_Z$

$\rightarrow$  If the load resistance  $R_L$  is less than a certain value  $R_{L\min}$ , the voltage  $V_L = I_L R_{L\min}$  across the load resistance may become less than  $V_Z$  which implies that diode is not in its operating region.

$\rightarrow$  Considers the extreme case when  $R_L \rightarrow 0$  (i.e. nearly short-circuited) which results  $V_L \rightarrow 0$  & hence diode has no control over the load voltage.

→ Thus, in order to maintain a const. voltage  $V_L$  across the load resistor for different values of  $R_L$ , we must have to maintain a minimum value  $R_{L\min}$  of load resistance to ensure that Zener diode operates in breakdown region.

→ The Th却en voltage facing the zener diode, say  $V_{TH}$ , is the voltage that appears b/w the diode terminals  $A_3 \& B_3$  when diode is removed from the ckt.

$$I_L = I_S = \frac{V_S}{R_L + R_S} \text{ when diode is open-circuited.}$$

→ Thus voltage  $V_{TH}$  b/w  $A_3 \& B_3$  is basically the voltage dropped across  $R_L$

$$V_{TH} = I_L R_L = \frac{R_L V_S}{R_L + R_S}$$

→ Diode will be in breakdown region only when  $V_{TH} \geq V_Z$ , thus we can write the breakdown condition of diode as

$$\frac{R_L V_S}{R_L + R_S} \geq V_Z$$

$$\Rightarrow R_L \geq \frac{R_S V_Z}{V_S - V_Z} = R_{L\min}$$

$$\text{where } R_{L\min} = \frac{R_S V_Z}{V_S - V_Z}$$

→ For  $V_L \approx V_Z$ ,  $\frac{V_L}{R_L} = \frac{V_L}{R_L}$  implies that the increase in  $R_L$  will result in the decrease in load current & vice-versa

$$I_L \leq \frac{V_Z}{R_{L\min}} = \frac{V_S - V_Z}{R_S} = I_{Z\max}$$

where  $I_{Z\max}$  represents the max. Zener current corresponding to the min. value of load resistance  $R_{L\min}$ .

→ At  $I_L = I_{Z\max}$ ,  $I_Z = I_S - I_{Z\max} = 0$  which represents the minimum value  ~~$\approx \left(\frac{V_S - V_Z}{R_S}\right) R_S$~~  of the load resistance  $R_{L\min}$ .  ~~$\approx \left(\frac{V_S - V_Z}{R_S}\right) R_S$~~  from Zener current  $I_{Z\max}$  gives the min. value of the load current  $I_L = I_{Z\max}$  (say) which can be written as  $I_{L\min} = I_S - I_{Z\max}$

$$\rightarrow I_{L\min} = \left( \frac{V_s - V_z}{R_s} \right) - I_{Z\max}$$

- The min. value of  $R_L$  should be such that  $I_{L\min} \leq I_L \leq I_{L\max}$
- Since  $V_L = V_z$  is const. in the breakdown region of diode,  $I_{L\min}$  will correspond to the max. possible value of load resistance which is defined as

$$R_{L\max} = \frac{V_z}{I_{L\min}}$$

### Case-II: Fixed $R_L$ and Variable $V_s$

→ When no load dc voltage obtained by using a suitable rectifier-filter combination is fluctuating due to the fluctuation in the line voltage or some other reasons whereas the load resistance is const.

→ Using the condition  $V_{TH} \geq V_z$ .

$$\frac{R_s V_s}{R_L + R_s} \geq V_z$$

$$\Rightarrow V_s \geq \left( \frac{R_s + R_L}{R_L} \right) V_z = V_{s\min}$$

where  $V_{s\min} = \left( \frac{R_s + R_L}{R_L} \right) V_z$  is minimum dc voltage required to turn on Zener diode into the breakdown region.

→ For  $V_s \geq V_{s\min}$ , the increase in  $V_s$  will result in increase in Zener current  $I_z$  since  $P_L$  is const.

→ This implies that the non-clipping value  $V_{s\max}$  (say) of  $V_s$  for which Zener diode will work satisfactorily can be obtained using the calculation for which Zener current is max., i.e.  $I_z = I_{z\max}$

→ Since  $P_L$  is const., the max. Zener current will result in max. value of  $I_s$  flowing through the series resistance  $R_s$  which is defined by

$$I_{s\max} = I_{z\max} + I_L$$

For  $\gamma \approx 0$ ,  $V_s = V_{s\max}$  &  $I_s = I_{s\max}$

$$V_{s\max} = R_s I_{s\max} + V_z$$

→ The load current remains const. at  $\frac{V_s}{R_L}$  for all the values of  $V_s$  since  $R_L$  is const.