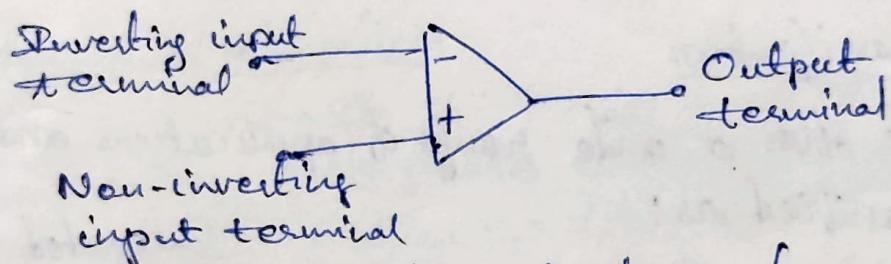


## Operational Amplifiers

- Linear integrated circuits are being used in a number of electronic applications such as in fields like audio, and radio communications, medical electronics, instrumentation control, etc.
- An important linear IC is operational amplifiers
- The operational amplifiers (commonly referred to as op-amp) is a multi-terminal device which internally is quite complex.
- The circuit schematic of an op-amp is a triangle



- It has two input terminals and one output terminal
- The terminal with a (-) sign is called inverting input terminal and the terminal with (+) sign is called the non-inverting input terminal.
- There are three popular packages available:
  - 1) The metal can (TO) package
  - 2) The dual-in-line package (DIP)
  - 3) The flat package or flat pack
- Op-amps have five basic terminals, i.e.; 2 ip terminals, 1 op terminal and 2 power supply terminals
- The  $V^+$  and  $V^-$  power supply terminals are connected to the 2 dc voltage sources.


- A number of manufacturers also produce popular ICs of the other manufacturers.
- For example, Fairchild's original 741 is also manufactured by other manufacturers as follows:
 

1) National Semiconductors	LM741
2) Motorola	MC1741
3) RCA	CA3741
4) Texas Instruments	SN52741
5) Signetics	N5741

→ Some linear ICs are available in different classes such as A, C, E, S and SC. The main difference of these op-amps are:

- 741 Military grade op-amp  
(Operating temperature range  $-55^{\circ}\text{C}$  to  $125^{\circ}\text{C}$ )
- 741C Commercial grade op-amp  
(Operating temperature range  $0^{\circ}$  to  $70^{\circ}/75^{\circ}\text{C}$ )
- 741A Improved version of 741 { Better electrical
- 741E Improved version of 741C } specifications
- 741S Military grade op-amps with higher slew-rate
- 741SC Commercial grade op-amps with higher slew-rate

### The Ideal Operational Amplifiers

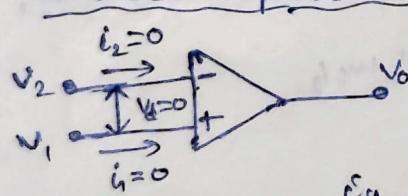

→ If  $V_1 = 0$ , o/p  $V_0$  is  $180^{\circ}$  out of phase with i/p signal  $V_2$

→ When  $V_2 = 0$ , o/p  $V_0$  will be in phase with i/p signal applied at  $V_1$ .

→ This op-amp is said to be ideal if it has the following characteristics.

Open loop voltage gain,  $A_{OL} = \infty$

Input impedance,  $R_i = \infty$


Output impedance,  $R_o = 0$

Bandwidth,  $BW = \infty$

Zero offset, i.e.,  $V_0 \neq 0$  when  $V_1 = V_2 = 0$

→ The above properties can never be realized in practice.

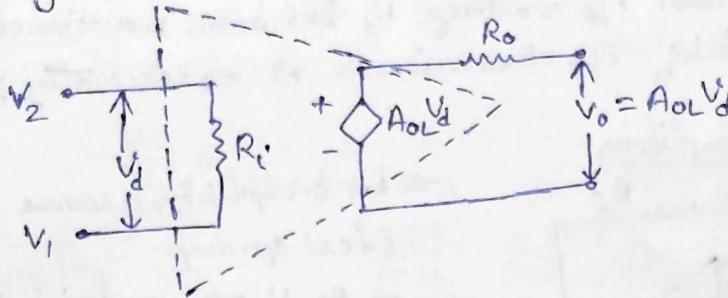→ A physical amplifier is not an ideal one



→ So the equivalent circuit of an op-amp may be shown as above, where  $A_{OL} \neq \infty$ ,  $R_i \neq \infty$ , and  $R_o \neq 0$


→ It can be seen that op-amp is a voltage controlled voltage source and  $A_{OL}V_d$  is an equivalent Thvenin voltage source and  $R_o$  is the Thvenin equivalent resistance looking back into the off terminal of an op-amp.

→ The off voltage is  $V_o = A_{OL}V_d$

$$= A_{OL}(V_1 - V_2)$$

→ The equation shows that the op-amp amplifies the difference between the 2 off voltages.

### Open Loop Operation of Op-Amp

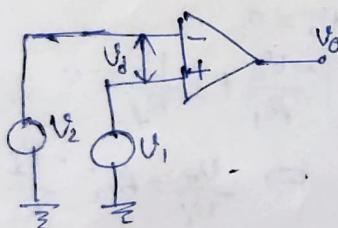

→ Since the gain is infinite, the off voltage  $V_o$  is either at its positive saturation voltage ( $+V_{sat}$ ) for  $V_1 > V_2$  or negative saturation voltage ( $-V_{sat}$ ) for  $V_2 > V_1$ .

→ The op assumes one of two possible off states, i.e.,  $+V_{sat}$  or  $-V_{sat}$  and the amplifier acts a switch only.

→ This has a limited number of applications such as voltage comparators, zero crossing detectors, etc.

### Feedback in Ideal Op-amp

→ The utility of an op-amp can be greatly increased by providing negative feedback.

→ The op in this case is not driven into saturation & the circuit behaves in a linear manner.

→ In order to understand the operation of feedback connections, we make two realistic simplifying assumptions

- i) The current drawn by either of the in terminals is negligible
- ii) The differential cap voltage  $V_d$  between non-inverting and inverting cap terminals is essentially zero.