

G. Narayanamma Institute of Technology & Science

(Autonomous) (for Women)

Shaikpet, Hyderabad- 500 104

II-B.Tech I-Semester Regular Examinations, March-2021.

DIGITAL SYSTEM DESIGN

(Common to ECE & ETE)

Max. Marks: 70

Time: 03 Hours

(Answer any 05 full questions. Each question carries 14 marks)

Q.No	Question	Marks	Bloom's Level
Q.1(a)	Solve $A - B$ using 2's complement if i) $A = (111.101)_2$ and $B = (101.110)_2$ ii) $A = (27)_8$ and $B = (16)_8$	[07]	[L3]
(b)	State and prove the Consensus theorem and De-Morgan's theorem with suitable examples.	[07]	[L2]
Q.2	Realize the following expression $F(A,B,C,D) = \sum m(0,1,2,3,4,7,9,11)$ using the following two level forms i) NAND-NAND ii) AND-OR iii) OR-AND iv) NOR-NOR	[14]	[L3]
Q.3(a)	Draw and explain TTL NAND logic with the help of truth table.	[07]	[L3]
(b)	Explain how a CMOS can be interfaced with ECL.	[07]	[L2]
Q.4(a)	Design a CMOS NAND and XNOR gates and explain the operation of the circuits.	[08]	[L4]
(b)	Compare CMOS, TTL and ECL with reference to digital IC constraints.	[06]	[L2]
Q.5(a)	Minimize the following Boolean expression using tabular method and realize using basic gates. $F(A, B, C, D) = \sum m(0,2,4,9,12,15) + \sum d(1,5,7,10)$	[08]	[L3]
(b)	Explain the operation of a 8x1 multiplexer with appropriate expression.	[06]	[L2]
Q.6(a)	Design a Binary to Gray code converter and realize the logic diagram.	[08]	[L6]
(b)	Differentiate PROM, PLA and PAL.	[06]	[L2]
Q.7(a)	Explain the operation of a Master-Slave JK flip flop with suitable timing Diagrams.	[08]	[L1]
(b)	Design a Serial Input – Parallel Output Shift Register and explain the operation.	[06]	[L2]
Q.8(a)	Draw an ASM chart to implement the function of Dice Game Controller.	[08]	[L4]
(b)	Explain the advantages of ASM over Conventional Flow Chart.	[06]	[L1]